

# **Chapter 2.4-2.7**


## **Introduction to VHDL**

**Version: 2023/11/21**

# Chapter 2 Introduction to VHDL

1	Computer-aided design	11	Simple synthesis examples
2	Hardware description language	12	VHDL models for multiplexers
3	VHDL description of combinational circuits	13	VHDL libraries
<b>4</b>	<b>VHDL modules</b>	14	Modeling registers and counters using VHDL processes
5	Sequential statements and VHDL processes	15	Behavioral and structural VHDL
6	Modeling flip-flop using VHDL processes	16	Variables, signals, and constants
7	Processes using wait statements	17	Arrays
8	Two types of VHDL delays: Transport and inertial delays	18	Loops in VHDL
9	Compilation, simulation, and synthesis of VHDL code	19	Assert and report statements
10	VHDL data types and operators		

## 2.4 VHDL Modules (模块)

 

```
entity two_gates is  
  port(A,B,D: in bit; E: out bit);  
end two_gates;
```


```
architecture gates of two_gates is  
  signal C: bit;  
begin  
  C <= A and B ; -- concurrent  
  E <= C or D ;  -- statements  
end gates;
```

**Library declaration**  
(库声明)

**Entity**  
(实体)



**Architecture**  
(结构体)

## 2.4 VHDL Modules

 


```
entity two_gates is  
  port(A,B,D: in bit; E: out bit);  
end two_gates;
```
  
```
architecture gates of two_gates is  
  signal C: bit;  
begin  
  C <= A and B ; -- concurrent  
  E <= C or D ;  -- statements  
end gates;
```



## 2.4 VHDL Modules

 

```
entity two_gates is
  port(A,B,D: in bit; E: out bit);
end two_gates;

architecture gates of two_gates is
  signal C: bit;
begin
  C <= A and B ; -- concurrent
  E <= C or D ;  -- statements
end gates;
```

C : internal signal

Concurrent statements are placed between **begin** and **end**

## 2.4 VHDL Modules

Entity and architecture  
at the top level

Entity  
Architecture

Entity  
Architecture

Module 1

Entity  
Architecture

Module 2

...


Entity  
Architecture

Module N

Entities and architectures for  
component modules

## 2.4 VHDL Modules

### Entity

 

```
entity two_gates is  
    port(A,B,D: in bit; E: out bit);  
end two_gates;
```

Interface signals can be used  
to connect to other modules  
or to the outside world

```
entity entity-name is  
    [port (interface-signal-declaration);]  
end [entity] [entity-name];
```

The items enclosed in **[ ]**  
are optional


## 2.4 VHDL Modules

```
entity entity-name is  
    [port (interface-signal-declaration) ;]  
end [entity] [entity-name];
```



```
list-of-interface-signals: mode type [:= initial-value]  
{; list-of-interface-signals: mode type [:= initial-value]};
```

Mode	Direction of information
<b>in</b>	input port signals
<b>out</b>	output port signals
<b>inout</b>	bidirectional signals

 

```
entity test is  
    port( CLK: inout bit);  
end test;  
|  
architecture equ of test is  
begin  
    CLK <= not CLK after 10 ns;  
end equ;
```



## 2.4 VHDL Modules

### Example: entity without port

```
entity test_code_conv is  
end test_code_conv;  
  
architecture tester of test_code_conv is  
  signal X, CLK Z: bit;  
  component Code_Converter is  
    port(X, CLK: in bit; Z: out bit);  
  end component;  
  begin  
    clk <= not clk after 100 ns;  
    X <= '0', '1' after 350 ns, '0' after 550 ns, '1' after  
        750 ns, '0' after 950 ns, '1' after 1350 ns;  
    CC: Code_Converter port map (X, clk, Z);  
end tester;
```

Example in Chp 2.19

## 2.4 VHDL Modules

### Type

```
list-of-interface-signals: mode type [:= initial-value]  
{; list-of-interface-signals: mode type [:= initial-value]};
```

bit, bit-vector, integer, ...

optional

### Initial value

### Example

A and B are initially set to 2

C and D are initially set to '0'

```
port (A, B: in integer := 2; C, D: out bit);
```

- The rules for initial values ensure that all simulations start from the same, known, state
- This means that identical simulations will give identical results even on different simulators

## 2.4 VHDL Modules

### Initial value

### Example

```
port (A, B: in integer := 2; C, D: out bit);
```

➤ These initial values are significant **only for simulation** and **not for synthesis**

- For synthesis, there is **no hardware interpretation** of an initial value
- It is not possible to initialize all signals in a circuit with a known value on power-up
- Even though it is possible to do a power-on reset in some logic technologies, it would not be desirable to do this for every wire in the circuit
- So, synthesis must ignore initial values

## 2.4 VHDL Modules

### Architecture

```
architecture gates of two_gates is
  signal C: bit;
begin
  C <= A and B ; -- concurrent
  E <= C or D ;  -- statements
end gates;
```


```
architecture architecture-name of entity-name is
  [declarations]
begin
  architecture body
end [architecture] [architecture-name];
```

[Declarations] (optional) declare internal signals and components (among others) used within the architecture

Architecture body contains statements that describe the operation of the module

## 2.4 VHDL Modules

### Full adder

 

**entity** FullAdder **is**  
    **port** (X, Y, Cin: **in** bit;   -- Inputs  
          Cout, Sum: **out** bit); -- Outputs  
**end** FullAdder;

$$Sum = X'Y'C_{in} + X'YC_{in}' + XY'C_{in} + XYC_{in} = X \oplus Y \oplus C_{in}$$

$$Cout = X'YC_{in} + XY'C_{in} + XYC_{in}' + XYC_{in} = XY + XC_{in} + YC_{in}$$

## 2.4 VHDL Modules

### Full adder

```
entity FullAdder is  
  port (X, Y, Cin: in bit;  -- Inputs  
        Cout, Sum: out bit); -- Outputs  
end FullAdder;
```

$$Sum = X'Y'C_{in} + X'YC_{in}' + XY'C_{in} + XYC_{in} = X \oplus Y \oplus C_{in}$$

$$Cout = X'YC_{in} + XY'C_{in} + XYC_{in}' + XYC_{in} = XY + XC_{in} + YC_{in}$$



```
architecture Equations of FullAdder is  
begin
```



```
  Sum <= X xor Y xor Cin after 10 ns;
```

```
  Cout <= (X and Y) or (X and Cin) or (Y and Cin) after 10 ns;
```

```
end Equations;
```

## 2.4.1 Four-bit full adder

### Adder4

 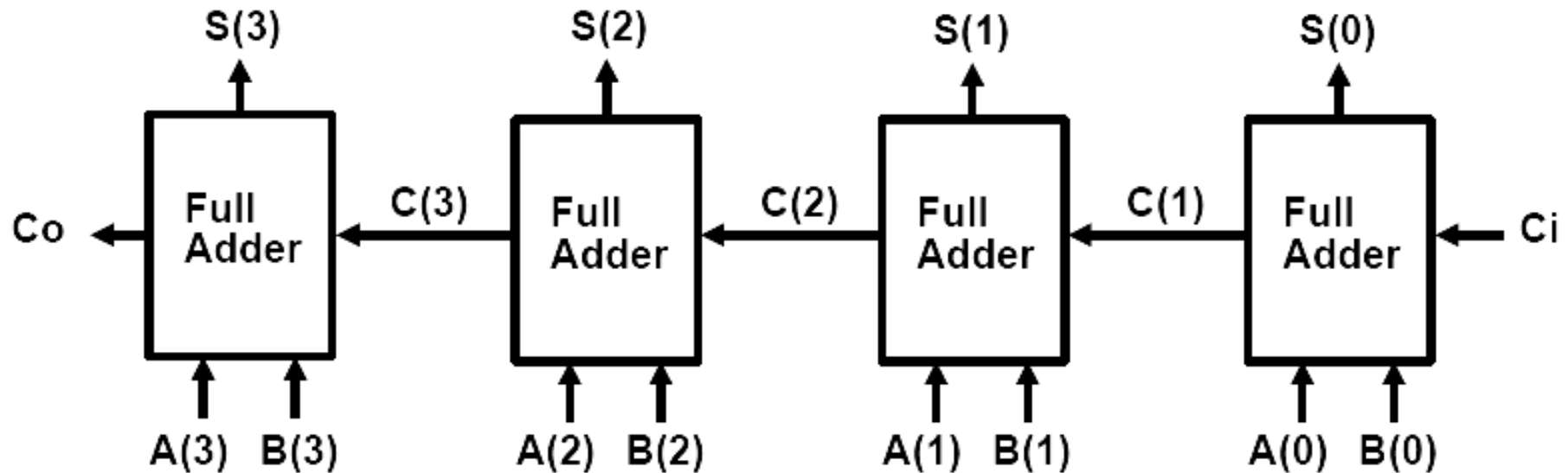

**entity FullAdder is**

**port** (X, Y, Cin: **in** bit; Cout, Sum: **out** bit);  
**end FullAdder;**


**architecture Equations of FullAdder is**  
**begin**

Sum <= X **xor** Y **xor** Cin **after** 10 ns;

Cout <= (X **and** Y) **or** (X **and** Cin) **or** (Y **and** Cin) **after** 10 ns;


**end Equations;**

## 2.4 VHDL Modules

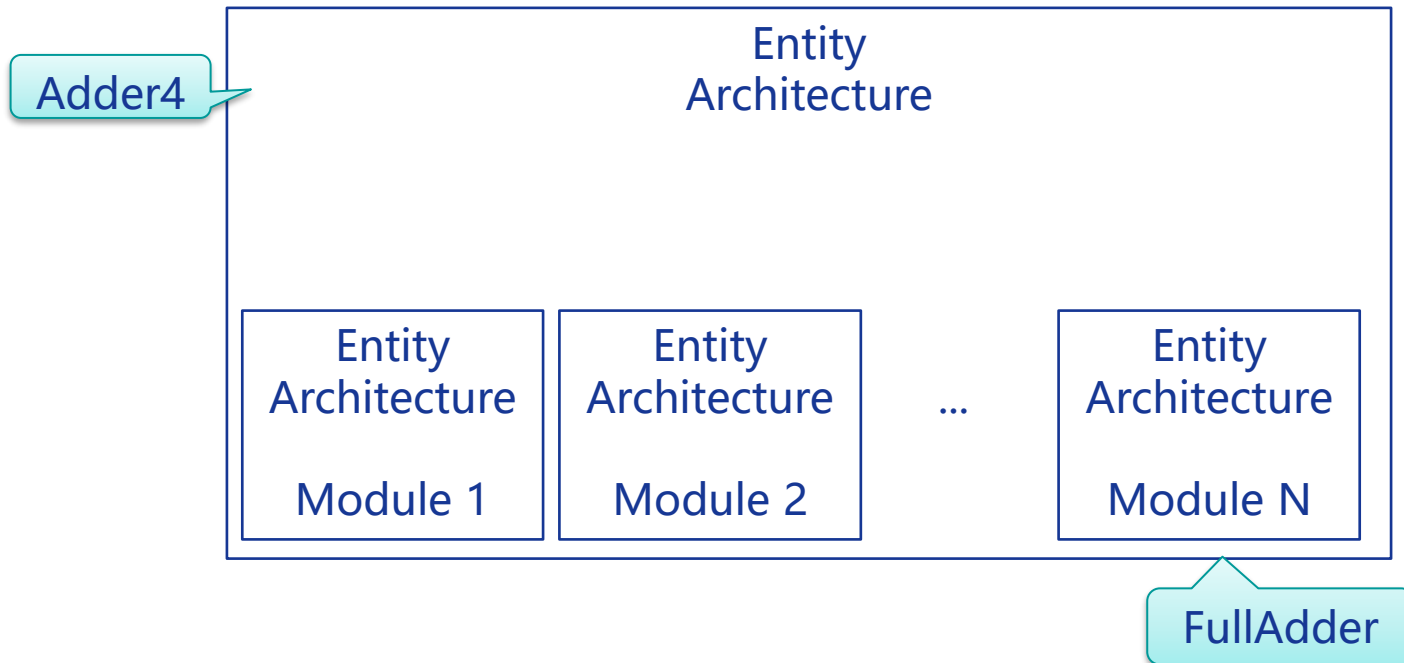




## 2.4.1 Four-bit full adder

 
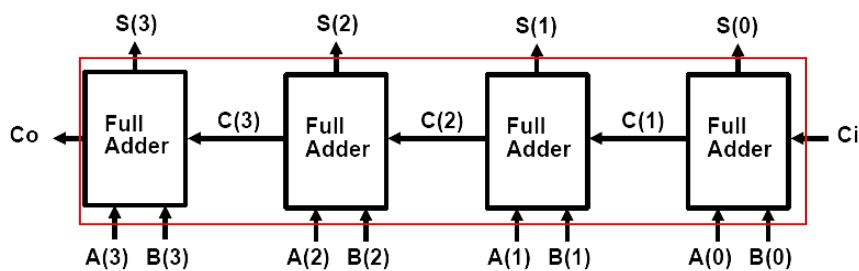
```
entity Adder4 is  
  port (A, B: in bit_vector(3 downto 0); Ci: in bit;  
        S: out bit_vector(3 downto 0); Co: out bit);  
end Adder4;
```



```
entity FullAdder is
  port (X, Y, Cin: in bit;
        Cout, Sum: out bit);
end FullAdder;
```

**entity Adder4 is**

```
  port (A, B: in bit_vector(3 downto 0); Ci: in bit;           -- inputs
        S: out bit_vector(3 downto 0); Co: out bit);          -- outputs
end Adder4;
```

**architecture Structure of Adder4 is**

**component FullAdder**

```
  port (X, Y, Cin: in bit;           -- Inputs
        Cout, Sum: out bit);         -- Outputs
end component;
```

**signal** C: bit\_vector(3 downto 1);

**begin** --instantiate four copies of the FullAdder

FA0: FullAdder **port map** (A(0), B(0), Ci, C(1), S(0));


FA1: FullAdder **port map** (A(1), B(1), C(1), C(2), S(1));

FA2: FullAdder **port map** (A(2), B(2), C(2), C(3), S(2));

FA3: FullAdder **port map** (A(3), B(3), C(3), Co, S(3));

**end Structure;**



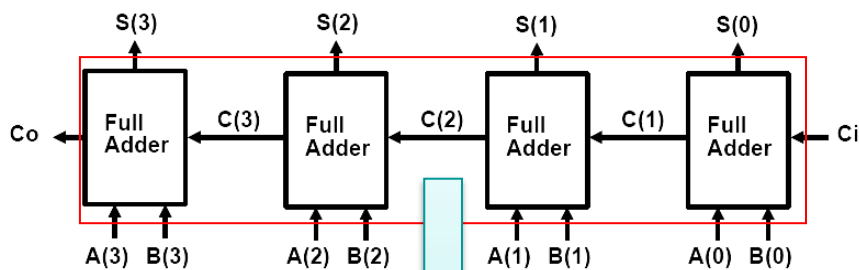

```
entity FullAdder is
  port (X, Y, Cin: in bit;
        Cout, Sum: out bit);
end FullAdder;
```


```
entity Adder4 is
  port (A, B: in bit_vector(3 downto 0); Ci: in bit;      -- Inputs
        S: out bit_vector(3 downto 0); Co: out bit);      -- Outputs
end Adder4;

architecture Structure of Adder4 is
  component FullAdder
    port (X, Y, Cin: in bit;      -- Inputs
          Cout, Sum: out bit);    -- Outputs
  end component;

  signal C: bit_vector(3 downto 1);

begin
  --instantiate four copies of the FullAdder
  FA0: FullAdder port map (A(0), B(0), Ci, C(1), S(0));
  FA1: FullAdder port map (A(1), B(1), C(1), C(2), S(1));
  FA2: FullAdder port map (A(2), B(2), C(2), C(3), S(2));
  FA3: FullAdder port map (A(3), B(3), C(3), Co, S(3));
end Structure;
```

3-bit internal carry signal

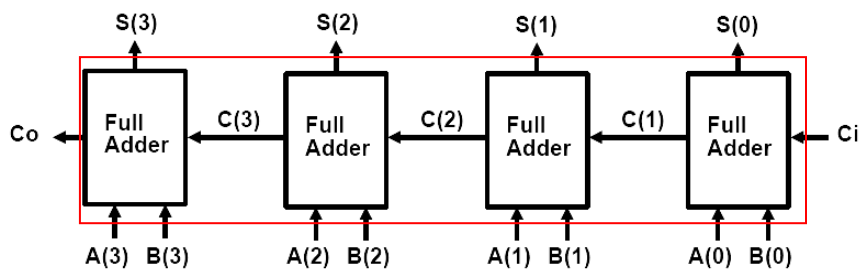

```
entity FullAdder is
  port (X, Y, Cin: in bit;
        Cout, Sum: out bit);
end FullAdder;
```

**entity Adder4 is**

```
  port (A, B: in bit_vector(3 downto 0); Ci: in bit;      -- Inputs
        S: out bit_vector(3 downto 0); Co: out bit);      -- Outputs
```

**end Adder4;**

**architecture Structure of Adder4 is**

**component FullAdder**

```
  port (X, Y, Cin: in bit;      -- Inputs
        Cout, Sum: out bit);    -- Outputs
```

**end component;**

**signal C: bit\_vector(3 downto 1);**


**begin** --instantiate four copies of the FullAdder

```
FA0: FullAdder port map (A(0), B(0), Ci, C(1), S(0));
FA1: FullAdder port map (A(1), B(1), C(1), C(2), S(1));
FA2: FullAdder port map (A(2), B(2), C(2), C(3), S(2));
FA3: FullAdder port map (A(3), B(3), C(3), Co, S(3));
```

**end Structure;**

label

port map

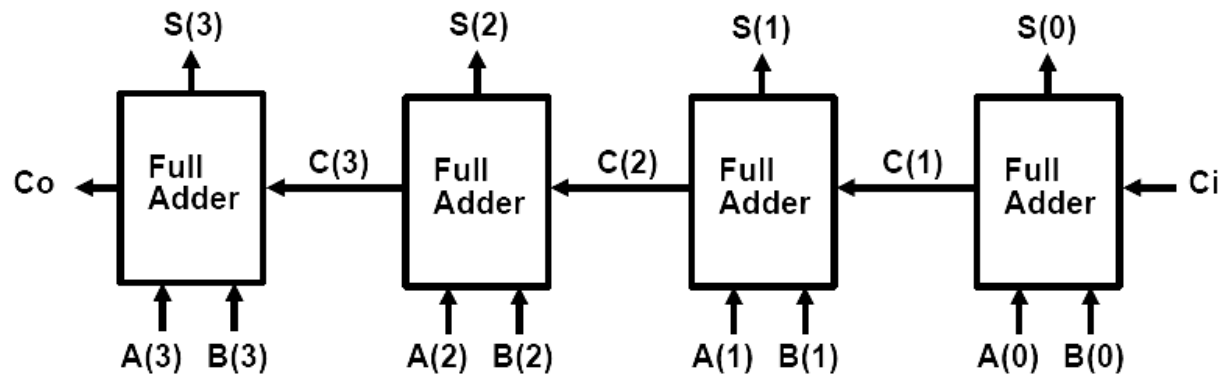

```

component FullAdder
  port (X, Y, Cin: in bit;           -- Inputs
        Cout, Sum: out bit);        -- Outputs
end component;

```

```

FA0: FullAdder port map (A(0), B(0), Ci, C(1), S(0));
FA1: FullAdder port map (A(1), B(1), C(1), C(2), S(1));
FA2: FullAdder port map (A(2), B(2), C(2), C(3), S(2));
FA3: FullAdder port map (A(3), B(3), C(3), Co, S(3));

```

The order of the signals must be the same as the order of the signals in the port of the component declaration  
(Positional Association)


```
component component-name  
    port(list-of-interface-signals-and-their-types);  
end component
```

Port clause used in component declaration  
has the same form as the port clause used in  
an entity declaration

```
label: component-name port map (list-of-actual-signal);
```

The list of actual signals must correspond  
**one-to-one** to the list of interface signals  
specified in the component declaration

# Simulation use ModelSim

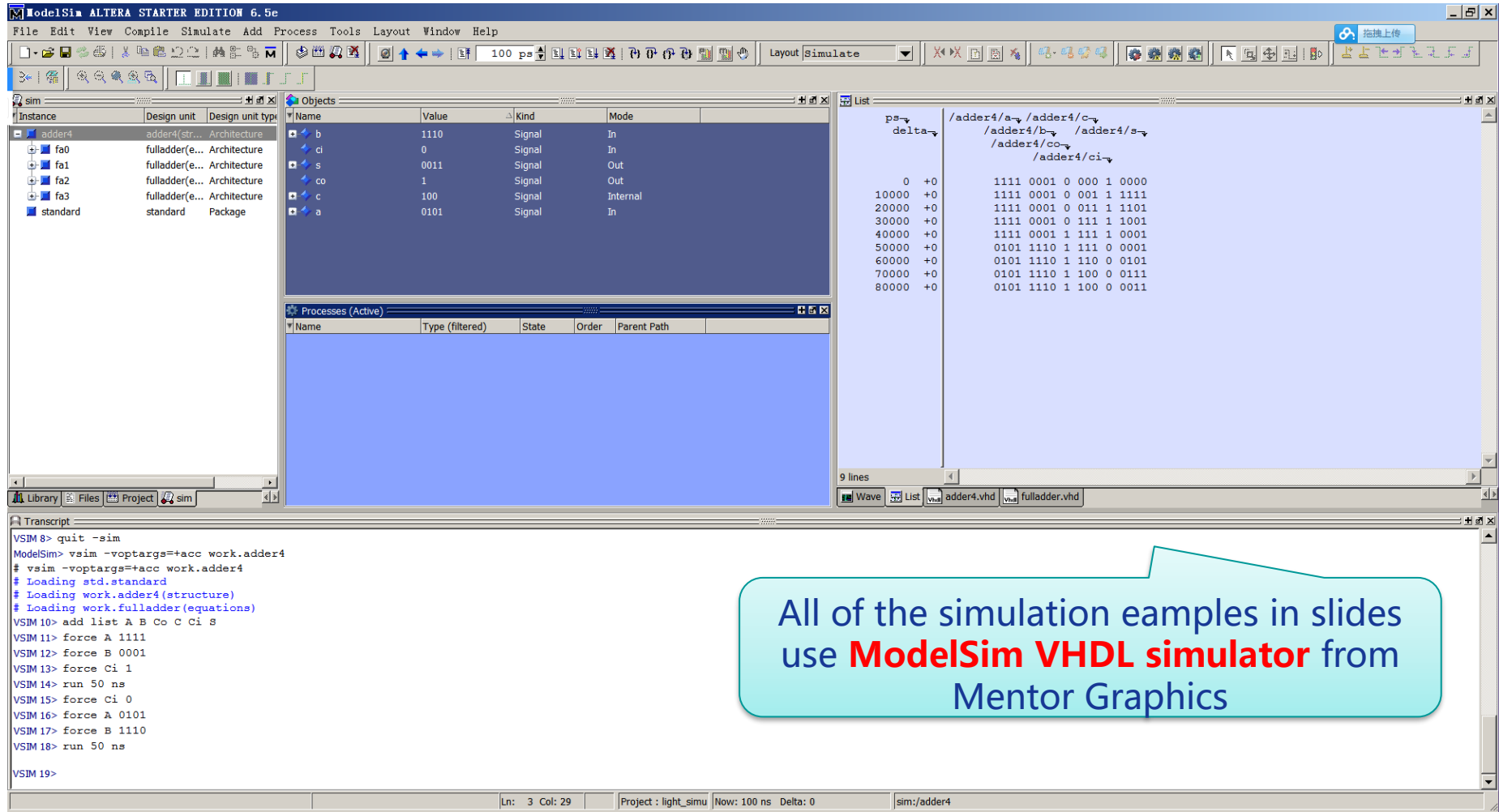

The screenshot displays the ModelSim ALTEA STARTER EDITION 6.5e interface. The main window is divided into several panes:

- Instance:** Lists the design units and their types. The 'adder4' instance is highlighted, showing its architecture as 'fulladder(e... Architecture'.
- Objects:** A table showing the signals and their values during simulation.
- Processes (Active):** A table showing the active processes and their states.
- List:** A window showing the simulation results, including the timing diagram for the adder's output 's'.
- Transcript:** A window showing the simulation commands and their results.

The simulation results in the List window show the output 's' for various input combinations of 'a' and 'b'.

The Transcript window shows the following commands and results:

```
VSIM 8> quit -sim
ModelSim> vsim -voptargs+=+acc work.adder4
# vsim -voptargs+=+acc work.adder4
# Loading std.standard
# Loading work.adder4(structure)
# Loading work.fulladder(equations)
VSIM 10> add list A B Co C Ci S
VSIM 11> force A 1111
VSIM 12> force B 0001
VSIM 13> force Ci 1
VSIM 14> run 50 ns
VSIM 15> force Ci 0
VSIM 16> force A 0101
VSIM 17> force B 1110
VSIM 18> run 50 ns
VSIM 19>
```


The status bar at the bottom indicates the current simulation time is 100 ns, and the delta time is 0.

All of the simulation examples in slides use **ModelSim VHDL simulator** from Mentor Graphics

# Simulation use ModelSim

## Create a New Project

**File > New > Project**

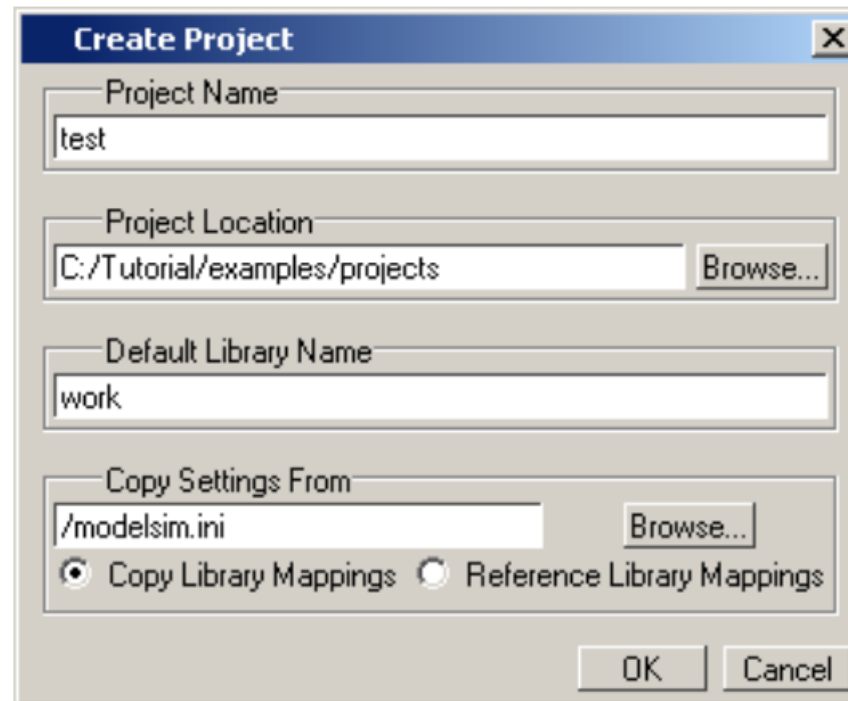

The image shows a 'Create Project' dialog box with the following fields and options:

- Project Name:** A text box containing the word 'test'.
- Project Location:** A text box containing the path 'C:/Tutorial/examples/projects' and a 'Browse...' button to its right.
- Default Library Name:** A text box containing the word 'work'.
- Copy Settings From:** A text box containing the path '/modelsim.ini' and a 'Browse...' button to its right.
- Copy Library Mappings:** A radio button that is selected.
- Reference Library Mappings:** An unselected radio button.
- Buttons:** 'OK' and 'Cancel' buttons at the bottom right.



# Simulation use ModelSim

ModelSim ALTERA STARTER EDITION 6.5e

File Edit View Compile Simulate Add Source Tools Layout Window Help

Layout NoDesign

GA\_Experiments/FPGA\_Experiments/ModelSim/light/light\_simu

Name	Status	Type	Order	Modified
fulladder.vhd	✓	VHDL	3	11/23/16 09:42:33 AM
light.vhd	✓	VHDL	0	10/11/16 04:20:38 PM
adder4.vhd	✓	VHDL	4	11/23/16 09:48:36 AM
test.vhd	?	VHDL	2	11/23/16 09:17:00 AM
lightVHD.vhd	✓	VHDL	1	10/12/16 02:18:56 PM

E:/Kuaipan/Teaching/FPGA/FPGA\_Experiments/FPGA\_Experiments/ModelSim/light/fulladder.vhd

```
Ln#
1  entity fulladder is
2      port( X, Y, Cin : in bit;
3            Cout, Sum : out bit);
4  end entity fulladder;
5
6  architecture Equations of fulladder is
7  begin
8      Sum  <= X xor Y xor Cin after 10 ns;
9      Cout <= (X and Y) or (X and Cin) or (Y and Cin) after 10 ns;
10 end architecture Equations;
```

fulladder

After 10 ns

Library Project

List adder4.vhd fulladder.vhd test.vhd

Transcript

```
# 1: ::vcop Action copy
VSIM 8> quit -sim
ModelSim>
```

Ln: 3 Col: 29 Project : light\_simu <No Design Loaded> <No Context>

# Simulation use ModelSim

The screenshot displays the ModelSim ALTERA STARTER EDITION 6.5e interface. The top menu bar includes File, Edit, View, Compile, Simulate, Add, Source, Tools, Layout, Window, and Help. The toolbar contains various icons for file operations, simulation, and layout. The left pane shows a project tree with the following files:

Name	Status	Type	Order	Modified
fulladder.vhd	✓	VHDL	3	11/23/16 09:42:33 AM
light.vhd	✓	VHDL	0	10/11/16 04:20:38 PM
adder4.vhd	✓	VHDL	4	11/23/16 09:48:36 AM
test.vhd	?	VHDL	2	11/23/16 09:17:00 AM
lightVHD.vhd	✓	VHDL	1	10/12/16 02:18:56 PM

The right pane shows the source code for `adder4.vhd` at line 19. The code defines a 4-bit adder entity and its architecture, which uses four fulladder components. A blue callout bubble with the text "adder4" points to the architecture section of the code.

```
1  entity adder4 is
2      port( A, B : in  bit_vector(3 downto 0);
3            Ci : in  bit;
4            S : out bit_vector(3 downto 0);
5            Co : out bit);
6  end entity adder4;
7
8  architecture structure of adder4 is
9      component fulladder
10         port( X, Y, Cin : in  bit;
11              Cout, Sum : out bit);
12     end component;
13     signal C: bit_vector(3 downto 1);
14     begin
15         FA0: fulladder port map (A(0), B(0), Ci,  C(1), S(0));
16         FA1: fulladder port map (A(1), B(1), C(1), C(2), S(1));
17         FA2: fulladder port map (A(2), B(2), C(2), C(3), S(2));
18         FA3: fulladder port map (A(3), B(3), C(3), Co , S(3));
19     end architecture structure;
```

The bottom pane shows the Transcript window with the following text:

```
# 1: ::vcop Action copy
VSI8> quit -sim
ModelSim>
```

The status bar at the bottom indicates the current line is 3, column is 10, the project is `light_simu`, and there is no design loaded.

# Simulation use ModelSim

## Compile the Design Units

**Compile > Compile**

## Load the Design

**Simulate > Start Simulation**

ModelSim ALTERA STARTER EDITION 6.5e

File Edit View Compile Simulate Add Process Tools Layout Window Help

100 ps

Layout Simulate

拖拽上传

sim

Instance	Design unit	Design unit type
adder4	adder4/str...	Architecture
fa0	fulladder(e...	Architecture
fa1	fulladder(e...	Architecture
fa2	fulladder(e...	Architecture
fa3	fulladder(e...	Architecture
standard	standard	Package

Objects

Name	Value	Kind	Mode
b	1110	Signal	In
ci	0	Signal	In
s	0011	Signal	Out
co	1	Signal	Out
c	100	Signal	Internal
a	0101	Signal	In

Processes (Active)

Name	Type (filtered)	State	Order	Parent Path
------	-----------------	-------	-------	-------------

List

```
ps-> /adder4/a-> /adder4/c->
delta-> /adder4/b-> /adder4/s->
/adder4/co->
/adder4/ci->

0 +0 1111 0001 0 000 1 0000
10000 +0 1111 0001 0 001 1 1111
20000 +0 1111 0001 0 011 1 1101
30000 +0 1111 0001 0 111 1 1001
40000 +0 1111 0001 1 111 1 0001
50000 +0 0101 1110 1 111 0 0001
60000 +0 0101 1110 1 110 0 0101
70000 +0 0101 1110 1 100 0 0111
80000 +0 0101 1110 1 100 0 0011
```


9 lines

Wave List vhd adder4.vhd vhd fulladder.vhd

Transcript

```
VSIM 8> quit -sim
ModelSim> vsim -voptargs="+acc work.adder4"
# vsim -voptargs="+acc work.adder4"
# Loading std.standard
# Loading work.adder4(structure)
# Loading work.fulladder(equations)
VSIM 10> add list A B Co C Ci S
VSIM 11> force A 1111
VSIM 12> force B 0001
VSIM 13> force Ci 1
VSIM 14> run 50 ns
VSIM 15> force Ci 0
VSIM 16> force A 0101
VSIM 17> force B 1110
VSIM 18> run 50 ns
VSIM 19>
```

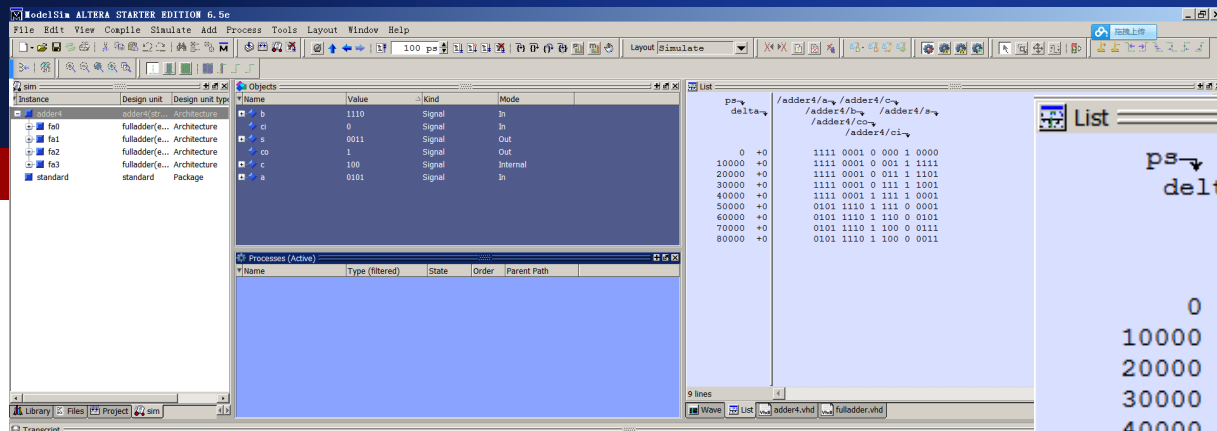Ln: 3 Col: 29 Project : light\_simu Now: 100 ns Delta: 0 sim:/adder4



ps	delta	/adder4/a	/adder4/b	/adder4/c	/adder4/co	/adder4/ci	/adder4/s
0	+0	1111	0001	0	000	1	0000
10000	+0	1111	0001	0	001	1	1111
20000	+0	1111	0001	0	011	1	1101
30000	+0	1111	0001	0	111	1	1001
40000	+0	1111	0001	1	111	1	0001
50000	+0	0101	1110	1	111	0	0001
60000	+0	0101	1110	1	110	0	0101
70000	+0	0101	1110	1	100	0	0111
80000	+0	0101	1110	1	100	0	0011

```

Transcript
VSI18> quit -sim
ModelSim> vsim -voptargs="+acc work.adder4
# vsim -voptargs="+acc work.adder4
# Loading std.standard
# Loading work.adder4(structure)
# Loading work.fulladder(equations)
VSI18> add list A B Co C Ci S
VSI11> force A 1111
VSI12> force B 0001
VSI13> force Ci 1
VSI14> run 50 ns
VSI15> force Ci 0
VSI16> force A 0101
VSI17> force B 1110
VSI18> run 50 ns
VSI19>

```

```


Transcript
VSI18> quit -sim
ModelSim> vsim -voptargs="+acc work.adder4
# vsim -voptargs="+acc work.adder4
# Loading std.standard
# Loading work.adder4(structure)
# Loading work.fulladder(equations)
VSI10> add list A B Co C Ci S
VSI11> force A 1111
VSI12> force B 0001
VSI13> force Ci 1
VSI14> run 50 ns
VSI15> force Ci 0
VSI16> force A 0101
VSI17> force B 1110
VSI18> run 50 ns
VSI19>

```


quit -sim
 
## 2.4 VHDL Modules



```
add list A B Co C Ci S  -- put these signal on the
output list
force A 1111          -- set the A inputs to 1111
force B 0001          -- set the B inputs to 0001
force Ci 1            -- set Ci to 1
run 50 ns              -- run the simulation for 50 ns
force Ci 0
force A 0101
force B 1110
run 50 ns
```



## 2.4 VHDL Modules

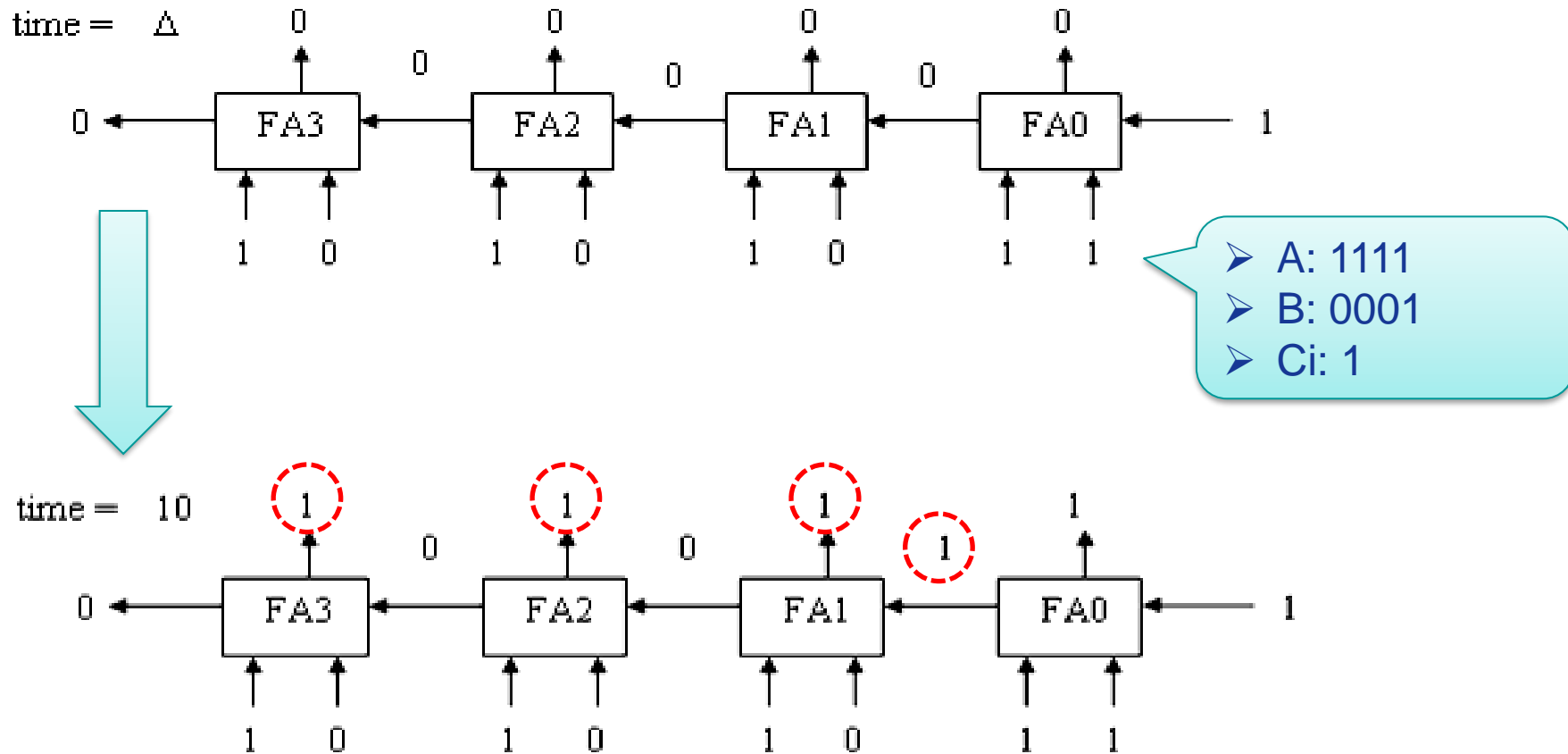


## 2.4 VHDL Modules

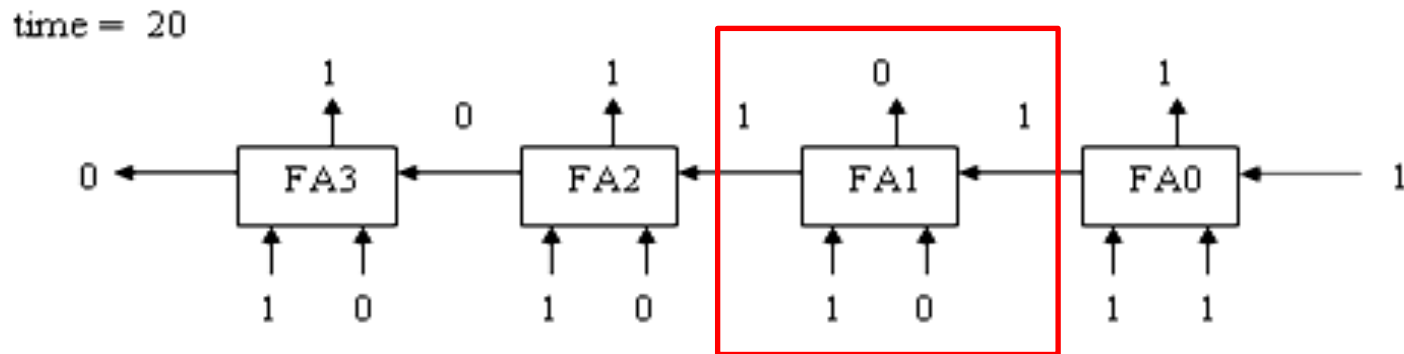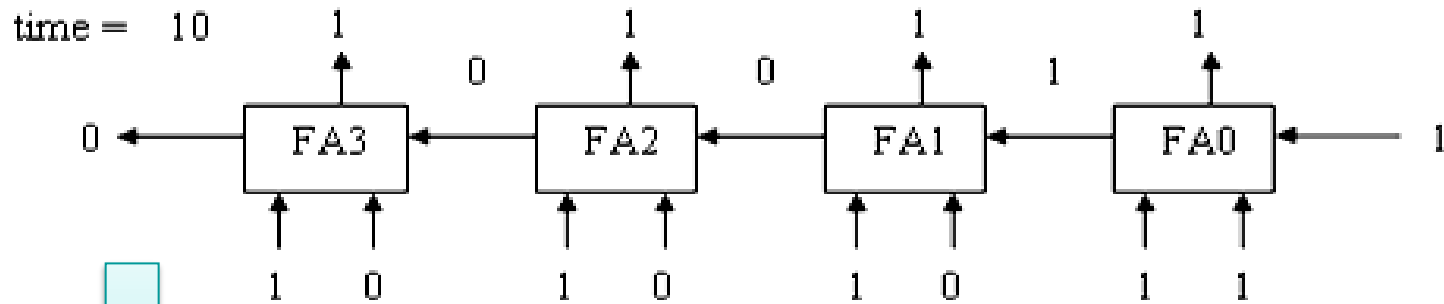






time = 20

 


time = 30

 

time = 30

  

time = 40

 

## 2.4.2 Use of "buffer" mode

```
entity gates is
    port(A, B, C: in bit; D, E: out bit);
end gates;

architecture example of gates is
begin
    D <= A or B after 5 ns; -- statement 1
    E <= C or D after 5 ns; -- statement 2
end example;
```

```
ModelSim> vcom figure2-13.vhd
# Model Technology ModelSim PE Student Edition vcom 10.4a Compiler 2015.03 Apr 7 2015
# Start time: 13:57:07 on May 04,2016
# vcom -reportprogress 300 figure2-13.vhd
# -- Loading package STANDARD
# -- Compiling entity gates
# -- Compiling architecture example of gates
# ** Error: figure2-13.vhd(8): Cannot read output "D".
#     VHDL 2008 allows reading outputs.
#     This facility is enabled by compiling with -2008.
# ** Error: figure2-13.vhd(9): VHDL Compiler exiting
# End time: 13:57:07 on May 04,2016, Elapsed time: 0:00:00
# Errors: 2, Warnings: 0
# C:/Modeltech_pe_edu_10.4a/win32pe_edu/vcom failed.
```

```
ModelSim> |
```

The code will not actually compile, simulate, or synthesize in many tools, why?

## 2.4.2 Use of "buffer" mode

```
entity gates is
    port(A, B, C: in bit; D, E: out bit);
end gates;

architecture example of gates is
begin
    D <= A or B after 5 ns; -- statement 1
    E <= C or D after 5 ns; -- statement 2
end example;
```

D is declared only  
as an **output**

D is used on the right side of  
the assignment (NOT allowed)

```
ModelSim> vcom figure2-13.vhd
# Model Technology ModelSim PE Student Edition vcom 10.4a Compiler 2015.03 Apr 7 2015
# Start time: 13:57:07 on May 04,2016
# vcom -reportprogress 300 figure2-13.vhd
# -- Loading package STANDARD
# -- Compiling entity gates
# -- Compiling architecture example of gates
# ** Error: figure2-13.vhd(8): Cannot read output "D".
#     VHDL 2008 allows reading outputs.
#     This facility is enabled by compiling with -2008.
# ** Error: figure2-13.vhd(9): VHDL Compiler exiting
# End time: 13:57:07 on May 04,2016, Elapsed time: 0:00:00
# Errors: 2, Warnings: 0
# C:/Modeltech_pe_edu_10.4a/win32pe_edu/vcom failed.
```

```
ModelSim>
```

## 2.4.2 Use of "buffer" mode

**entity** gates is

```
    port(A, B, C: in bit; D: inout bit; E: out bit);  
end gates;
```

**architecture** example **of** gates is  
**begin**

```
    D <= A or B after 5 ns;           -- statement 1  
    E <= C or D after 5 ns;         -- statement 2
```

**end** example

- Use of **inout** mode results in the synthesis tools creating a truly bidirectional signal
- D is **not an external input** to the circuit

## 2.4.2 Use of "buffer" mode

**entity** gates **is**

```
    port(A, B, C: in bit; D: buffer bit; E: out bit);  
end gates;
```


**architecture** example **of** gates **is**  
**begin**

```
    D <= A or B after 5 ns;           -- statement 1  
    E <= C or D after 5 ns;         -- statement 2
```

**end** example

- Mode **buffer** indicates a signal that is an output to the external world
  - Buffer value can also be read inside the entity's architecture
- 
- Another solution is to use an intermediate **internal signal** and read from that

## 2.4.2 Use of "buffer" mode

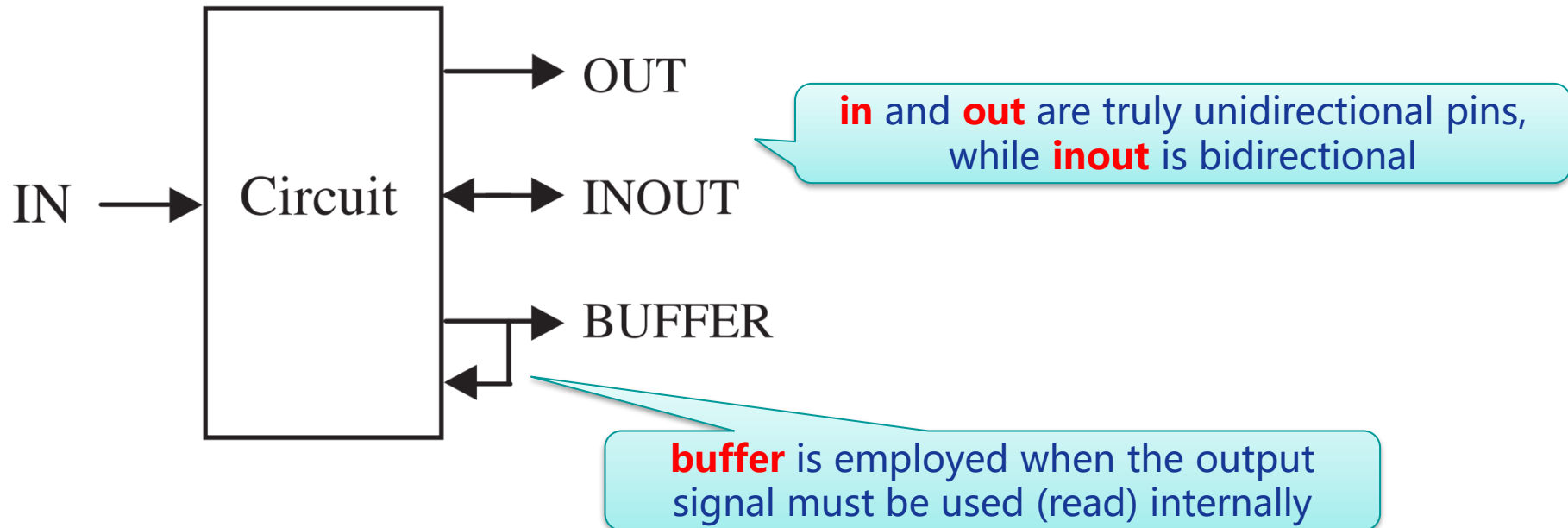

# Chapter 2 Introduction to VHDL

1	Computer-aided design	11	Simple synthesis examples
2	Hardware description language	12	VHDL models for multiplexers
3	VHDL description of combinational circuits	13	VHDL libraries
4	VHDL modules	14	Modeling registers and counters using VHDL processes
<b>5</b>	<b>Sequential statements and VHDL processes</b>	15	Behavioral and structural VHDL
6	Modeling flip-flop using VHDL processes	16	Variables, signals, and constants
7	Processes using wait statements	17	Arrays
8	Two types of VHDL delays: Transport and inertial delays	18	Loops in VHDL
9	Compilation, simulation, and synthesis of VHDL code	19	Assert and report statements
10	VHDL data types and operators		



## 2.5 Sequential statements and VHDL processes (进程)

- ❑ **Concurrent statements** are useful in modeling combinational logic
  - ❑ Combinational logic constantly reacts to input changes
  - ❑ In contrast, synchronous sequential logic responds to changes **dependent on the clock**
- 
- ❑ Many input changes might be ignored since output and state changes occur only at valid conditions of the clock
  - ❑ Modeling sequential logic requires primitives to model selective activity conditional on clock, edge-triggered devices, sequence of operations, and so on

To implement any clocked circuit (flip-flop, for example) we have to “force” VHDL to be **sequential**

## 2.5 Sequential statements and VHDL processes

**Process (进程)** executes whenever any signal in sensitivity list changes


```
process (sensitivity-list)
begin
    sequential-statements
end process;
```

Whenever one of the signals in sensitivity list changes

**Sequential statements** in process body are executed **in sequence one time**

## 2.5 Sequential statements and VHDL processes

```
process (sensitivity-list)
begin
    sequential-statements
end process;
```

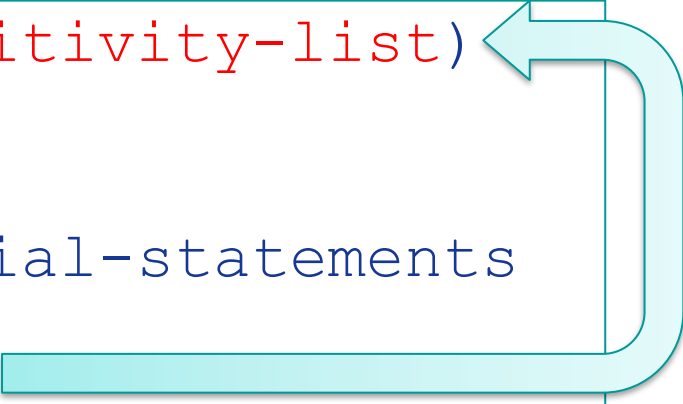A light blue arrow originates from the semicolon at the end of the 'end process;' line, extends horizontally to the right, then turns 90 degrees upwards and then 90 degrees to the left, pointing back to the 'sensitivity-list' parameter in the 'process' line.


When a process finished executing, it goes back to the beginning and waits for a signal on the sensitivity list to change again

- VHDL code is inherently concurrent. **Processes**, **functions**, and **procedures** are the only sections of code that are executed sequentially
- However, as a whole, any of these blocks is still **concurrent** with any other statements placed outside it
 
## 2.5 Sequential statements and VHDL processes

```
entity nogates is  
  port( A, B, C   : in      bit;  
         D         : buffer bit;  
         E         : out    bit);  
end nogates;
```

```
architecture behave of nogates is  
begin  
  process (A, B, C)  
  begin  
    D <= A and B after 5 ns; -- statement 1  
    E <= C or  D after 5 ns; -- statement 2  
  end process;  
end behave;
```




Process can be used to represent combinational logic

However, be careful!!!
 
# 2.5 Sequential statements and VHDL processes

```
entity nogates is
  port( A, B, C : in      bit;
        D       : buffer bit;
        E       : out    bit);
end nogates;
```




```
architecture behave of nogates is
begin
  process(A, B, C)
  begin
    D <= A and B after 5 ns; -- statement 1
    E <= C or D after 5 ns; -- statement 2
  end process;
end behave;
```


t(ns)	0	10	15	20	25
A	0				
B	1				
C	0				
D	0				
E	0				
 
## 2.5 Sequential statements and VHDL processes

```
entity nogates is
  port( A, B, C : in      bit;
        D       : buffer bit;
        E       : out    bit);
end nogates;
```




```
architecture behave of nogates is
begin
  process (A, B, C)
  begin
    D <= A and B after 5 ns; -- statement 1
    E <= C or D after 5 ns; -- statement 2
  end process;
end behave;
```

t(ns)	0	10	15	20	25
A	0 	1			
B	1	1			
C	0	0			
D	0	0			
E	0	0			
 
## 2.5 Sequential statements and VHDL processes

```
entity nogates is
  port( A, B, C   : in      bit;
        D         : buffer bit;
        E         : out    bit);
end nogates;
```




```
architecture behave of nogates is
begin
  process(A, B, C)
  begin
    D <= A and B after 5 ns; -- statement 1
    E <= C or D after 5 ns; -- statement 2
  end process;
end behave;
```

t	0	10	15	20	25
A	0	1	1		
B	1	1	1		
C	0	0	0		
D	0	0	1		
E	0	0	0		
 
## 2.5 Sequential statements and VHDL processes

```
entity nogates is
  port( A, B, C : in      bit;
        D       : buffer bit;
        E       : out    bit);
end nogates;
```



```
architecture behave of nogates is
begin
```

```
  process (A, B, C)
  begin
```

`D <= A and B after 5 ns; -- statement 1`

`E <= C or D after 5 ns; -- statement 2`

```
  end process;
```

```
end behave;
```

? If D is in the sensitivity list


t	0	10	15	20	25
A	0	1	1	1	1
B	1	1	1	1	1
C	0	0	0	0	0
D	0	0	1	1	1
E	0	0	0	0	0

E stays at '0'


 
## 2.5 Sequential statements and VHDL processes

```
entity nogates is
  port( A, B, C : in      bit;
        D       : buffer bit;
        E       : out    bit);
end nogates;
```




```
architecture behave of nogates is
begin
  process(A, B, C, D)
  begin
    D <= A and B after 5 ns; -- statement 1
    E <= C or D after 5 ns; -- statement 2
  end process;
end behave;
```

t	0	10	15	20	25
A	0	1			
B	1	1			
C	0	0			
D	0	0			
E	0	0			
 
## 2.5 Sequential statements and VHDL processes

```
entity nogates is
  port( A, B, C : in      bit;
        D       : buffer bit;
        E       : out    bit);
end nogates;
```



```
architecture behave of nogates is
begin
  process(A, B, C, D)
  begin
    D <= A or B after 5 ns; -- statement 1
    E <= C or D after 5 ns; -- statement 2
  end process;
end behave;
```


t	0	10	15	20	25
A	0	1	1	1	1
B	1	1	1	1	1
C	0	0	0	0	0
D	0	0	1	1	1
E	0	0	0	1	1

# Chapter 2 Introduction to VHDL

1	Computer-aided design	11	Simple synthesis examples
2	Hardware description language	12	VHDL models for multiplexers
3	VHDL description of combinational circuits	13	VHDL libraries
4	VHDL modules	14	Modeling registers and counters using VHDL processes
5	Sequential statements and VHDL processes	15	Behavioral and structural VHDL
6	<b>Modeling flip-flop using VHDL processes</b>	16	Variables, signals, and constants
7	Processes using wait statements	17	Arrays
8	Two types of VHDL delays: Transport and inertial delays	18	Loops in VHDL
9	Compilation, simulation, and synthesis of VHDL code	19	Assert and report statements
10	VHDL data types and operators		

## 2.6 Modeling flip-flops using VHDL processes

### D flip-flop

 


```
process (CLK)
begin
    if CLK'event and CLK = '1'
    then Q <= D;
    end if;
end process;
```

Rising edge of CLK

CLK'event is TRUE whenever  
CLK changes

## 2.6 Modeling flip-flops using VHDL processes

### D flip-flop

 

```
process (CLK)
begin
    if CLK'event and CLK = '1'
    then Q <= D;
    end if;
end process;
```

If VHDL is used only for simulation purposes, one might use a statement such as


**if CLK = '1' ...**

and obtain action corresponding to rising edge

When VHDL code is used to synthesize hardware


- **CLK='1'** results in **latches**
- **CLK'event** results in **edge-triggered** devices
 
## 2.6 Modeling flip-flops using VHDL processes



```
process (CLK)
begin
    if CLK'event and CLK = '1'
    then Q <= D;
    end if;
end process;
```

Flip-flop

 

```
process (CLK, D)
begin
    if CLK = '1'
    then Q <= D;
    end if;
end process;
```


Latch

```
Q <= D;
```

Wire

## 2.6 Modeling flip-flops using VHDL processes

### D flip-flop

 


```
process (CLK)
begin
    if CLK'event and CLK = '1'
        then Q <= D;
    end if;
end process;
```

D is not on the sensitivity list, why?

## 2.6 Modeling flip-flops using VHDL processes

### D flip-flop

 


```
process (CLK)
begin
    if CLK'event and CLK = '1'
        then Q <= D;
    end if;
end process;
```

For D flip-flop, changing D will not cause the flip-flop to change state



## 2.6 Modeling flip-flops using VHDL processes


### Transparent latch

 

```
process (G, D)
begin
    if G = '1'
        then Q <= D;
    end if;
end process;
```

## 2.6 Modeling flip-flops using VHDL processes


### D flip-flop

 

```
process (CLK)
begin
    if CLK'event and CLK = '1'
    then Q <= D;
    end if;
end process;
```

Both G and D are on the sensitivity list, why?

### Transparent latch

 


```
process (G, D)
begin
    if G = '1'
    then Q <= D;
    end if;
end process;
```

- Since if  $G = '1'$ , a change in  $D$  causes  $Q$  to change
- If  $G$  changes to  $'0'$ , the process executes, but  $Q$  does not change

## 2.6 Modeling flip-flops using VHDL processes


### D flip-flop with asynchronous clear

 

Active-low **asynchronous** clear input resets the flip-flop **independently of the clock**

## 2.6 Modeling flip-flops using VHDL processes

### D flip-flop with asynchronous clear

 

```
process (CLK, ClrN)  
begin  
    if ClrN = '0' then Q <= '0' ;  
    else  
        if CLK'event and CLK = '1' then Q <= D;  
        end if;  
    end if;  
end process;
```

ClrN overrides CLK

## 2.6 Modeling flip-flops using VHDL processes

### If statement

```
if condition then
    sequential statements1
else sequential statements2
end if;
```

The **condition** is a Boolean expression which evaluates to TRUE or FALSE

**if statements cannot be used as concurrent statements outside of a process**

### Nested ifs

```
if condition1 then
    sequential statements1
else if condition2 then
    sequential statements2
    else
        sequential statements3
    end if;
end if;
```

## 2.6 Modeling flip-flops using VHDL processes

### If statement


```
if condition then
    sequential statements
{elsif condition then
    sequential statements}
[else sequential statements]
end if;
```

Any number of **elsif** clauses  
may be included

**else** clause is optional

## 2.6 Modeling flip-flops using VHDL processes


### Nested ifs and elsifs

 


```
if (C1) then S1; S2;  
  else if (C2) then S3; S4;  
    else if (C3) then S5; S6;  
      else S7; S8;  
    end if;  
  end if;  
end if;
```

## 2.6 Modeling flip-flops using VHDL processes

### Nested ifs and elsif

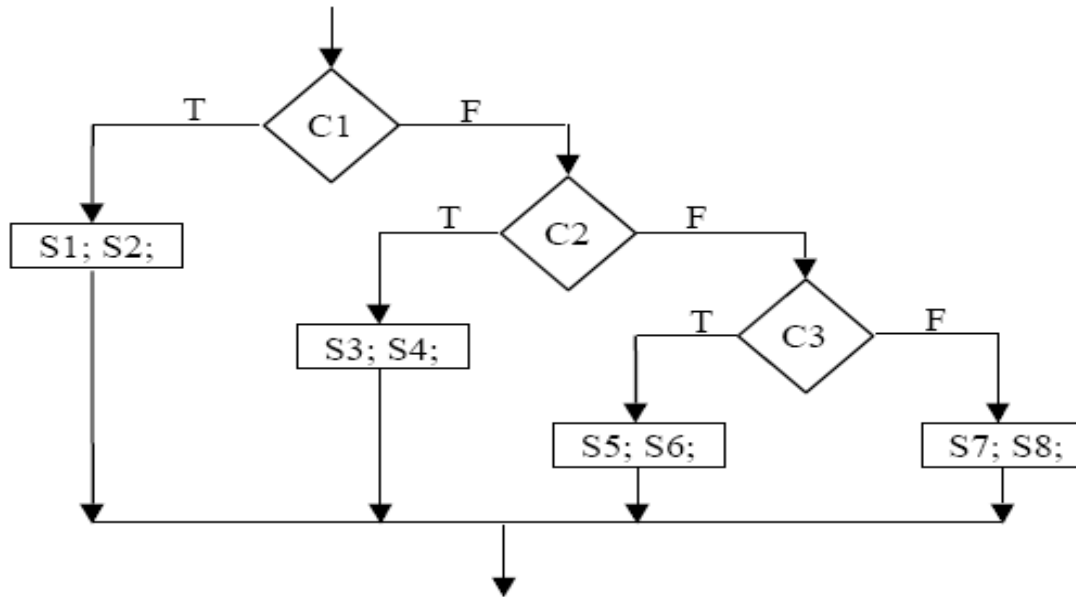
 
```
if (C1) then S1; S2;  
  else if (C2) then S3; S4;  
    else if (C3) then S5; S6;  
      else S7; S8;  
    end if;  
  end if;  
end if;
```




```
if (C1) then S1; S2;  
  elsif (C2) then S3; S4;  
  elsif (C3) then S5; S6;  
  else S7; S8;  
end if;
```




## 2.6 Modeling flip-flops using VHDL processes

### Nested ifs and elsif

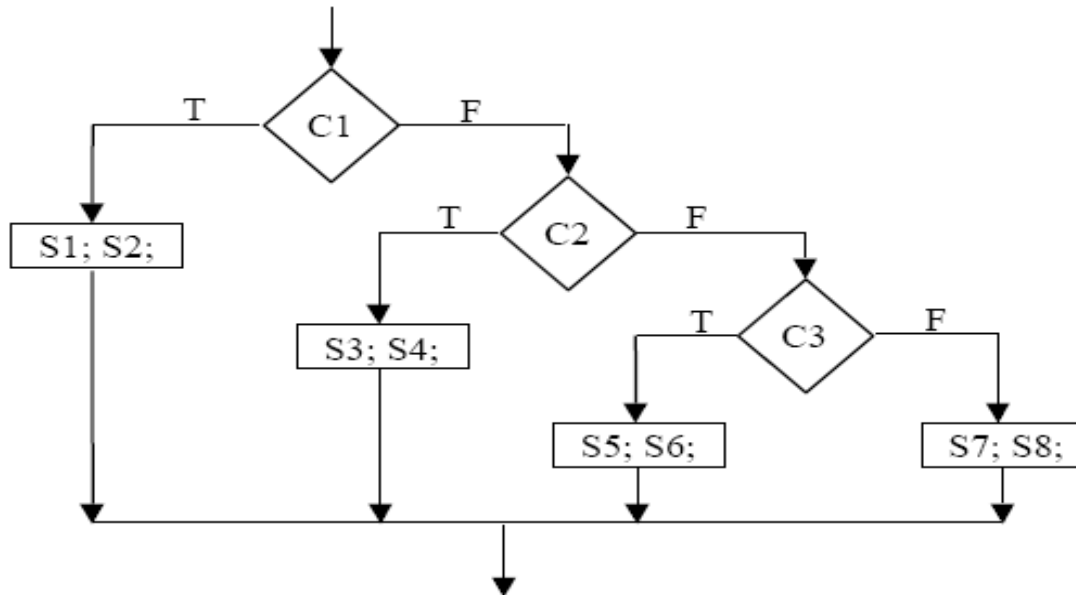
 
```
if (C1) then S1; S2;  
  else if (C2) then S3; S4;  
    else if (C3) then S5; S6;  
      *  
    end if;  
  end if;  
end if;
```




```
if (C1) then S1; S2;  
  elsif (C2) then S3; S4;  
  elsif (C3) then S5; S6;  
  else S7; S8;  
end if;
```

Each **if** requires a corresponding **end** **if**, but **elsif**s do not

## 2.6 Modeling flip-flops using VHDL processes

### J-K flip-flop

 


SN : active-low asynchronous preset  
RN : active-low asynchronous clear

For simplicity, we will assume that  
the condition  $SN = RN = 0$  does not  
occur

```
entity JKFF is
    port(
        SN, RN, J, K, CLK: in bit;           -- inputs
        Q, QN: out bit);
end JKFF;
```

# J-K flip-flop

 

J	K	Q+
0	0	Q
0	1	0
1	0	1
1	1	Q'

$$Q^+ = JQ' + K'Q$$

```
architecture JKFF1 of JKFF is
  signal Qint: bit;
begin
  Q <= Qint;
  QN <= not Qint;

  process(SN, RN, CLK)
  begin
    if RN = '0' then Qint <= '0' after 8 ns;
    elsif SN = '0' then Qint <= '1' after 8 ns;
    elsif CLK'event and CLK = '0' then
      Qint <= (J and not Qint) or (not K and Qint) after 10 ns;
    end if;
  end process;
end JKFF1;
```

-- Qint can be used as input or output

-- output Q and QN to port

-- combinational output

-- outside process

-- RN = '0' will clear the FF

-- SN = '0' will set the FF

# J-K flip-flop

architecture JKFF1 of JKFF is

signal Qint: bit;

begin

Q <= Qint;

QN <= not Qint;

process(SN, RN, CLK)

begin

if RN = '0' then Qint <= '0' after 8 ns;

elsif SN = '0' then Qint <= '1' after 8 ns;

elsif CLK'event and CLK = '0' then

Qint <= (J and not Qint) or (not K and Qint) after 10 ns;

end if;

end process;

end JKFF1;

-- Qint can be used as input or output


-- output Q and QN to port

-- combinational output

-- outside process

-- RN = '0' will clear the FF

-- SN = '0' will set the FF

 


- Within architecture we define a signal **Qint** that represents the state of the flip-flop internal to the module
- Two concurrent statements transmit Qint to the **Q** and **QN** output of the flip-flop, WHY?

# J-K flip-flop

```
entity JKFF is
    port(    SN, RN, J, K, CLK: in bit;           -- inputs
           Q, QN: out bit);
end JKFF;

architecture JKFF1 of JKFF is
    signal Qint: bit;                            -- Qint can be used as input or output
begin
    Q <= Qint;                                   -- output Q and QN to port
    QN <= not Qint;                             -- combinational output
                                                -- outside process

     process(SN, RN, CLK)
    begin
        if RN = '0' then Qint <= '0' after 8 ns;    -- RN = '0' will clear the FF
        elsif SN = '0' then Qint <= '1' after 8 ns; -- SN = '0' will set the FF
        elsif CLK'event and CLK = '0' then
            Qint <= (J and not Qint) or (not K and Qint) after 10 ns;
        end if;
    end process;
end JKFF1;
```



We do it this way because an output signal in a port cannot appear on the right side of an assignment statement within the architecture

# Chapter 2 Introduction to VHDL

1	Computer-aided design	11	Simple synthesis examples
2	Hardware description language	12	VHDL models for multiplexers
3	VHDL description of combinational circuits	13	VHDL libraries
4	VHDL modules	14	Modeling registers and counters using VHDL processes
5	Sequential statements and VHDL processes	15	Behavioral and structural VHDL
6	Modeling flip-flop using VHDL processes	16	Variables, signals, and constants
7	<b>Processes using wait statements</b>	17	Arrays
8	Two types of VHDL delays: Transport and inertial delays	18	Loops in VHDL
9	Compilation, simulation, and synthesis of VHDL code	19	Assert and report statements
10	VHDL data types and operators		

## 2.7 Processes using wait statements

```
process
```

```
begin
```

```
    sequential-statements
```

```
    wait-statement
```

```
    sequential-statements
```

```
    wait-statement
```

```
    ...
```

```
end process;
```

An alternative form for a process uses **wait** statements instead of a sensitivity list

The process will wait until the specified wait condition is satisfied

# Forms of wait statements

**wait on** sensitivity-list;

waits until one of the signals on the sensitivity-list changes

**wait for** time-expression;

waits until the time specified by the time-expression has lapsed

Not synthesizable

If **wait for 0 ns** is used, the wait for one delta time

**wait until** Boolean-expression;

Boolean-expression is evaluated whenever one of the signal in the expression changes

The process continues execution when the expression evaluates to **TRUE**



## 2.7 Processes using wait statements

```
process (A, B, C, D)
begin
    C<= A and B after 5ns;
    E<= C or B after 5ns;
end process;
```



```
process
begin
    C<= A and B after 5ns;
    E<= C or B after 5ns;
    wait on A,B,C,D;
end process;
```

After a VHDL simulator is initialized, it executes each process with a sensitivity list one time through

## 2.7 Processes using wait statements

```
process
begin
    wait until clk'event and clk='1';
    A <= E after 10ns;           -- (1)
    B <= F after 5ns;           -- (2)
    C <= G;                     -- (3)
    D <= H after 5ns;           -- (4)
end process;
```

The order in which sequential statements execute in a process is **not necessarily** the order in which the signal are updated

## 2.7 Processes using wait statements

```
process (CLK)
begin
    if CLK'event and CLK='0' then
        Q <= A;
        Q <= B;
        Q <= C;
    end if;
end process;
```


Every time CLK changes from '1' to '0',  
after delta time, Q will change to C

**If several VHDL statements in a process update the same  
signal at a given time, the last value overrides**
 
## 2.7 Processes using wait statements

```
entity gates is
    port(A, B, C: in bit; D, E: out bit);
end gates;

architecture exam of gates is
begin
    process
    begin
        D <= A or B after 2 ns;
        E <= not C and A;
    end process;
end exam;
```



(vcom-1090) Possible infinite loop: Process contains no WAIT statement.

A process must have either a sensitivity list or wait statements

A process cannot have both wait statements and a sensitivity list