

-**ALU:** Arithmetic Logic Unit: **-FPGA:** Field Programmable Gate Array **-HDL:** Hardware Description Language **-VHDL:** Very-High-Speed Integrated Circuit Hardware Description Language **-Verilog:** Verify Logic **-VHSIC:** Very-High-Speed Integrated Circuit **-CH1:**

-**Combinational logic:** 当前输出只与当前输入有关  
-**Sequential logic:** present output depends on the present input and past sequence of inputs

-**Boolean Algebra and Algebra Simplification:**  
分配律  $X+YZ=(X+Y)(X+Z)$  化简定理  $X(X+Y)=X$   
 $XY+Y=XY$   $XY+YZ+XZ=XY+XZ$

-**DeMorgan:**  $\overline{(X1X2...0n1,+)}=\overline{(X1'X2'...Xn,1,0,+)}$   
-**Duality:**  $\overline{\overline{(X1X2...Xn,0,1,+)}}=\overline{(X1'X2'...Xn,1,0,+)}$   
注意替换顺序, 先取反后变号  $(A+BC)=(A+B)(A+C)$

-**Karnaugh maps:** 相邻的两个方块之间只有一个变量不同; 最上面一行和下面一行是相邻的, 左右也是  
-**don't care:** 不会出现或者该组合未定义。  
-**prime implicant 质蕴涵项:** 1,2,4个相连的 1;基本质蕴涵项是至少包含一个其他质蕴涵项没有的 1 的项

**MinSOP 最小与或; Zmi MinPOS 最小或与表达; Fmi MinSOP = MinPOS** 利用 DeMorgan laws 转化


- **NAND and NOR Gates**

**-Static 1/0-hazard:**保持应该是保持 1/0 但有时候变成 0/1  
A static 1-hazard occurs in a SOP implementation when two minterms differing by only one input variable are not covered by the same product term  
-**Dynamic hazard:** 当输出应该从 1 到 0 或者反过来时, 的 output 可能产生三个 or more times  
-**触发器只有在使能信号上升和下降的时候内容才会变化, 但是锁存器的变化是 immediately**

-**Clocked D flip-flop(rising):**  $Q^+=Q$   
-**Clocked J-K flip-flop(falling):**  $Q^+=Q^+K^+Q^+$   
-**Clocked T flip-flop(rising):**  $Q^+=QT^+Q^+T^+Q^+orT^+$   
-**S-R (set-reset) latch:**  $Q^+=S^+R^+Q^+$   
-**Gated D latch:**  $Q^+=GD^+G^+Q^+DQ^+$

-**Mealy Circuit:** 输出与当前状态和当前输入有关  
-**Moore Circuit:** 输出只与当前状态有关, 但可以有输入  
-**最优状态分配:** 1.States which have the same next state (NS) for a given input should be given adjacent assignments 2. States that are the next states of the same state should be given adjacent assignments 3. States that have the same output for a given input should be given adjacent assignments **to clump 1's together on K-map**

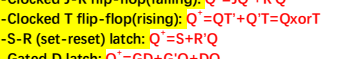-**状态等价:** 两个状态对应的充要条件是对于每个输入 X 输出都一样并且下一个状态都一个样。  
-**-Tristate logics:**



-**CH2**  
-**VHDL intro:** The actual circuit will depend on the compiler/optimizer being used: Top-down design; 1.Behavioral level: 行为级, 无需给出逻辑表达式; Data flow level: 数据流级, 需给出逻辑方程; Structural level: 结构级, 指定添加电路的端口和门之间的互连;  
-**Concurrent statements:** 并列, 语句右边的值变化就会马上执行; 如果没有限定 delay, **delay=delta**  
-**the time statement executes\*the time signal updated**  
-**标识符命名规则:** 字母开头, 可由字母、数字、下划线组成, 不能以下划线结尾, 不能使用保留字;  
-**初始值:** 只对仿真有意义 :=  
-**Buffer mode:** 表明是对外部世界的输出同时也能被结构里读, inout 表示是双向但是不是电路的外部输入

-**Process:** 当 sensitive list 里的信号发生变化之后进程开始执行, 结束后再返回开头等待敏感列表里面信号变化  
Processes, functions, and procedures are the only sections of code that are executed sequentially 但是这些代码块和外部的信号依然是并发的; if 语句不能用作进程外的并

-**发语句:** 函数中禁止进行信号声明和元件实例化  
-**wait:** 对于进程的敏感列表的替代方式是使用 wait 语句 **wait on sensitivity-list;** 等待列表中信号发生变化

wait for time-expression; 等待一段时间时间过

wait for 0 ns = wait for a delta time

**wait until** Boolean-expression; 当表达式中的信号变化时 对表达式估值, 为真就继续运行, 如果多个语句对一个信号赋值, 最后的赋值会 override 一个进程必须且只能包含敏感列表或者 wait 语句之一

-**delay:** 分为传输延时和惯性延时  
-**Transport delay:** 单纯延时  
**signal <= transport expression** after delay-time;  
bit vector(15 downto 0);  
-**Inertial delays(d):** 不会将过短的脉冲从输入给输出, 如果脉冲宽度小于 pulse-width 就消除 signal\_name <= reject pulse-width inertial expression after delay-time;

实际上使用 reject 相当于用二者的组合: **Z3 <= reject 4 ns inertial X after 10 ns;** 等价于 **Zm <= X after 4 ns;** **Z3 <= transport Zm after 6 ns;**

-**Simulation:** 1.Analysis (compilation)分析 (编译) 2. Elaboration 细化 3. Simulation 仿真  
-**Elaboration:** ① Ports are created for each instance of a component ②Memory storage is allocated for the required signals ③The interconnections among the port signals are specified ④A mechanism is established for executing VHDL statements in the proper sequence;

⑤The resulting data structure represents the digital system being simulated;  
-**如果一个 model 里面有多进程, 他们是并行的, 这些进程和其他的语句也是并行的。** A process **takes no time** to execute unless it has wait statements in it. Signals **take delta time** to update when no delay is specified;

-**Data types:** Real and time types are **not synthesizable** VHDL 是强类型, 如果类型不匹配那么需要显式的类型转换或者重载运算符  
example: Ci 为 bit 类型, A, B, Sum, of unsigned, 则应 **sum<='0' & A+B;unsigned('0'=>Ci1);** bit 不能直接与 unsigned 相加。

-**Operators:** 从下到上优先级降低  
1 Binary logical and or nand nor xor nxor  
2 Relational = /= < <= > >=  
3 Shift sll srl sla sra rol ror  
4 Adding + - &  
5 Unary sign + -  
6 Multiplying \* / mod rem  
7 Miscellaneous not abs \*\*

-**shift:** l = logical, a = arithmetic  
sll: 左移补零 srl:右移补零 rol: 循环左移 ror: 循环右移  
sla: 左移用最右边的位 sra: 右移用最左边的位补  
example: A = "10010101"; A sll 2="01010100"; A sla 3 = "10101111"; A ror 5 = "10101100"

-**条件信号赋值(simple when);**  
signal\_name <= expression1 when condition1  
{else expression2 when condition2}  
{else expressionN};  
-**选择信号赋值(selected when);条件完全 others 可省略**  
with expression\_s select  
signal\_s <= expression1 [after delay-time] when choice1,  
expression2 [after delay-time] when choice2,  
...[expression\_n [after delay-time] when others];  
-**case (这个在 process 里用, 上面两个都是并发的)**  
case expression is  
when choice1 => sequential statement1  
when choice2 => sequential statement2  
...[when others => sequential statements]  
end case;

-**IEEE:** Institute of Electrical and Electronic Engineers.  
-**IEEE.std\_logic:** has nine values, including '0', '1', 'X'(unknown), and 'Z' (high impedance) 没有运算  
-**IEEE.numeric\_bit** 带有符号数用补码表示, 有运算重载  
"011"+ "110" => "1011" + "0110" => "0001" 进位被掉  
-**Variables:** 信号在 "延迟后更新" (new value 必须保留可用) only available at the conclusion of the Process, Function, or Procedure), 变量立即更新; 信号用 <= 赋值, 变量用 := 赋值; 信号必须在进程外声明和初始化, 变量必须在进程里; 变量的更新是立即的, 后续计算会用新值。  
-**数组:** 声明类型  
type SHORT\_WORD is array (3 downto 0) of bit;  
实例 signal word1; short\_word := "1101";  
-**多维数组:** 声明类型: type matrix is array (1 to 4, 3 downto 1) of integer;  
实例 variable mat : matrix := ( (1,2,3), (4,5,6), (7,8,9), (10,11,12) );

矩阵索引: mat(2,1), 第 2 行最后一个;

-**无约束数组:** 声明无约束数组: type int\_vec is array (natural range<>) of integer, 实例必须指明 range:  
signal int\_vec5 : int\_vec(1 to 5) := (3, 2, 6, 8, 1); 声明字符串: type string is array (positive range <>) of character; 实例: constant string1 : string(1 to 29) := "This string is 29 characters."

-**Subtype:** 在声明类型之后, 可以声明相关的子类型以包含该类型指定的值的子集。subtype short\_word is bit\_vector(15 downto 0);  
-**Loop:** [loop-label:] loop sequential statements end loop [loop-label]; exit: exit;或者 exit when condition; loop 是 sequential 的, 只能在进程函数过程里面用, 对于 for-loop: [loop-label:] for loop-index in range loop sequential statements end loop [loop-label]; loop-index 是 loop 循环之后自动定义的, 不能被更改, 但可以使用, 进入循环后不可用 [loop-label:] while condition loop sequential statements end loop [loop-label];

IF, WAIT, CASE, LOOP are intended exclusively for sequential code, They can only be used inside a PROCESS (进程), FUNCTION (函数) or PROCEDURE (过程)

**CH3**  
-**FPGA intro:** FPGA is IC(集成电路) that contain an array of identical logic blocks with programmable interconnections. The user can program the functions realized by each logic block and the connections between the blocks. FPGAs are less dense than traditional gate arrays. In FPGAs, a lot of resources are spent merely to achieve the needed programmability. Programmable points have resistance and capacitance. They slow down signals, so FPGAs are slower than traditional gate arrays. Interconnection delays are unpredictable in FPGAs.

"Field" programmability is achieved by reconfigurable elements(可被用户控制). FPGA 内部通常包含三个元素: Programmable logic blocks, Programmable input/output blocks, Programmable routing resources.

-**MPGA:** mask programmable gate arrays.  
-**Layout of FPGA:** Arrays of programmable logic blocks are distributed within FPGA. Logic blocks are surrounded by input/output interface blocks. These I/O blocks can be considered to be on the periphery of the chip. They connect the logic signals to FPGA pins. The space between the logic blocks is used to route connections between the logic blocks.

-**Programmable logic blocks:** created by using multiplexers, look-up tables, and AND-OR or NAND-NAND arrays. Programming means: ① changing the input or control signals to the multiplexers. ② changing the look-up table contents. ③ selecting or not selecting particular gates in AND-OR gate blocks.

-**Programmable interconnect:** be required to interconnect various blocks in the chip and to connect specific I/O pins to specific logic blocks. Programming means making or breaking specific connections.

-**Programmable I/O blocks:** can be programmed to be input, output, or bidirectional lines(双向线路)。  
The general-purpose interconnect gives FPGA a lot of flexibility But it has the disadvantage of being slow

-**Architectures for FPGAs:** Matrix-based(symmetrical array) architecture: 矩阵(对称阵列型). Row-based architecture: 横向型. Hierarchical PIL architecture: 从属型. Sea-of-gate architecture: 门海型, classification is based on the layout of the general purpose logic region in the FPGA

-**Matrix-based Architecture:** The logic blocks are organized in a matrix-like fashion. The logic blocks in these architectures are typically of a large granularity(粒度) ( capable of implementing 4-variable functions or more). These architectures typically contain 8\*8 arrays in the smaller chips and 100\*100 or larger arrays in the bigger chips. 二维通道布线 Two-dimensional channelled routing: routing resources are generally available in horizontal and vertical directions

-**Row-based architecture:** The logic blocks in this architecture are organized into rows. There are rows of logic blocks and routing resources. 二维通道布线 One-dimensional channelled routing: the routing resources are located as a channel in between rows of logic resources.

-**Hierarchical architecture:** Blocks of logic cells are grouped together by a local interconnect. Several such groups are interconnected by another level of interconnect. There is a hierarchy in the organization of these FPGAs: ① these FPGAs contain clusters of logic blocks with localized resources for interconnection. The global interconnect network is used for the interconnections between the clusters of logic blocks.

-**Sea-of-gate architecture:** The general FPGA fabric(结构) consists of a large number of gates. There is an interconnect superimposed on the sea of gates.

-**reconfigurability:** can be achieved by: ① changing the contents of static RAM cells; ② changing the contents of flash memory cells; ③ fusing metal links. FPGAs use one of the following programming methods: ① StaticRAM programming technology; (Key idea is to use pass transistors to create switches and then control them using SRAM content) ② EPROM/ EEPROM/ flash programming technology;

③AntiFuse programming technology (irreversible, but faster) Only SRAM and EEPROM/Flash programming technologies allow in-circuit programmability 在线可重构编程

-**Routing Matrix for General-Purpose Interconnection in an FPGA:** Many FPGAs use switch matrices that provide interconnections between routing wires connected to the switch matrix. Each cross point in the switch matrix must support six possible interconnections.

-**Direct Interconnects between Neighboring Logic Blocks:** Many FPGAs provide direct interconnections to the four nearest neighbors(有时是 8 邻居). 直接互连不通过开关矩阵, 而是通过专用 dedicated switches 开, 延迟小。

-**Global Lines:** For purposes such as high fan-out and low-skew clock distribution, most FPGAs provide routing lines that span the entire width/height of device. A limited number (two or four) of such global lines are provided by many FPGAs in the horizontal and vertical directions.

-**Typical Routing Resources in a Row-Based FPGA:** The interconnects in row-based channeled architecture can be classified into two categories: non-segmented routing, segmented routing


-**I/O Block:** I/O blocks on modern FPGAs allow use of the pin as input and/or output, in direct (combinational) or latched forms, in tristate true or inverted forms, and with a variety of I/O standards. To use the cell as an output, the tristate buffer must be enabled. To use the cell as an input, the tristate control must be set to place the tristate buffer, which drives the output pin, in the high-impedance state.


**CH4**  
-**Design:** Design methodology splits a design into a "data path" and a "controller". ① Controller: sends control signals or commands to data path and obtain feedback(status signals) from data path. ② Data path: hardware that actually performs the data processing.


-**CLA:** 先行进位加法器 Carry look-ahead adders. Ci+1 = AiBi + (Ai ⊕ Bi)Ci = Gi + Pi, Gi = AiBi, Pi = Ai ⊕ Bi. Gi = indicates whether a stage should generate a carry. Pi = indicates whether an adder should propagate the carry it receives from the lower stage. 优点: delays will be the same independent of the number of bits we need to add. 缺点: 4bit 以上逻辑复杂 CLA adders are usually implemented as 4-bit modules and are used in a hierarchical structure to realize 4-bit adders.


-**State Graphs for Control Circuits:** If an arc is labeled with XiXj/ZpZq, it means ① If inputs Xi and Xj are 1 (we don't care what the other inputs are), ② outputs Zp and Zq are 1 (and the other outputs are 0) ③ and we traverse this arc to the next state. In general, if we label an arc with an input expression, I, we will traverse the arc when I=1. Constraints on the input labels: ① If i and j are any pair of input labels on arcs exiting state Sk, then IiIj = 0 ② if i≠j If n arcs exit state Sk and the n arcs have input labels I1, I2, ..., In, respectively, then I1I2+...+InI1 = 1

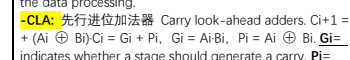
-**Score Board:** 2 位 BCD 数字 inc/dec 信号, 数码管显示, 复位信号超过 5 个 cycle 清零



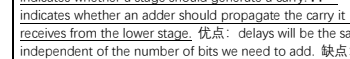

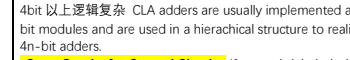-**Binary Dividers**  
Unsigned:  

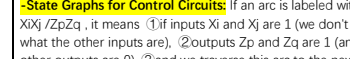
Signed:  

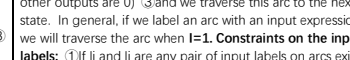


-**Synchronization and Debouncing:** 去抖动:remove the transients in the switch output. Three flip-flops can provide debouncing, synchronization, and single pulsing.

-**Add-and-Shift Multiplier:** Multiplicand=被乘数 A. Multiplier=乘数 B, A\*B=C, 串并乘法器: Multiplier bits are processed serially, at the addend takes place in parallel.


-**Array Multiplier:** Array of AND gates and adders to perform multiplication. This multiplier has no sequential logic or registers. 全加器 3 输入, 半加器 2 输入. Carry must propagate along each row of cells. Sum must propagate from row to row. n-bit-by-n-bit array multiplier requires: n^2 与门, (n-1)n 加法器. Array multiplier: number of components required increases quadratically: Serial-parallel multiplier: the amount of hardware required in addition to the control circuit increases linearly with n. worst-case multiply time: (3n-4)td+tg, tag=加法器延迟, tg=与门延迟

-**Signed number representations:** 有符号的 4-bit 二进制数: +8 没有原反补码; -8 没有原反补码, 补码为 1000; -0 原反补码皆为 0000; -0 原码 1000, 反码 1111, 补码 0000; 反码 One's complement: 正数反码等于原码, 负数的反码等于相反数的

反码取反; 补码 Two's complement: 正数补码等于原码, 负数补码等于求出反码之后+1(+0 例外)。  
-**Fraction:** The leftmost bit represents the sign of the fraction (sign bit). A signed binary fraction x0 x-1x-2x-3 represents the quantity x0 (-2^0) + x-1 (2^-1) + x-2 (2^-2) + x-3 (2^-3)

Example:  
(0.101)two=0\*(-2^0)+1\*(2^-1)+0\*(2^-2)+1\*(2^-3)=5/8;  
(1.011)two=1\*(-2^0)+0\*(2^-1)+1\*(2^-2)+1\*(2^-3)=-5/8  
从右边开始找到第一个 1, 对他左边的取反, 比如:  
(0.111)two=(5/8)dec, (1.011)two=(-5/8)dec

0.111... is the largest positive fraction 无法用补码表达 1.  
特例: (1.000)two=(-1)dec (0.111)two=(7/8)dec

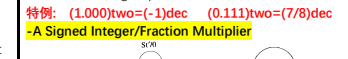-**A Signed Integer/Fraction Multiplier**  




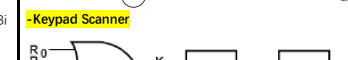
















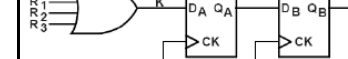

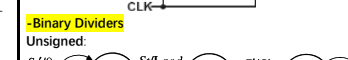

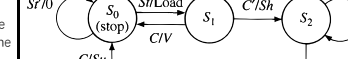

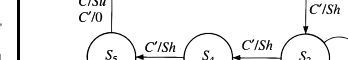
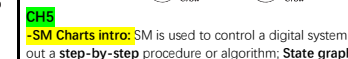

















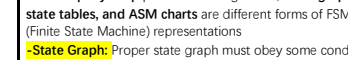


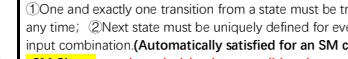


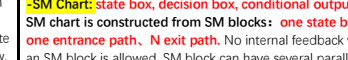

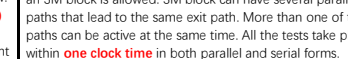

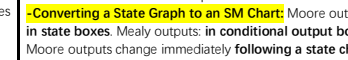


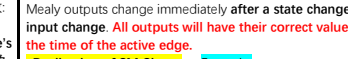


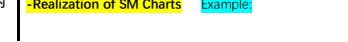






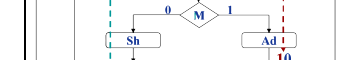

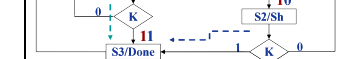








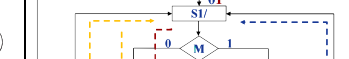





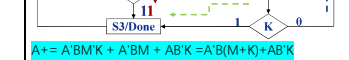


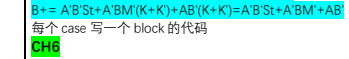


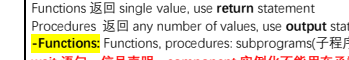

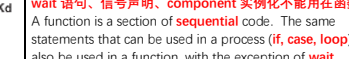

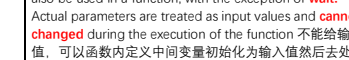


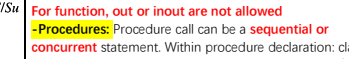


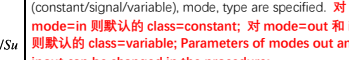








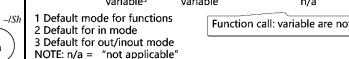


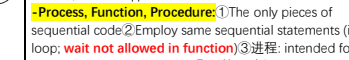


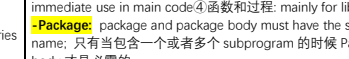


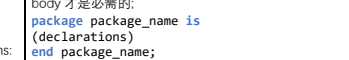


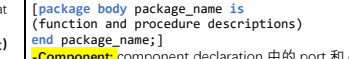


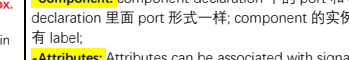

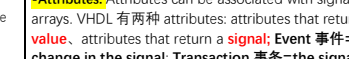

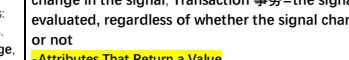

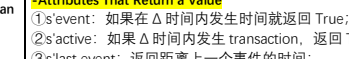

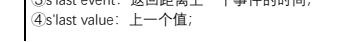

last active: 返回距离上一个 transaction 的时间; b.  
返回信号:  
-Attributes That Create a Signal ([Time])可选项 1 个 Δ  
(1's delayed([time]): 返回延时了 time 的信号 s, time 可  
选;  
(2's stable([time]): 返回 Boolean 信号, 如果指定时间  
(preceding)内 s 没有发生值, 信号值为 true;  
(3's quiet([time]): 返回 Boolean 信号, 如果指定时间  
(preceding)内 s 没有发生 transaction, 信号值为 true(初  
始值为 false);  
(4's transaction: bit signal, s 发生 transaction 时, 该信  
号发生翻转(初始值 1);  
-Array Attributes:  
A can either be an array name or an array type

#### -4-Valued Logic System:

Symbols	represents ...	Examples
'X'	Unknown	> The initial values of a signal is unknown > A signal is simultaneously driven to two conflicting values
'0'	0	
'1'	1	
'Z'	High impedance	Tristate buffers and buses

-Signal Resolution Functions: necessary when different wires  
in a system are driving a common signal path; VHDL with  
multivalued logic can be used to create resolutions when  
signals are connected. Resolved signals have an associated  
resolution function; With unresolved signals, if we drive a bit  
signal to two different values in two concurrent statements, the  
compiler will flag an error.

#### -IEEE 9-Valued Logic System:


(1)'U': 未初始化; (2)'0': 强 0; (3)'1': 强 1;  
(4)'X': 强未知; (5)'Z': 高阻态; (6)'W': 弱未知;  
(7)'L': 弱 0; (8)'H': 弱 1; (9)'.': 无所谓;  
大多数只限于仿真, '0', '1' 和 'Z' 可综合, 无限制。  
区别: (1)'1': as perfect as the power supply voltage; (2)'H':  
logically high, but has a voltage drop; (3)'0': perfect  
grounding; (4)'L': logically low; If a forcing signal and a weak  
signal are tied together, the forcing signal dominates.

U	U	X	0	1	Z	W	L	H	.
U	U	U	U	U	U	U	U	U	U
X	U	X	X	X	X	X	X	X	X
0	U	X	0	X	0	0	0	0	X
1	U	X	X	1	1	1	1	1	X
Z	U	X	0	1	Z	W	L	H	X
W	U	X	0	1	W	W	W	W	X
L	U	X	0	1	L	W	L	W	X
H	U	X	0	1	H	W	W	H	X
.	U	X	X	X	X	X	X	X	X

std\_logic is a subtype of std\_ulogic  
IEEE.numeric\_std package uses std\_logic
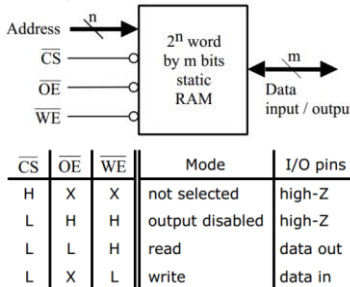
#### -SRAM Model

n address lines, m data lines. 3 control lines: CS, b, OE, WE, b  
This memory can store 2<sup>n</sup> words, each m bits wide




CS	OE	WE	Mode	I/O pins
H	X	X	not selected	high-Z
L	H	H	output disabled	high-Z
L	L	H	read	data out
L	X	L	write	data in

CS, b: chip select selects memory chip so that memory read  
and write operation are possible; OE, b: output enables  
memory output onto an external bus; WE, b: write enable data  
to be written to RAM; Writing to the latches in the memory  
cells is not completed until: (1)WE, b goes high (2)CS, b goes  
high.  
-Generics: generics is a way of specifying a generic  
parameter; Generic parameter is a static parameter; It can be  
easily modified and adapted to different applications  
generic (n : integer := 8); Whenever n is found in the  
entity itself or in the architecture that follows, its value will be  
assumed to be 8  
-Named association: 按位置或者显式地指定  
-Generate Statements:  
for 生成语句: 编译的时候会按照规则生成一系列语句


generate\_label: for identifier in range generate\_label;  
begin  
concurrent statement(s)  
end generate\_label;  
-Conditional Generate: 条件为真的时候生成, 不允许 else  
generate\_label: if condition generate\_label;  
begin  
concurrent statement(s)  
end generate\_label;

#### -Sequence Detector: 检测 101

 
 
#### -NRZ to Manchester

Manchester code: 0=前半 0 后半 1, 1=前半 1 后半 0



#### (b) State Graph (c) State table

-BCD to Seven-Segment Display Decoder  
entity bcd\_seven is  
port(bcd: in bit\_vector(3 downto 0); seven: out bit\_vector(7 downto 1));  
end bcd\_seven;

architecture behavior of bcd\_seven is  
begin  
process(bcd)  
begin  
case bcd is  
when "0000" => seven <= "0111111";  
when "0001" => seven <= "0000110";  
when "0010" => seven <= "1011011";  
when "0011" => seven <= "1011011";  
when "0100" => seven <= "1100111";  
when "0101" => seven <= "1101101";  
when "0110" => seven <= "1111011";  
when "0111" => seven <= "0000111";  
when "1000" => seven <= "1111111";  
when "1001" => seven <= "1101111";  
when others => null;  
end case;  
end process;  
end behavior;

#### -A BCD Adder

library IEEE;  
use IEEE.numeric\_bit.all;

entity BCD\_Adder is  
port(X, Y: in unsigned(7 downto 0); Z: out unsigned(11 downto 0));  
end BCD\_Adder;

architecture BCDadd of BCD\_Adder is  
alias Xdigi1: unsigned(3 downto 0) is X(7 downto 4);  
alias Xdigi0: unsigned(3 downto 0) is X(3 downto 0);  
alias Ydigi1: unsigned(3 downto 0) is Y(7 downto 4);  
alias Ydigi0: unsigned(3 downto 0) is Y(3 downto 0);  
alias Zdigi2: unsigned(3 downto 0) is Z(11 downto 8);  
alias Zdigi1: unsigned(3 downto 0) is Z(7 downto 4);  
alias Zdigi0: unsigned(3 downto 0) is Z(3 downto 0);  
signal S0, S1: unsigned(4 downto 0);  
signal C: bit;  
begin  
S0 <= '0' & Xdigi0 + Ydigi0;  
Zdigi0 <= S0(3 downto 0) + 6 when S0 > 9  
else S0(3 downto 0); -- add 6 if needed  
C <= '1' when S0 > 9 else '0';  
S1 <= '0' & Xdigi1 + Ydigi1 + unsigned('0' > C);  
Zdigi1 <= S1(3 downto 0) + 6 when S1 > 9  
else S1(3 downto 0);  
Zdigi2 <= "0001" when S1 > 9 else "0000";  
end BCDadd;

#### -Keyboard Scanner

S1: wait with output C0=C1=C2=1 until a key is pressed  
S2: C0=1, so if the pressed key is in column 0, K = 1, and  
the circuit output V=1 and goes to S5  
S3: S4: If no key is found in column 0, column 1 is checked,  
and if necessary, column 2 is checked  
S5: The circuit waits until all keys are released and Kd goes to 0  
before resetting

entity scanner is  
port(R0, R1, R2, R3, CLK: in bit; C0, C1, C2: inout bit;  
N0, N1, N2, N3, V: out bit);  
end scanner;  
architecture behavior of scanner is  
signal QA, K, Kd: bit;  
signal state, nextstate: integer range 0 to 5;  
begin  
K <= R0 or R1 or R2 or R3;  
N3 <= (R2 and not C0) or (R3 and not C1);  
N2 <= R1 or (R2 and C0);  
N1 <= (R0 and not C0) or (not R2 and C2) or (not R1 and not R0 and  
C0);  
N0 <= (R1 and C1) or (not R1 and C2) or (not R3 and not R1 and not  
C1);

process(state, R0, R1, R2, R3, C0, C1, C2, K, Kd, QA)  
begin  
C0 <= '0'; C1 <= '0'; C2 <= '0'; V <= '0';  
case state is  
when 0 => nextstate <= 1;  
when 1 => C0 <= '1'; C1 <= '1'; C2 <= '1';  
if (Kd and K) => '1' then nextstate <= 2;  
else nextstate <= 1;  
end if;  
when 2 => C0 <= '1';  
if (Kd and K) => '1' then V <= '1'; nextstate <= 5;  
else K <= '0' then nextstate <= 4;  
else nextstate <= 3;  
end if;  
when 3 => C1 <= '1';  
if (Kd and K) => '1' then V <= '1'; nextstate <= 5;  
else K <= '0' then nextstate <= 4;  
else nextstate <= 3;  
end if;  
when 4 => C2 <= '1';  
if (Kd and K) => '1' then V <= '1'; nextstate <= 5;  
else nextstate <= 4;  
end if;  
when 5 => C0 <= '1'; C1 <= '1'; C2 <= '1';  
if Kd <= '0' then nextstate <= 1;  
else nextstate <= 5;  
end if;  
end case;  
end process;  
process(CLK)  
begin  
if CLK <= '1' and CLK'event then  
state <= nextstate;  
QA <= K;  
Kd <= QA;  
end if;  
end process;  
end behavior;

#### -UART

When no data is being transmitted, D remains high.  
library IEEE; use IEEE.std\_logic\_1164.all;  
use IEEE.numeric\_std.all; -- use this if unsigned type is used.  
entity UART\_Transmitter is port(Bclk, sysclk\_rst\_b, TDRE, loadTDR: in std\_logic;  
DBus: in unsigned(7 downto 0);  
setTDRE, TxOut: out std\_logic);  
end UART\_Transmitter;

architecture xmit of UART\_Transmitter is  
type stateType is (IDLE, SYNCH, TDATA);  
signal state: stateType;  
signal TSR: unsigned(8 downto 0); -- Shift Register  
signal Bct: integer range 0 to 9;  
signal inc, clr, loadTSR, shiftTSR: std\_logic;  
signal Bclk\_rising, Bclk\_Delayed: std\_logic;

begin  
TxD <= TSV(0);  
setTDR <= loadTSR;  
Bclk\_rising <= Bclk and (not Bclk\_Delayed); -- indicates the rising edge of bit  
clock  
Xmit\_Control: process(state, TDRE, Bct, Bclk\_rising)  
Begin  
inc <= '0'; clr <= '0'; loadTSR <= '0'; shiftTSR <= '0'; start <= '0'; -- reset  
case state is  
when IDLE =>  
if (TDRE = '0') then  
loadTSR <= '1'; nextstate <= SYNCH;  
else nextstate <= IDLE; end if;  
when SYNCH => -- synchronize with the bit clock  
if (Bclk\_rising = '1') then  
start <= '1'; nextstate <= TDATA;  
else nextstate <= SYNCH; end if;  
when TDATA =>  
if (Bclk\_rising = '0') then nextstate <= TDATA;  
else if (Bct = 9) then  
shiftTSR <= '1'; inc <= '1'; nextstate <= TDATA;  
else clr <= '1'; nextstate <= IDLE; end if;  
end case; end process;  
Xmit\_update: process(sysclk\_rst\_b)  
Begin  
if (rst\_b = '0') then  
TSR <= "111111111";  
state <= IDLE; Bct <= 0; Bclk\_Delayed <= '0';  
else if (sysclk'event and sysclk = '1') then  
state <= nextstate;  
if (clr = '1') then Bct <= 0;  
else if (inc = '1') then Bct <= Bct + 1; end if;  
if (loadTSR = '1') then TSR <= DBus; end if;  
if (loadTSR = '1') then TSR <= DBus; end if;  
if (start = '1') then TSR(0) <= '0'; end if;  
if (shiftTSR = '1') then TSR <= TSR < 1 & TSR(8 downto 1);  
end if; -- shift out one bit  
Bclk\_Delayed <= Bclk; -- Bclk delayed by 1 sysclk  
end if; end process; end xmit;



#### entity UART\_Receiver is

port(RxD, BclkX8, sysclk\_rst\_b, RDRF: in std\_logic;  
RDR: out unsigned(7 downto 0);  
setRDRF, OE: out std\_logic);  
end UART\_Receiver;
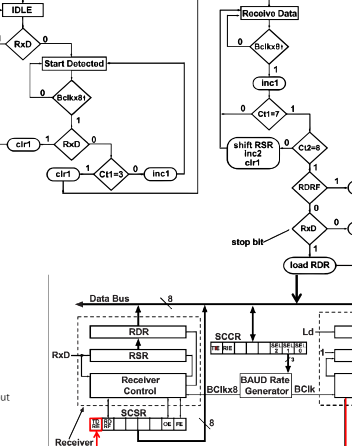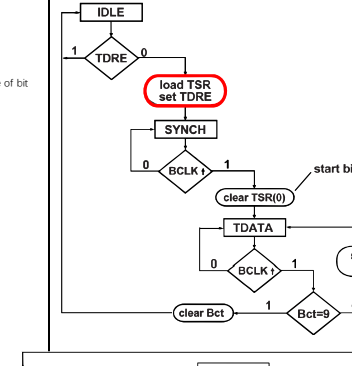
#### architecture rxv of UART\_Receiver is

type stateType is (IDLE, START\_DETECTED, RECVD\_DATA);  
signal state: stateType;  
signal RSR: unsigned(7 downto 0); -- receive shift register  
signal c2: integer range 0 to 7; -- indicates when to read the RDR input  
signal c2: integer range 0 to 8; -- counts number of bits read  
signal inc1, c2, c2r2, shiftRSR, loadRDR: std\_logic;  
signal BclkX8\_Delayed, BclkX8\_rising: std\_logic;

begin  
BclkX8\_rising <= BclkX8 and (not BclkX8\_Delayed); -- indicates the rising edge  
of bitX8 clock  
Rxv\_Control: process(state, RxD, RDRF, c1, c2, BclkX8\_rising)  
begin  
-- reset control signals  
inc1 <= '0'; c2 <= '0'; c2r2 <= '0';  
if (Kd and K) => '1' then nextstate <= 2;  
else nextstate <= 1;  
end if;  
when 2 => C0 <= '1';  
if (Kd and K) => '1' then V <= '1'; nextstate <= 5;  
else K <= '0' then nextstate <= 4;  
else nextstate <= 3;  
end if;  
when 3 => C1 <= '1';  
if (Kd and K) => '1' then V <= '1'; nextstate <= 5;  
else K <= '0' then nextstate <= 4;  
else nextstate <= 3;  
end if;  
when 4 => C2 <= '1';  
if (Kd and K) => '1' then V <= '1'; nextstate <= 5;  
else nextstate <= 4;  
end if;  
when 5 => C0 <= '1'; C1 <= '1'; C2 <= '1';  
if Kd <= '0' then nextstate <= 1;  
else nextstate <= 5;  
end if;  
end case;  
end process;  
process(CLK)  
begin  
if CLK <= '1' and CLK'event then  
state <= nextstate;  
QA <= K;  
Kd <= QA;  
end if;  
end process;  
end behavior;



#### -Dice Game

entity DiceGame is  
port (Rb, Reset, CLKG: in bit;  
Sum: in integer range 2 to 12;  
Roll, Win, Lose: out bit);  
end DiceGame;

architecture DiceBehave of DiceGame is  
signal State: integer range 0 to 5;  
signal Sp: bit;  
begin  
process (Rb, Reset, Sum, State)  
begin  
Sp <= '0'; Roll <= '0'; Win <= '0'; Lose <= '0';  
case State is  
when 0 =>  
if Rb = '1' then Nextstate <= 1;  
end if;  
when 1 =>  
if Rb = '1' then Roll <= '1';  
else Sum = 7 or Sum = 11 then Nextstate <= 2;  
else Sum = 2 or Sum = 3 or Sum = 12 then Nextstate <= 3;  
else Sp <= '1'; Nextstate <= 4;  
end if;  
when 2 => Win <= '1';  
if Reset = '1' then Nextstate <= 0; end if;  
when 3 => Lose <= '1';  
if Reset = '1' then Nextstate <= 0; end if;  
when 4 => if Rb = '1' then Nextstate <= 5; end if;  
when 5 =>  
if Rb = '1' then Roll <= '1';  
else Sum = Point then Nextstate <= 2;  
else Sum = 7 then Nextstate <= 3;  
else Nextstate <= 4;  
end if;  
end case;  
end process;  
end DiceBehave;

process (CLK)  
begin  
if rising\_edge (CLK) then  
State <= Nextstate;  
if Sp = '1' then Point <= Sum;  
end if;  
end if;  
end process;

#### -Divider

library IEEE;  
use IEEE.numeric\_bit.all;  
entity sdv is  
port(CLK, St: in bit; Dbus: in unsigned(15 downto 0);  
Quotient: out unsigned(15 downto 0);  
Rdy: out bit);  
end sdv;

architecture Sdivdv of sdv is  
signal State: integer range 0 to 6;  
signal Count: unsigned(3 downto 0);  
signal Sign, C, Cm2: bit;  
signal Divisor, Sum, Compout: unsigned(15 downto 0);  
signal Dividend: unsigned(31 downto 0);  
alias Acc: unsigned(15 downto 0) is Dividend(31  
downto 16);  
begin  
Cm2 <= not divisor(15);  
compout <= divisor when Cm2 = '0' else not divisor;  
Sum <= Acc + compout + unsigned('0' > Cm2);  
C <= not Sum(15);  
Quotient <= Dividend(15 downto 0);  
Rdy <= '1' when State = 0 else '0';  
process (CLK)  
begin  
if CLK'event and CLK = '1' then  
case State is  
when 0 =>  
if St = '1' then  
Acc <= Dbus; -- load upper dividend  
Sign <= Dbus(15);  
State <= 1;  
V <= '0'; -- initialize overflow  
Count <= 0000; -- initialize counter  
end if;  
when 1 => Dividend(15 downto 0) <= Dbus; -- load lower dividend  
State <= 2;  
when 2 =>  
Divisor <= Dbus;  
if Sign = '1' then -- two's complement Dividend if necessary  
Dividend <= not Dividend + 1;  
end if;  
State <= 3;  
when 3 =>  
Dividend <= Dividend(30 downto 0) & '0'; -- left shift  
Count <= Count + 1;  
State <= 4;  
when 4 => if C = '1' then  
V <= '1';  
State <= 0;  
else  
Dividend <= Dividend(30 downto 0) & '0';  
Count <= Count + 1;  
State <= 5;  
end if;  
when 5 => if c = '1' then  
Acc <= Sum; -- subtract  
Dividend(0) <= '1';  
else  
Dividend <= Dividend(30 downto 0) & '0'; -- left shift

if Count = 15 then State <= 6; end if; -- KC  
Count <= Count + 1;

end if;  
when 6 => State <= 0;  
if C = '1' then  
Acc <= Sum; -- subtract  
Dividend(0) <= '1';  
State <= 6;  
else if (Sign xor Divisor(15)) = '1' then  
Dividend <= not Dividend + 1;  
end if;  
end case;  
end if;  
end process;  
end Sdivdv;

In the following VHDL process A, B, C, and D are all integers that have a value  
of 0 at time = 10 ns. If E changes from '0' to '1' at time = 20 ns, specify the  
time(s) at which each signal will change and the value to which it will change.  
List these changes in chronological order (20, 20+Δ, 20+2Δ, etc.).

Time	A	B	C	D	E
10 ns	0	0	0	0	0
20 ns	0	0	0	0	1
20 + Δns	0	1	0	0	1
20 + 2Δns	0	8	0	0	1
23 ns	0	8	0	0	1
30 ns	0	8	1	0	1
35 ns	5	8	1	0	1

Packages	Type defined	Conversion functions	Logic operations	Arithmetic operations
----------	--------------	----------------------	------------------	-----------------------

std_logic_1161	std_logic std_logic_vector		✓	x
numeric_bit	(un)signed (using bit_vector)	to_integer(A) to_unsigned(B,N) unsigned(A) bit_vector(B)	✓	✓
numeric_std	(un)signed (using std_logic_vector)		✓	✓
std_logic_unsigned			x	✓

Type ROM is array (0 to 15, 7 downto 0) of bit;  
Signal ROM1 : ROM;

Attribute	Returns	Examples
A'LEFT(N)	left bound of Nth index range	ROM1'LEFT(1)=0 ROM1'RIGHT(2)=7
A'RIGHT(N)	right bound of Nth index range	ROM1'RIGHT(1)=15 ROM1'RIGHT(2)=0
A'HIGH(N)	largest bound of Nth index range	ROM1'HIGH(1)=15 ROM1'HIGH(2)=7
A'LOW(N)	smallest bound of Nth index range	ROM1'LOW(1)=0 ROM1'LOW(2)=0
A'RANGE(N)	Nth index range	ROM1'RANGE(1)=0 to 15 ROM1'RANGE(2)=7 downto 0
A'REVERSE_RANGE(N)	reversed Nth index range	ROM1'REVERSE_RANGE(1)=15 downto 0 ROM1'REVERSE_RANGE(2)=0 to 7
A'LENGTH(N)	size of Nth index range	ROM1'LENGTH(1)=16 ROM1'LENGTH(2)=8

