



Chapter 4.11-12

Design Examples


Version: 2023/12/12

Chapter 4 Design Examples

	Contents
1	BCD to Seven-Segment Display Decoder
2	A BCD Adder
3	32-Bit Adders
4	Traffic Light Controller
5	State Graphs for Control Circuits
6	Scoreboard and Controller
7	Synchronization and Debouncing
8	Add-and-Shift Multiplier
9	Array Multiplier
10	A Signed Integer/Fraction Multiplier
11	Keypad Scanner
12	Binary Dividers

11 Keypad Scanner

Keypad with Three Columns and Four Rows

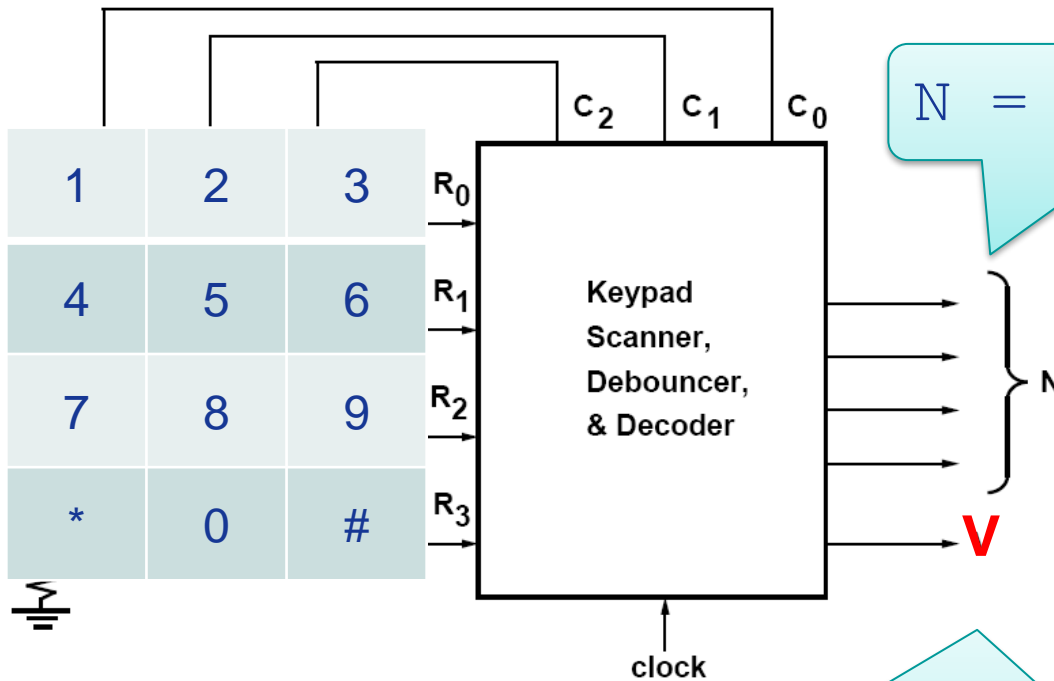

$$N = N_3N_2N_1N_0$$

Examples:


5 : 0101

* : 1010


: 1011

When a valid key has been detected, SCANNER outputs **V** for one clock time

11 Keypad Scanner

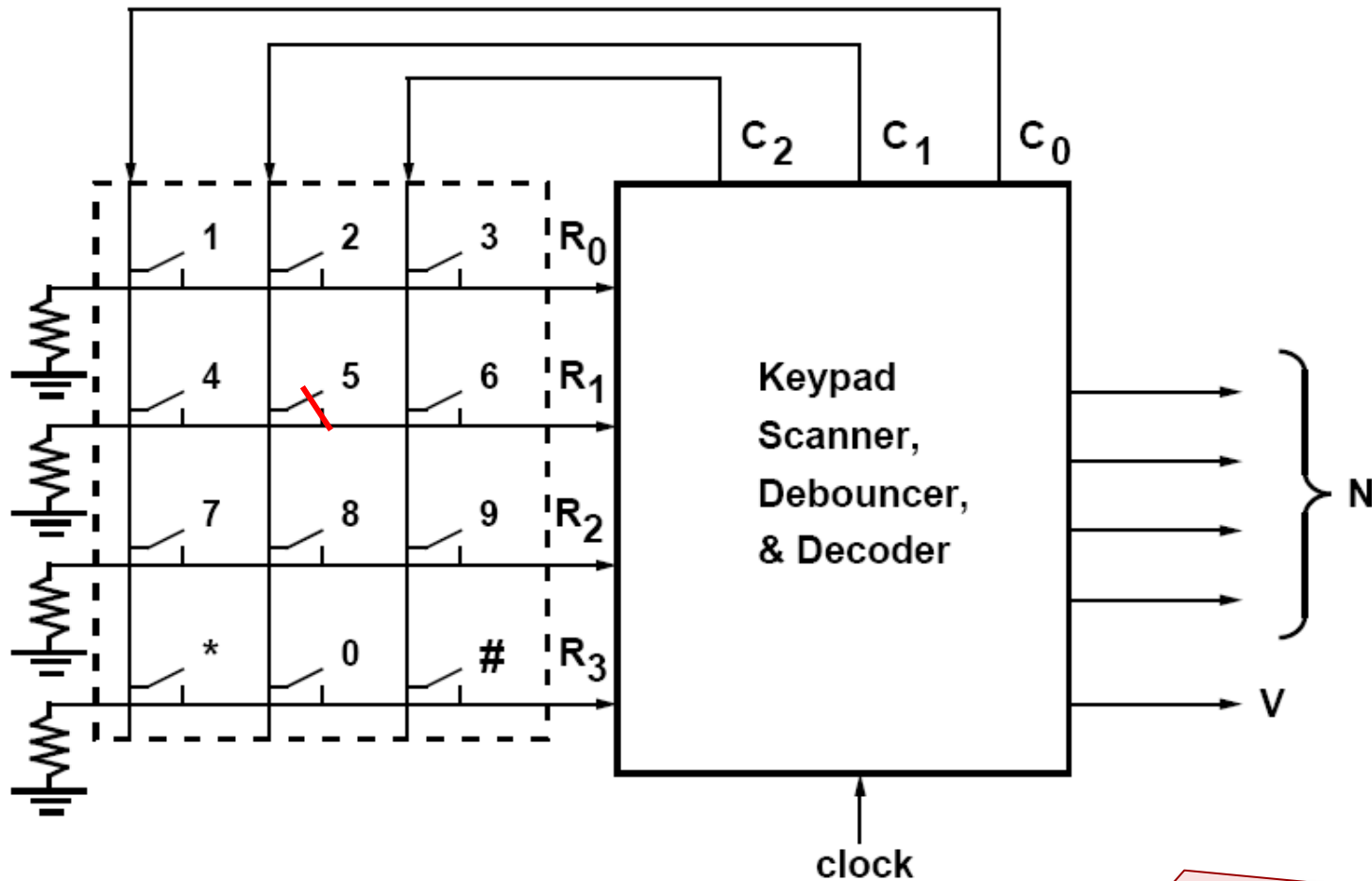


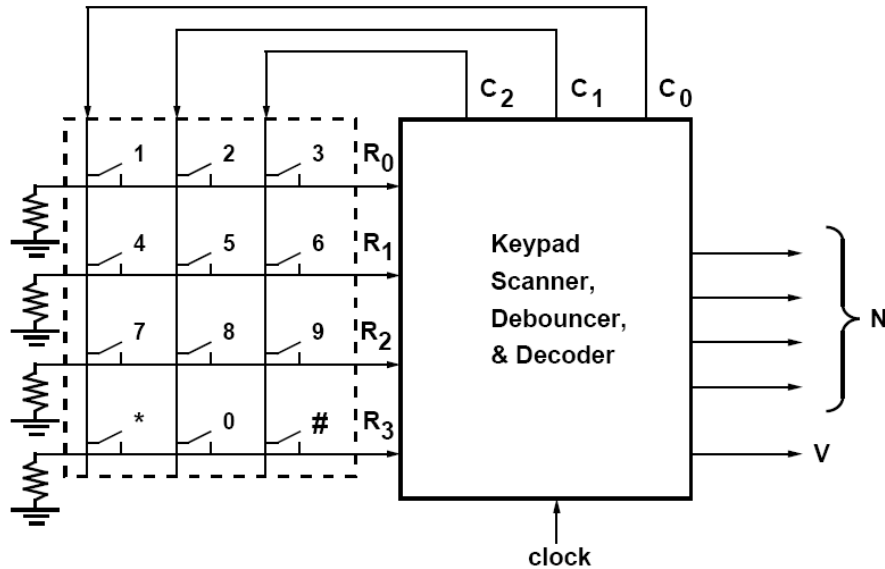Assumption: only one key is pressed at a time





Scanner modules

K : key press
Kd : debounded key press

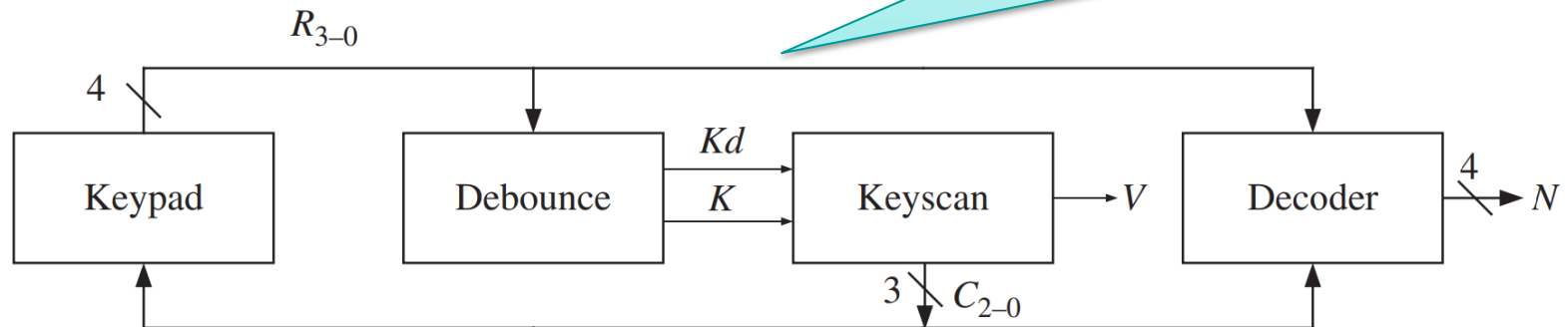



4.11.1 Scanner

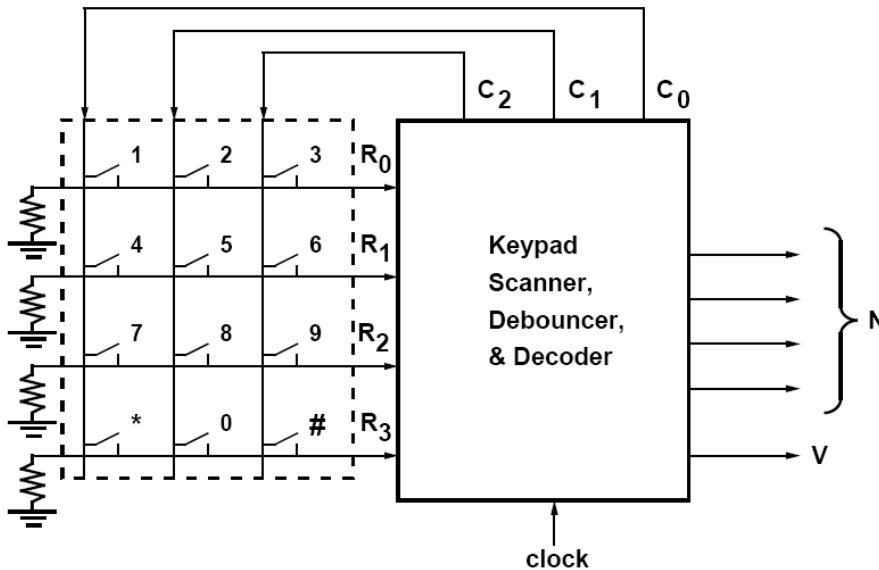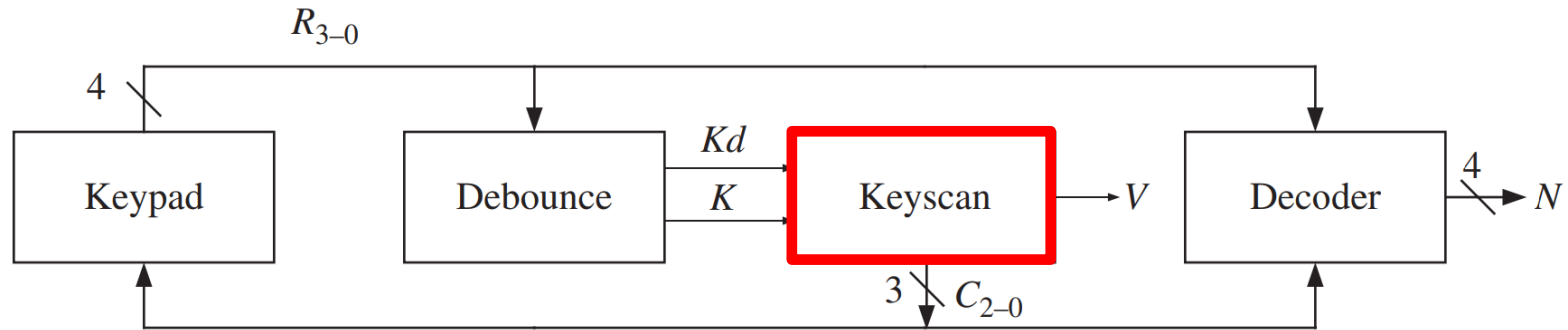

Step 1: Apply logic 1's to C_0 , C_1 , C_2 and wait

Step 2: If any key is pressed, apply a 1 to $C_0 \rightarrow C_1 \rightarrow C_2$


4.11.1 Scanner

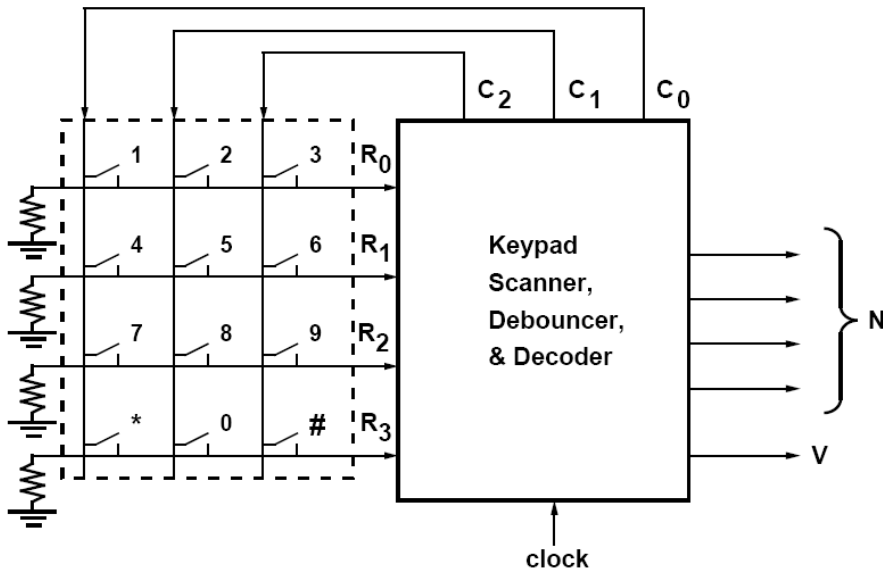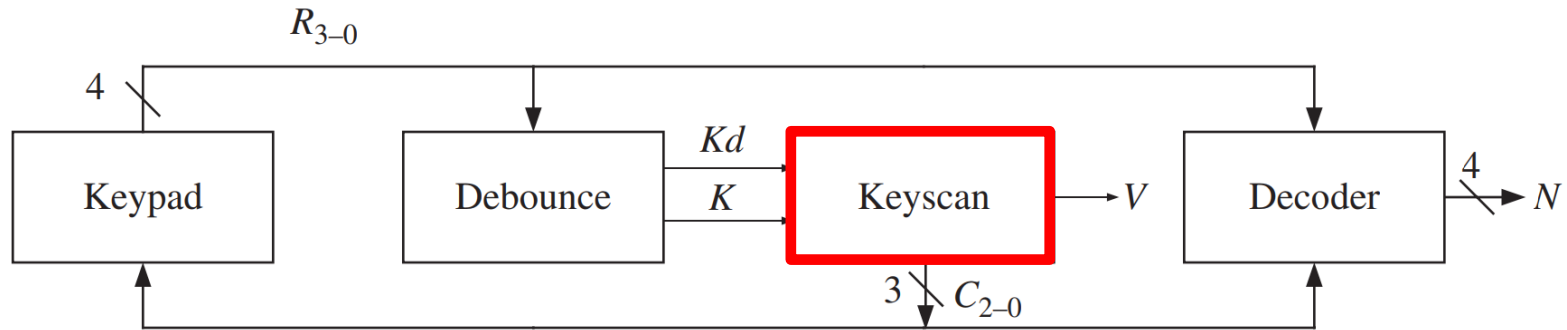


Step 3: If R_i is detected, set $V = 1$

Step 4: Apply 1's to C_0 , C_1 , C_2 and wait until no key is pressed

4.11.2 Debouncer

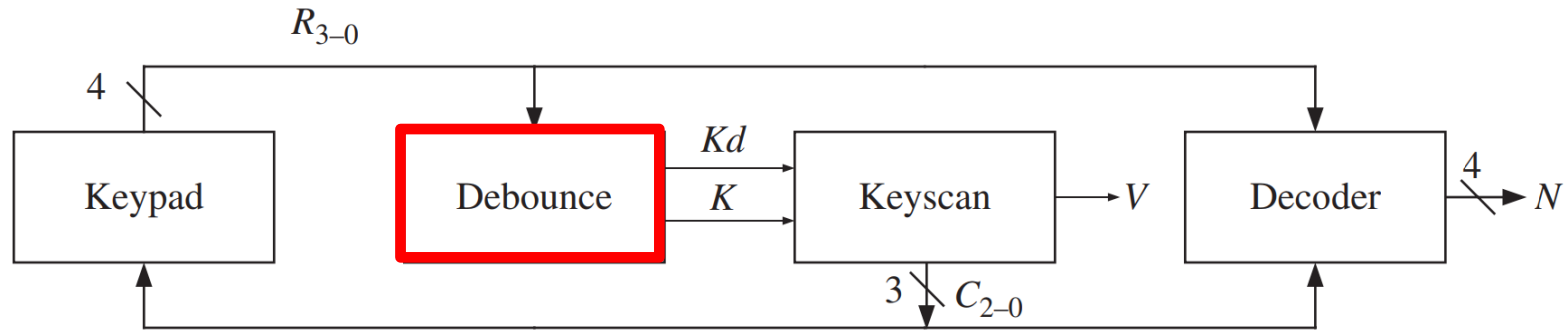


Debouncing and Synchronizing Circuit

 

- Kd is fed to sequential circuit


- $R_0 \sim 3$ are connected to an OR gate to form K
- K turns on when a key is pressed and a column signal is applied

4.11.3 Decoder

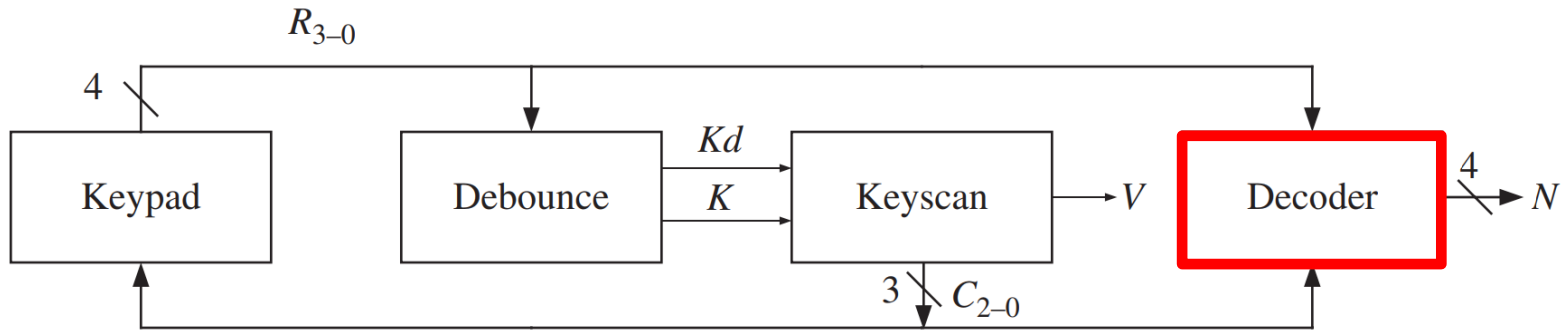

- Decoder is combinational circuit, its output will change as the keypad is scanned
- At the a valid key is detected ($K=1$ and $V=1$), decoder will have the correct output and this value can be saved in a register

4.11.3 Decoder

 

Truth Table for Decoder

$R_3 R_2 R_1 R_0 C_0 C_1 C_2$	N_3	N_2	N_1	N_0
0 0 0 1 1 0 0	0	0	0	1
0 0 0 1 0 1 0	0	0	1	0
0 0 0 1 0 0 1	0	0	1	1
0 0 1 0 1 0 0	0	1	0	0
0 0 1 0 0 1 0	0	1	0	1
0 0 1 0 0 0 1	0	1	1	0
0 1 0 0 1 0 0	0	1	1	1
0 1 0 0 0 1 0	1	0	0	0
0 1 0 0 0 0 1	1	0	0	1
1 0 0 0 1 0 0	1	0	1	0 (*)
1 0 0 0 0 1 0	0	0	0	0
1 0 0 0 0 0 1	1	0	1	1 (#)

Logic Equations for Decoder

$N_3 =$
 $N_2 =$
 $N_1 =$
 $N_0 =$



4.11.3 Decoder

R ₃ R ₂ R ₁ R ₀ C ₀ C ₁ C ₂	N ₃	N ₂	N ₁	N ₀
0 0 0 1 1 0 0	0	0	0	1
0 0 0 1 0 1 0	0	0	1	0
0 0 0 1 0 0 1	0	0	1	1
0 0 1 0 1 0 0	0	1	0	0
0 0 1 0 0 1 0	0	1	0	1
0 0 1 0 0 0 1	0	1	1	0
0 1 0 0 1 0 0	0	1	1	1
0 1 0 0 0 1 0	1	0	0	0
0 1 0 0 0 0 1	1	0	0	1
1 0 0 0 1 0 0	1	0	1	0 (*)
1 0 0 0 0 1 0	0	0	0	0
1 0 0 0 0 0 1	1	0	1	1 (#)

\R ₃ R ₂ R ₁ R ₀ \	00	01	11	10
00	X		X	
01		X	X	X
11	X	X	X	X
10		X	X	X

4.11.3 Decoder

R ₃ R ₂ R ₁ R ₀ C ₀ C ₁ C ₂	N ₃	N ₂	N ₁	N ₀
0 0 0 1 1 0 0	0	0	0	1
0 0 0 1 0 1 0	0	0	1	0
0 0 0 1 0 0 1	0	0	1	1
0 0 1 0 1 0 0	0	1	0	0
0 0 1 0 0 1 0	0	1	0	1
0 0 1 0 0 0 1	0	1	1	0
0 1 0 0 1 0 0	0	1	1	1
0 1 0 0 0 1 0	1	0	0	0
0 1 0 0 0 0 1	1	0	0	1
1 0 0 0 1 0 0	1	0	1	0 (*)
1 0 0 0 0 1 0	0	0	0	0
1 0 0 0 0 0 1	1	0	1	1 (#)

\R ₃ R ₂ R ₁ R ₀ \	00	01	11	10
00	X		X	
01		X	X	X
11	X	X	X	X
10		X	X	X

4.11.3 Decoder

R ₃ R ₂ R ₁ R ₀ C ₀ C ₁ C ₂	N ₃	N ₂	N ₁	N ₀
0 0 0 1 1 0 0	0	0	0	1
0 0 0 1 0 1 0	0	0	1	0
0 0 0 1 0 0 1	0	0	1	1
0 0 1 0 1 0 0	0	1	0	0
0 0 1 0 0 1 0	0	1	0	1
0 0 1 0 0 0 1	0	1	1	0
0 1 0 0 1 0 0	0	1	1	1
0 1 0 0 0 1 0	1	0	0	0
0 1 0 0 0 0 1	1	0	0	1
1 0 0 0 1 0 0	1	0	1	0 (*)
1 0 0 0 0 1 0	0	0	0	0
1 0 0 0 0 0 1	1	0	1	1 (#)

\R ₃ R ₂ R ₁ R ₀ \	00	01	11	10
00	X	C0'	X	C1'
01	0	X	X	X
11	X	X	X	X
10	0	X	X	X

4.11.3 Decoder

R ₃ R ₂ R ₁ R ₀ C ₀ C ₁ C ₂	N ₃	N ₂	N ₁	N ₀
0 0 0 1 1 0 0	0	0	0	1
0 0 0 1 0 1 0	0	0	1	0
0 0 0 1 0 0 1	0	0	1	1
0 0 1 0 1 0 0	0	1	0	0
0 0 1 0 0 1 0	0	1	0	1
0 0 1 0 0 0 1	0	1	1	0
0 1 0 0 1 0 0	0	1	1	1
0 1 0 0 0 1 0	1	0	0	0
0 1 0 0 0 0 1	1	0	0	1
1 0 0 0 1 0 0	1	0	1	0 (*)
1 0 0 0 0 1 0	0	0	0	0
1 0 0 0 0 0 1	1	0	1	1 (#)

\R ₃ R ₂ R ₁ R ₀ \	00	01	11	10
00	X	C0'	X	C1'
01	0	X	X	X
11	X	X	X	X
10	0	X	X	X

$$N_3 = R_2C_0' + R_3C_1'$$

4.11.3 Decoder

R ₃ R ₂ R ₁ R ₀ C ₀ C ₁ C ₂	N ₃	N ₂	N ₁	N ₀
0 0 0 1 1 0 0	0	0	0	1
0 0 0 1 0 1 0	0	0	1	0
0 0 0 1 0 0 1	0	0	1	1
0 0 1 0 1 0 0	0	1	0	0
0 0 1 0 0 1 0	0	1	0	1
0 0 1 0 0 0 1	0	1	1	0
0 1 0 0 1 0 0	0	1	1	1
0 1 0 0 0 1 0	1	0	0	0
0 1 0 0 0 0 1	1	0	0	1
1 0 0 0 1 0 0	1	0	1	0 (*)
1 0 0 0 0 1 0	0	0	0	0
1 0 0 0 0 0 1	1	0	1	1 (#)

\R ₃ R ₂ R ₁ R ₀ \	00	01	11	10
00	X		X	
01		X	X	X
11	X	X	X	X
10		X	X	X

4.11.3 Decoder

R ₃ R ₂ R ₁ R ₀ C ₀ C ₁ C ₂	N ₃	N ₂	N ₁	N ₀
0 0 0 1 1 0 0	0	0	0	1
0 0 0 1 0 1 0	0	0	1	0
0 0 0 1 0 0 1	0	0	1	1
0 0 1 0 1 0 0	0	1	0	0
0 0 1 0 0 1 0	0	1	0	1
0 0 1 0 0 0 1	0	1	1	0
0 1 0 0 1 0 0	0	1	1	1
0 1 0 0 0 1 0	1	0	0	0
0 1 0 0 0 0 1	1	0	0	1
1 0 0 0 1 0 0	1	0	1	0 (*)
1 0 0 0 0 1 0	0	0	0	0
1 0 0 0 0 0 1	1	0	1	1 (#)

\R ₃ R ₂ R ₁ R ₀ \	00	01	11	10
00	X	C0	X	0
01	0	X	X	X
11	X	X	X	X
10	1	X	X	X

4.11.3 Decoder

R ₃ R ₂ R ₁ R ₀ C ₀ C ₁ C ₂	N ₃	N ₂	N ₁	N ₀
0 0 0 1 1 0 0	0	0	0	1
0 0 0 1 0 1 0	0	0	1	0
0 0 0 1 0 0 1	0	0	1	1
0 0 1 0 1 0 0	0	1	0	0
0 0 1 0 0 1 0	0	1	0	1
0 0 1 0 0 0 1	0	1	1	0
0 1 0 0 1 0 0	0	1	1	1
0 1 0 0 0 1 0	1	0	0	0
0 1 0 0 0 0 1	1	0	0	1
1 0 0 0 1 0 0	1	0	1	0 (*)
1 0 0 0 0 1 0	0	0	0	0
1 0 0 0 0 0 1	1	0	1	1 (#)

\R ₃ R ₂ R ₁ R ₀ \	00	01	11	10
00	X	C0	X	0
01	0	X	X	X
11	X	X	X	X
10	1	X	X	X

$$N_2 = R_2C_0 + R_1$$

4.11.3 Decoder


$R_3 R_2 R_1 R_0 C_0 C_1 C_2$	N_3	N_2	N_1	N_0
0 0 0 1 1 0 0	0	0	0	1
0 0 0 1 0 1 0	0	0	1	0
0 0 0 1 0 0 1	0	0	1	1
0 0 1 0 1 0 0	0	1	0	0
0 0 1 0 0 1 0	0	1	0	1
0 0 1 0 0 0 1	0	1	1	0
0 1 0 0 1 0 0	0	1	1	1
0 1 0 0 0 1 0	1	0	0	0
0 1 0 0 0 0 1	1	0	0	1
1 0 0 0 1 0 0	1	0	1	0 (*)
1 0 0 0 0 1 0	0	0	0	0
1 0 0 0 0 0 1	1	0	1	1 (#)

$\backslash R_3 R_2$ $R_1 R_0 \backslash$	00	01	11	10
00	X	C1'	X	C2
01	C1'	X	X	X
11	X	X	X	X
10	C1	X	X	X

$$N_0 = R_1 C_1 + R_3 C_2 + R_3' R_1' C_1'$$

4.11.3 Decoder


$R_3 R_2 R_1 R_0 C_0 C_1 C_2$	N_3	N_2	N_1	N_0
0 0 0 1 1 0 0	0	0	0	1
0 0 0 1 0 1 0	0	0	1	0
0 0 0 1 0 0 1	0	0	1	1
0 0 1 0 1 0 0	0	1	0	0
0 0 1 0 0 1 0	0	1	0	1
0 0 1 0 0 0 1	0	1	1	0
0 1 0 0 1 0 0	0	1	1	1
0 1 0 0 0 1 0	1	0	0	0
0 1 0 0 0 0 1	1	0	0	1
1 0 0 0 1 0 0	1	0	1	0 (*)
1 0 0 0 0 1 0	0	0	0	0
1 0 0 0 0 0 1	1	0	1	1 (#)

 

$$N_3 = R_2 C_0' + R_3 C_1'$$

4.11.3 Decoder


$R_3 R_2 R_1 R_0 C_0 C_1 C_2$	N_3	N_2	N_1	N_0
0 0 0 1 1 0 0	0	0	0	1
0 0 0 1 0 1 0	0	0	1	0
0 0 0 1 0 0 1	0	0	1	1
0 0 1 0 1 0 0	0	1	0	0
0 0 1 0 0 1 0	0	1	0	1
0 0 1 0 0 0 1	0	1	1	0
0 1 0 0 1 0 0	0	1	1	1
0 1 0 0 0 1 0	1	0	0	0
0 1 0 0 0 0 1	1	0	0	1
1 0 0 0 1 0 0	1	0	1	0 (*)
1 0 0 0 0 1 0	0	0	0	0
1 0 0 0 0 0 1	1	0	1	1 (#)

 

$$N2 = R1 + R2C0$$

4.11.3 Decoder


$R_3 R_2 R_1 R_0 C_0 C_1 C_2$	N_3	N_2	N_1	N_0
0 0 0 1 1 0 0	0	0	0	1
0 0 0 1 0 1 0	0	0	1	0
0 0 0 1 0 0 1	0	0	1	1
0 0 1 0 1 0 0	0	1	0	0
0 0 1 0 0 1 0	0	1	0	1
0 0 1 0 0 0 1	0	1	1	0
0 1 0 0 1 0 0	0	1	1	1
0 1 0 0 0 1 0	1	0	0	0
0 1 0 0 0 0 1	1	0	0	1
1 0 0 0 1 0 0	1	0	1	0 (*)
1 0 0 0 0 1 0	0	0	0	0
1 0 0 0 0 0 1	1	0	1	1 (#)

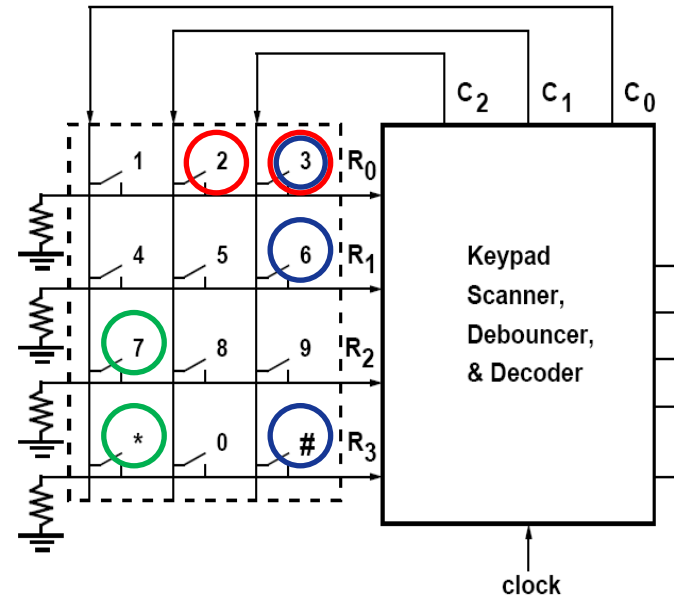

$$N1 = R0C0' + R2'C2 + R0'R1'C0$$

4.11.3 Decoder

$R_3 R_2 R_1 R_0 C_0 C_1 C_2$	N_3	N_2	N_1	N_0
0 0 0 1 1 0 0	0	0	0	1
0 0 0 1 0 1 0	0	0	1	0
0 0 0 1 0 0 1	0	0	1	1
0 0 1 0 1 0 0	0	1	0	0
0 0 1 0 0 1 0	0	1	0	1
0 0 1 0 0 0 1	0	1	1	0
0 1 0 0 1 0 0	0	1	1	1
0 1 0 0 0 1 0	1	0	0	0
0 1 0 0 0 0 1	1	0	0	1
1 0 0 0 1 0 0	1	0	1	0 (*)
1 0 0 0 0 1 0	0	0	0	0
1 0 0 0 0 0 1	1	0	1	1 (#)

 


$$N_0 = R_1 C_1 + R_1' C_2 + R_3' R_1' C_1'$$

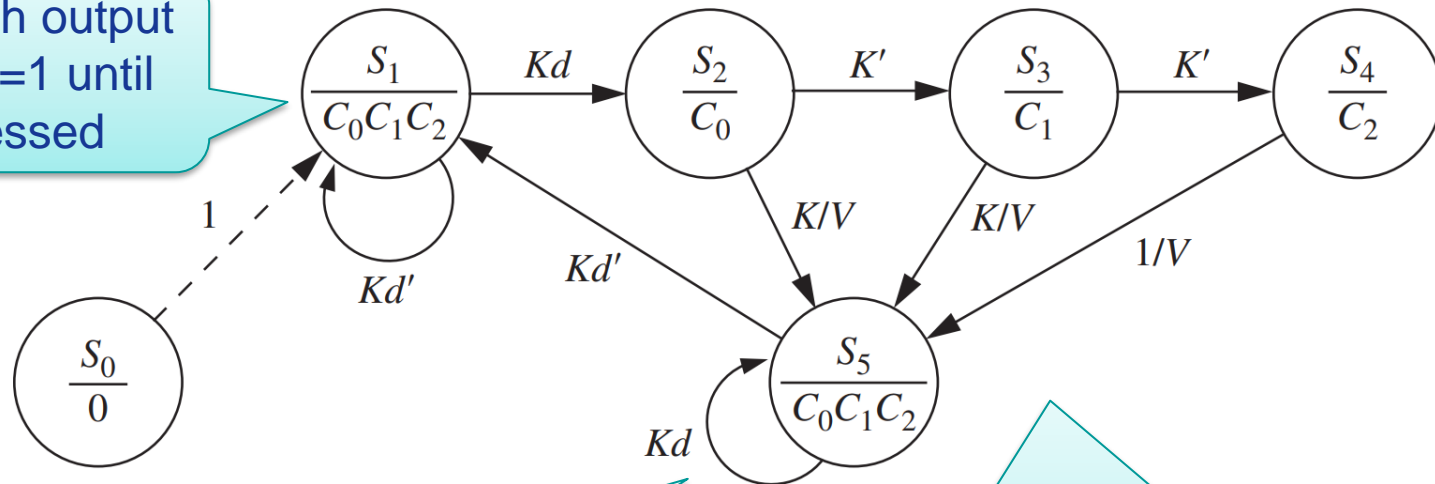4.11.4 Controller

State graph for Keypad Scanner_V1

S1: wait with output $C_0=C_1=C_2=1$ until a key is pressed




S2: $C_0=1$, so if the pressed key is in column 0, $K = 1$, and the circuit output $V=1$ and goes to S_5

S5: The circuit waits until all key are released and Kd goes to 0 before resetting

S3, S4: If no key is found in column 0, column 1 is checked, and if necessary, column 2 is checked

4.11.4 Controller

State graph for Keypad Scanner_V1

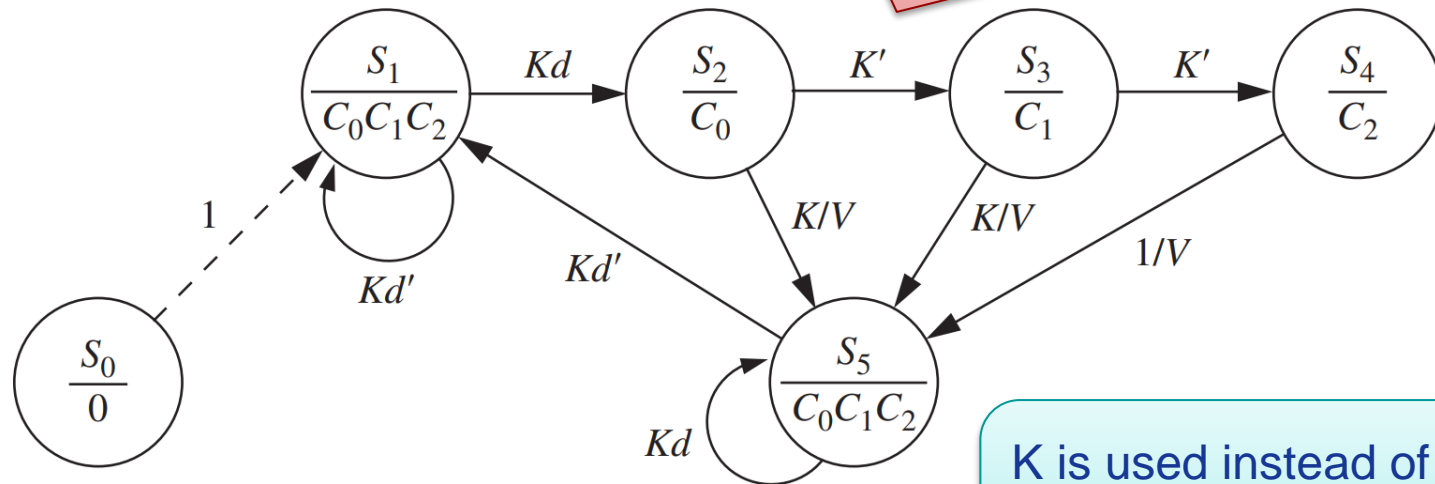


Why we use K here instead of Kd?


K is used instead of Kd, since the key press is already debounced


For example ...

4.11.4 Controller

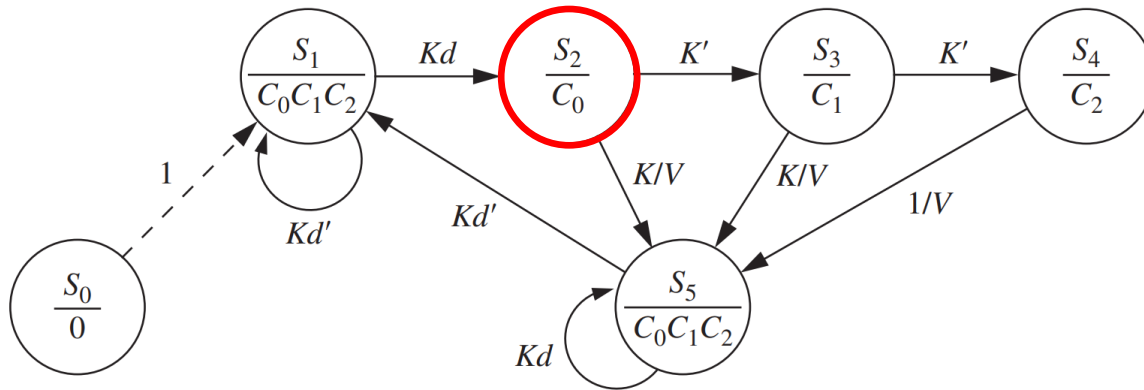

Example: assume **5** is pressed

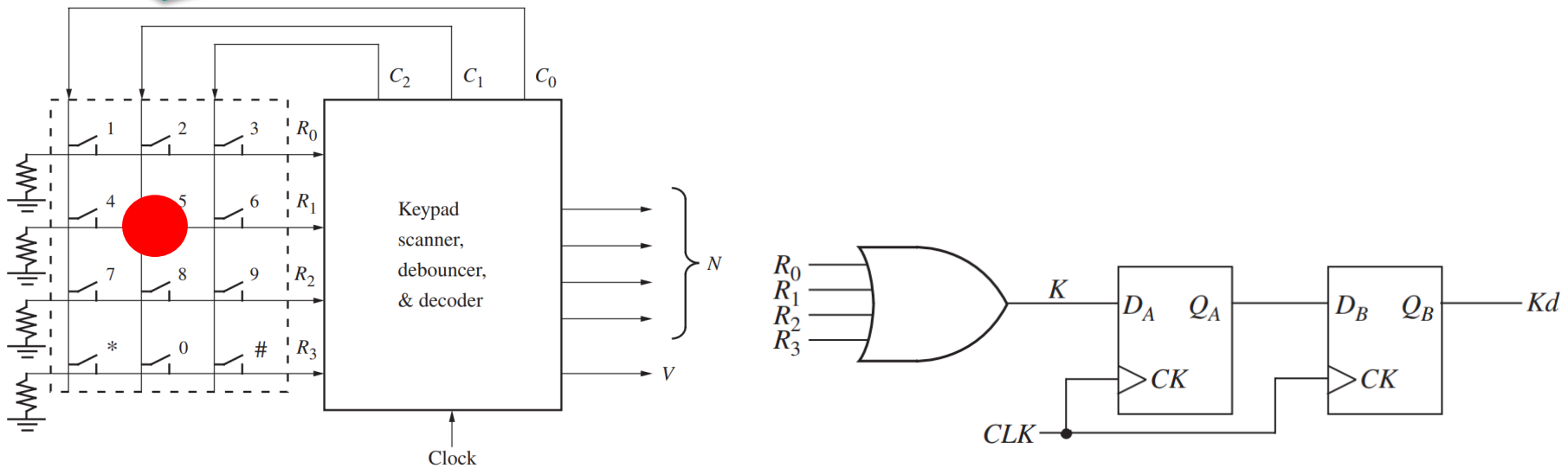


 

However, due to the two flip-flops, Kd will keep 1 for 2 clock periods



4.11.4 Controller

Timing problem with State graph_V1

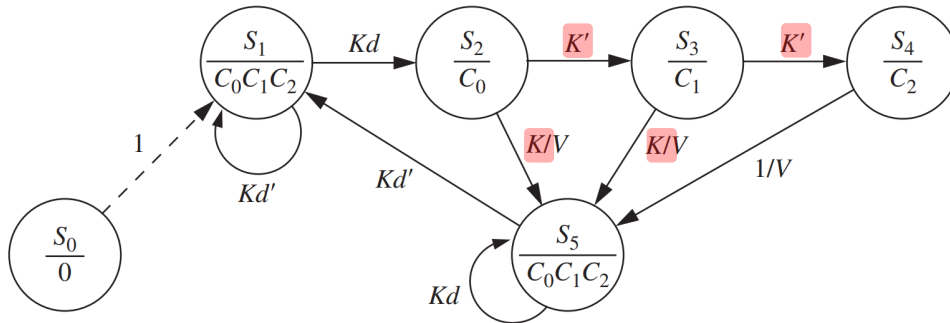

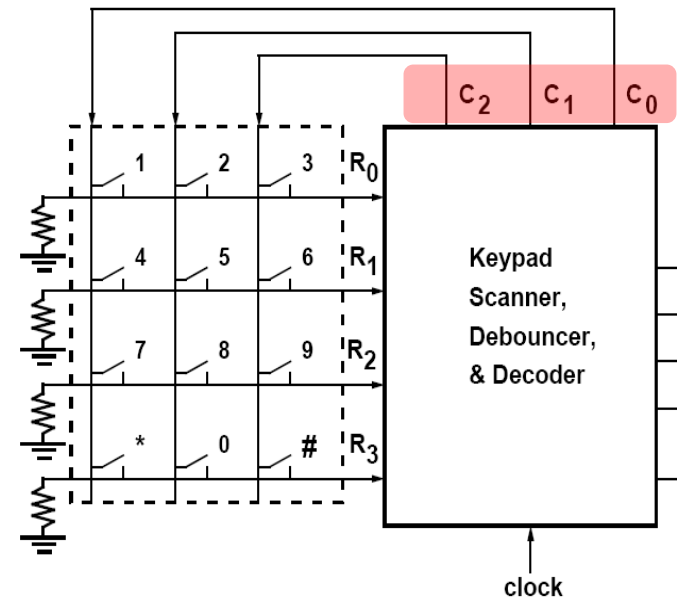
 
Problem 1: Is $K=1$ whenever a button is pressed?

- No.** Although K is true if any one of the row signals R_1 , R_2 , R_3 , or R_4 is true
- if the column scan signals are not active, none of R_1 – R_4 can be true, although the button is pressed




4.11.4 Controller

Timing problem with State graph_V1

 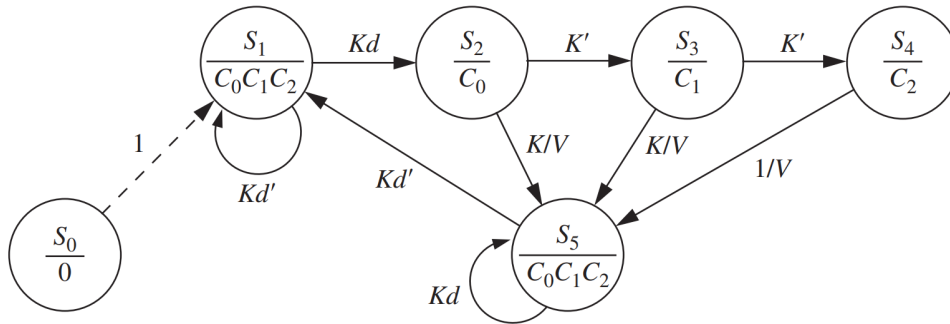



A button is pressed $\Rightarrow K = 1$

 A button is pressed & corresponding C_i is active $\Rightarrow K = 1$



4.11.4 Controller

Timing problem with State graph_V1

 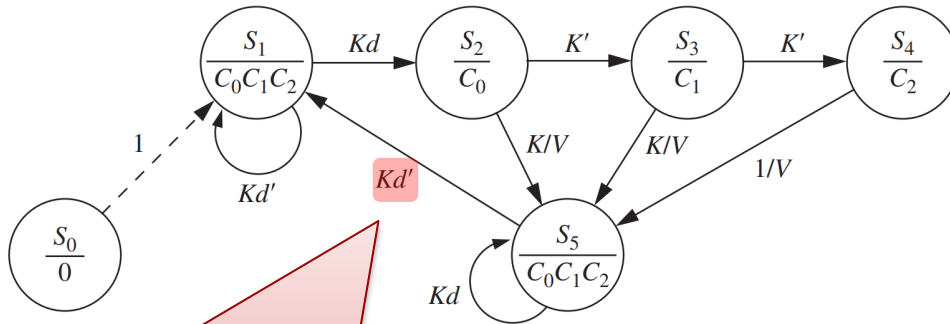




Problem 2: Can $Kd=0$ when a button is continuing to be pressed?

- **Yes.** Signal Kd is nothing but K delayed by two clock cycles
- K can go to 0 during the scan process even when the button is being pressed

➤ For example...

4.11.4 Controller

Timing problem with State graph_V1

  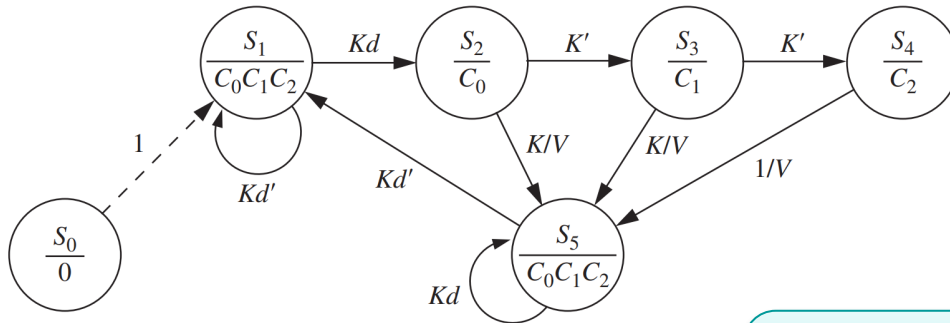



Example: consider the case when a key in the rightmost column is pressed

- During scan of the first two columns, K goes to 0
- If K goes to 0 at any time, Kd will go to zero two cycles later

Neither K nor Kd is the same as pressing the button

4.11.4 Controller

Timing problem with State graph_V1

 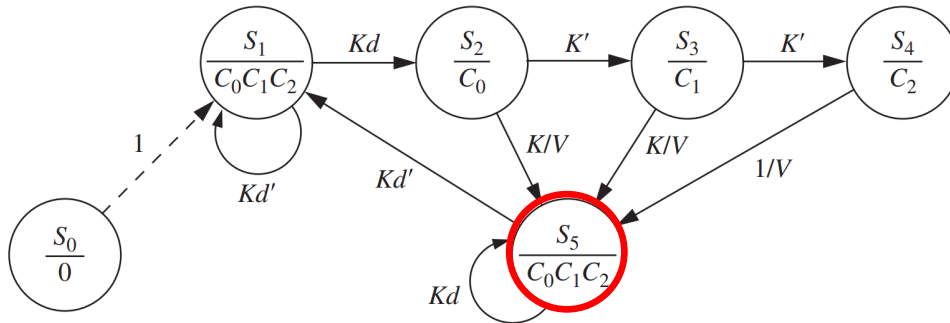



Problem 3: Can S_5 go to S_1 when a button is still pressed?

- **Yes.** S_4 -to- S_5 transition could happen when $Kd = 0$. Kd might have become false while scanning C_0 and C_1
- Hence, it is possible that one reaches back to S_1 when the key is still being pressed


➤ For example...




4.11.4 Controller

Timing problem with State graph_V1

 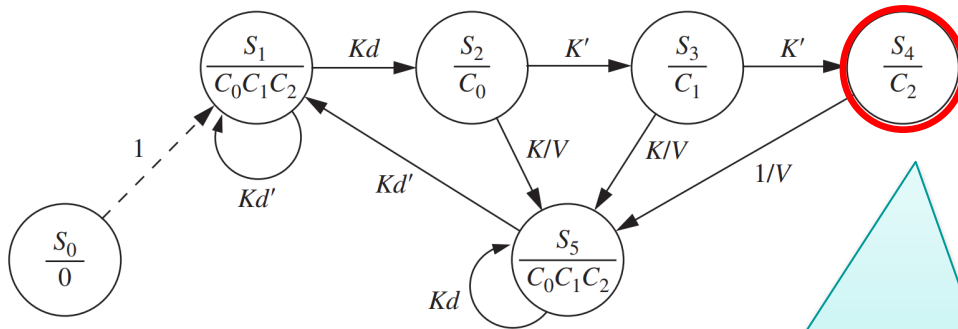



 
- Let us assume that a button is pressed in column C2
- This is to be detected in S_4



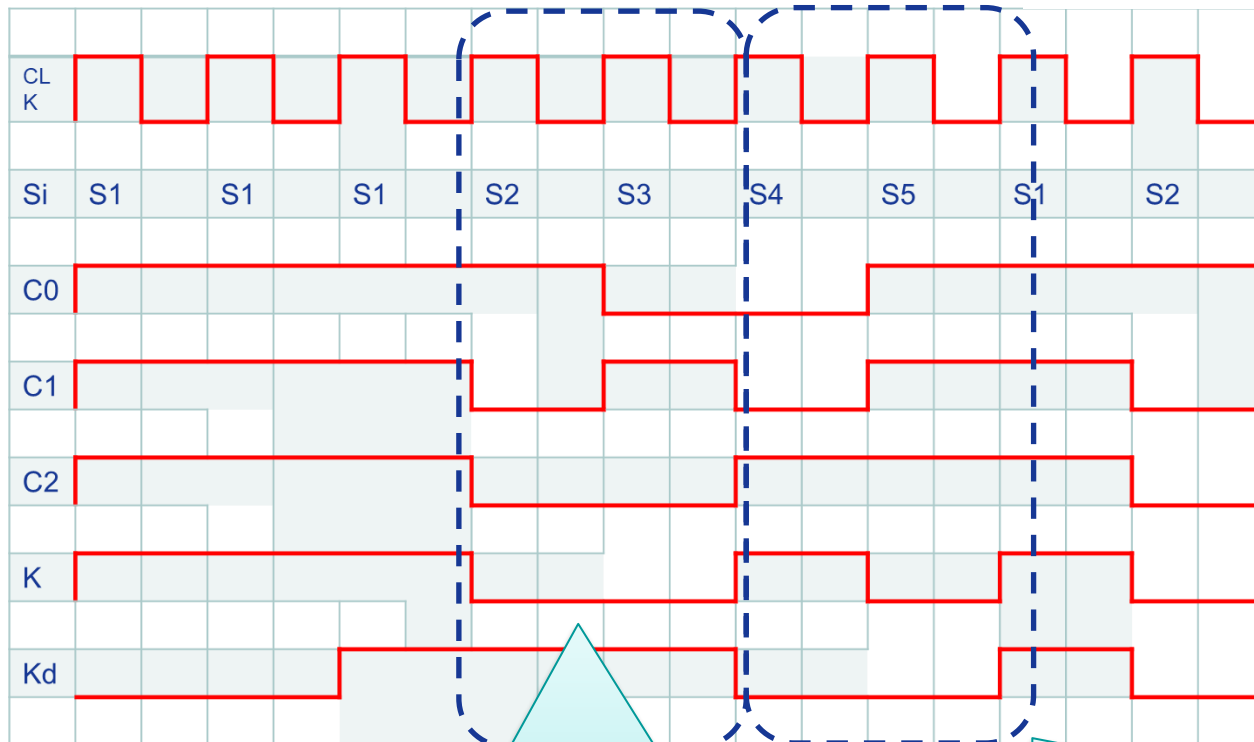 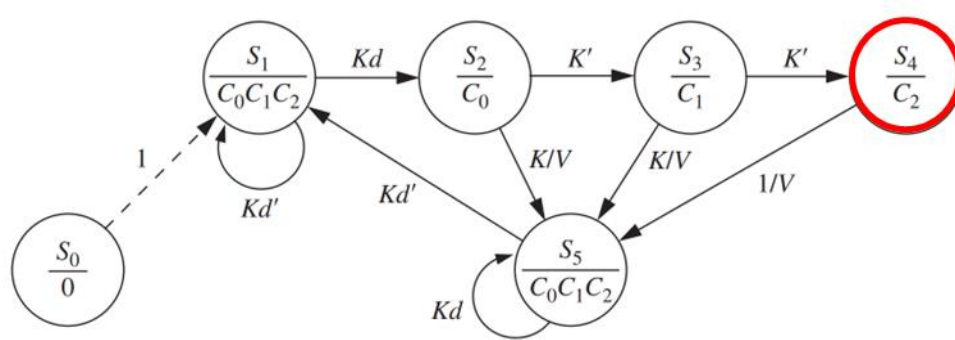

➤ However, during the scanning process in S2 and S3, K is 0

 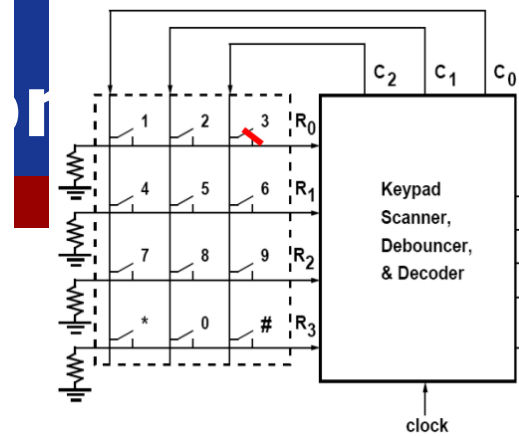 ➤ Hence, two cycles later Kd will be 0 even if the button stays pressed




➤ During the scan in S_4 , the correct key can be found



➤ However, the system can reach S_5 when Kd is still 0 and a malfunction can happen




4.11.4 Controller

Timing problem with State graph_V1

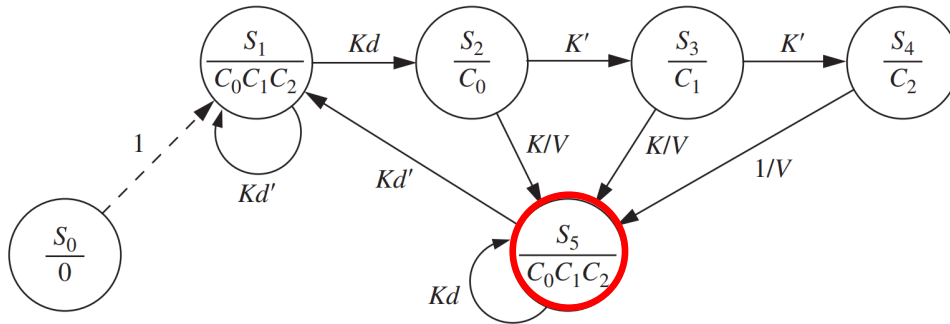

  - S_5 is intended to sense the release of the key
- However, Kd is not synonymous to pressing the button and Kd' does not truly indicate that the button got released




   


➤ In such a case, the same key may be read multiple times

➤ Since Kd' can appear when the button is still pressed, if S5 is reached when Kd' is true due to scanning activity in a previous state, the system can go from S5 to S1 without a key release



State graph for Keypad Scanner_V1

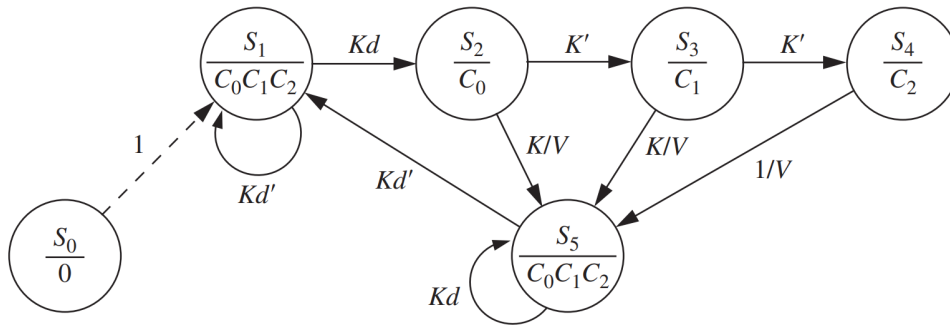

State graph for Keypad Scanner_V2

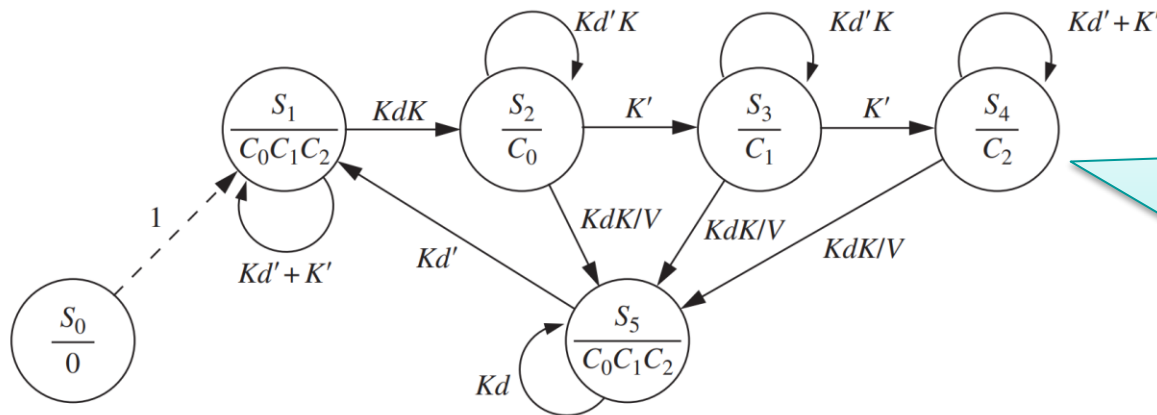

  The above problems can be fixed by assuring that one can reach S5 only if Kd is true



4.11.5 VHDL Code

entity scanner **is**

port(R0, R1, R2, R3, CLK: **in** bit;
C0, C1, C2: **inout** bit;
N0, N1, N2, N3, V: **out** bit);

end scanner;

architecture behavior **of** scanner **is**

signal QA, K, Kd: bit;

signal state, nextstate: integer **range** 0 to 5;

begin


K <= R0 **or** R1 **or** R2 **or** R3;

N3 <= (R2 **and not** C0) **or** (R3 **and not** C1);

N2 <= R1 **or** (R2 **and** C0);

N1 <= (R0 **and not** C0) **or** (**not** R2 **and** C2) **or** (**not** R1 **and not** R0 **and** C0);

 N0 <= (R1 **and** C1) **or** (**not** R1 **and** C2) **or** (**not** R3 **and not** R1 **and not** C1);



$$N3 = R2 C0' + R3 C1'$$

$$N2 = R1 + R2 C0$$

$$N1 = R0 C0' + R2' C2 + R1' R0' C0$$

$$N0 = R1 C1 + R1' C2 + R3' R1' C1'$$

Decoder

```
process(state, R0, R1, R2, R3, C0, C1, C2, K, Kd, QA)
```

```
begin
```

```
  C0 <= '0'; C1 <= '0'; C2 <= '0'; V <= '0';
```

```
  case state is
```

```
    when 0 => nextstate <= 1;
```

```
    when 1 => C0 <= '1'; C1 <= '1'; C2 <= '1';
```

```
      if (Kd and K) = '1' then nextstate <= 2;
```

```
      else nextstate <= 1;
```

```
      end if;
```

```
    when 2 => C0 <= '1';
```

```
      if (Kd and K) = '1' then V <= '1'; nextstate <= 5;
```

```
      elsif K = '0' then nextstate <= 3;
```

```
      else nextstate <= 2;
```

```
      end if;
```

```
    when 3 => C1 <= '1';
```

```
      if (Kd and K) = '1' then V <= '1'; nextstate <= 5;
```

```
      elsif K = '0' then nextstate <= 4;
```

```
      else nextstate <= 3;
```

```
      end if;
```

```
    when 4 => C2 <= '1';
```

```
      if (Kd and K) = '1' then V <= '1'; nextstate <= 5;
```

```
      else nextstate <= 4;
```

```
      end if;
```

```
    when 5 => C0 <= '1'; C1 <= '1'; C2 <= '1';
```

```
      if Kd = '0' then nextstate <= 1;
```



```
      else nextstate <= 5;
```

```
      end if;
```

```
  end case;
```

```
end process;
```

Scanner

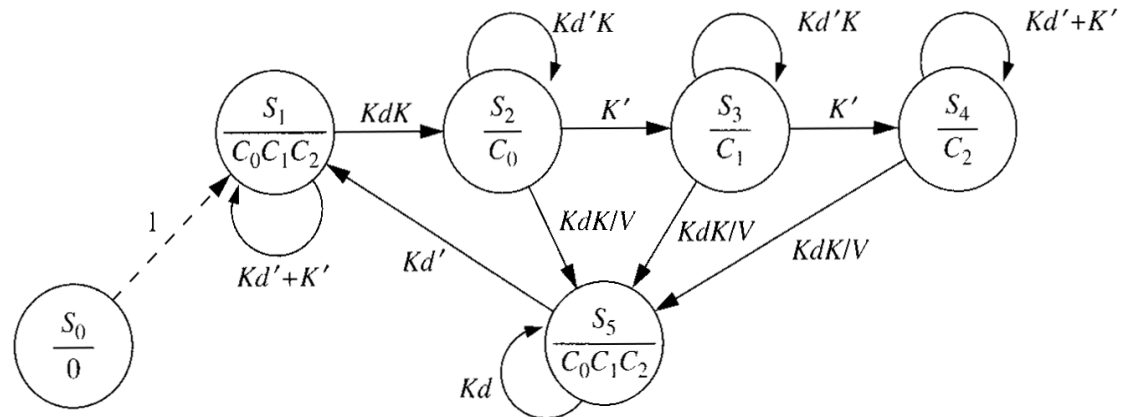 


```
process(CLK)
```

```
begin
```

```
  if CLK = '1' and CLK'EVENT then
```

```
    state <= nextstate;
```

```
    QA <= K;
```

```
    Kd <= QA;
```


```
  end if;
```

```
end process;
```

```
end behavior;
```



Debouncer

 

4.11.6 Test Bench for Keypad Scanner

```
library IEEE;  
use IEEE.numeric_bit.all;
```

```
entity scantest is  
end scantest;
```

```
architecture test1 of scantest is  
  component scanner
```

```
    port(R0, R1, R2, R3, CLK: in bit;  
          C0, C1, C2: inout bit;  
          N0, N1, N2, N3, V: out bit);
```

```
  end component;
```


```
  type arr is array (0 to 23) of integer;      -- array of keys to test
```

```
  constant KARRAY: arr := (2,5,8,0,3,6,9,11,1,4,7,10,1,2,3,4,5,6,7,8,9,10,11,0);
```



```
  signal C0, C1, C2, V, CLK, R0, R1, R2, R3: bit;  -- interface signals
```

```
  signal N: unsigned(3 downto 0);
```
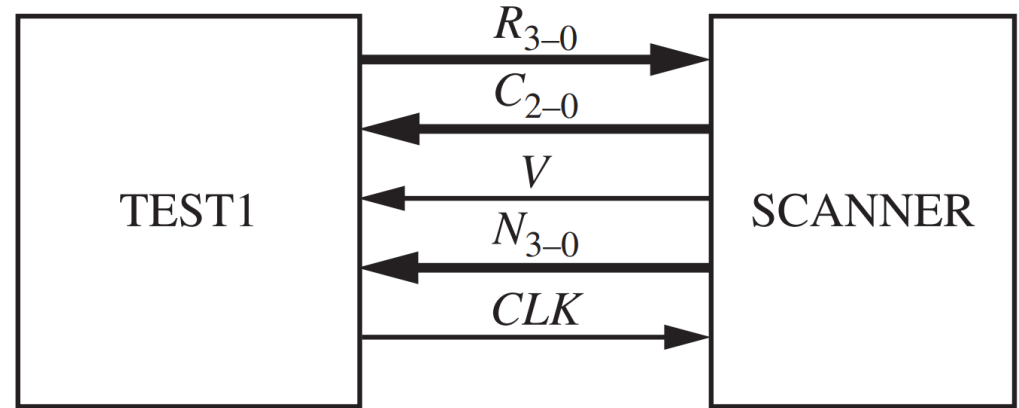
```
  signal KN: integer;                             -- key number to test
```



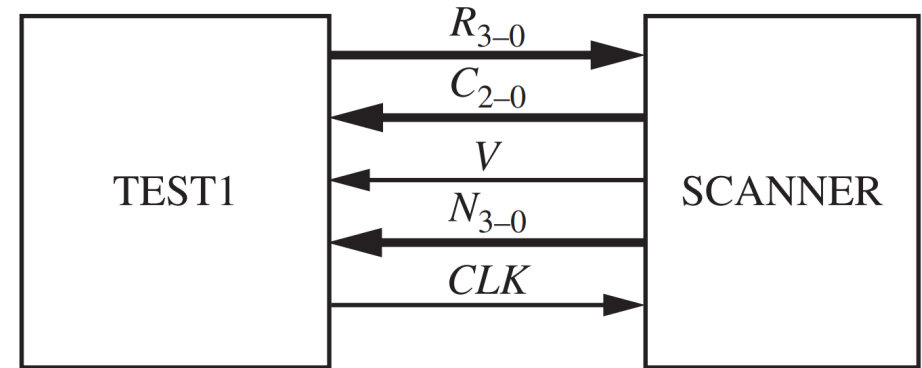 Scanner is treated as a **component** and embedded in test bench



Emulate the keypad

begin

CLK <= **not** CLK **after** 20 ns;

-- generate clock signal

R0 <= '1' when (C0='1' and KN=1) or (C1='1' and KN=2) or (C2='1' and KN=3)
else '0';

R1 <= '1' when (C0='1' and KN=4) or (C1='1' and KN=5) or (C2='1' and KN=6)
else '0';

R2 <= '1' when (C0='1' and KN=7) or (C1='1' and KN=8) or (C2='1' and KN=9)
else '0';

R3 <= '1' when (C0='1' and KN=10) or (C1='1' and KN=0) or (C2='1' and KN=11)
else '0';

```
process  
begin
```

```
-- this section tests scanner
```

```
for i in 0 to 23 loop
```

```
-- test every number in key array
```

```
KN <= KARRAY(i);
```

```
-- simulates keypress
```

```
wait until (V = '1' and rising_edge(CLK));
```

CLK = '1' and CLK'EVENT

```
assert (to_integer(N) = KN) -- check if output matches
```

```
report "Numbers don't match"
```

```
severity error;
```

```
KN <= 15;
```

```
-- equivalent to no key pressed
```

```
wait until rising_edge(CLK); -- wait for scanner to reset
```

```
wait until rising_edge(CLK);
```

```
wait until rising_edge(CLK);
```

```
end loop;
```


```
report "Test Complete.";
```

```
end process;
```

```
scanner1: scanner port map(R0,R1,R2,R3,CLK,C0,C1,C2,N(0),N(1),N(2),N(3),V);
```

```
-- connect test1 to scanner
```

```
end test1;
```

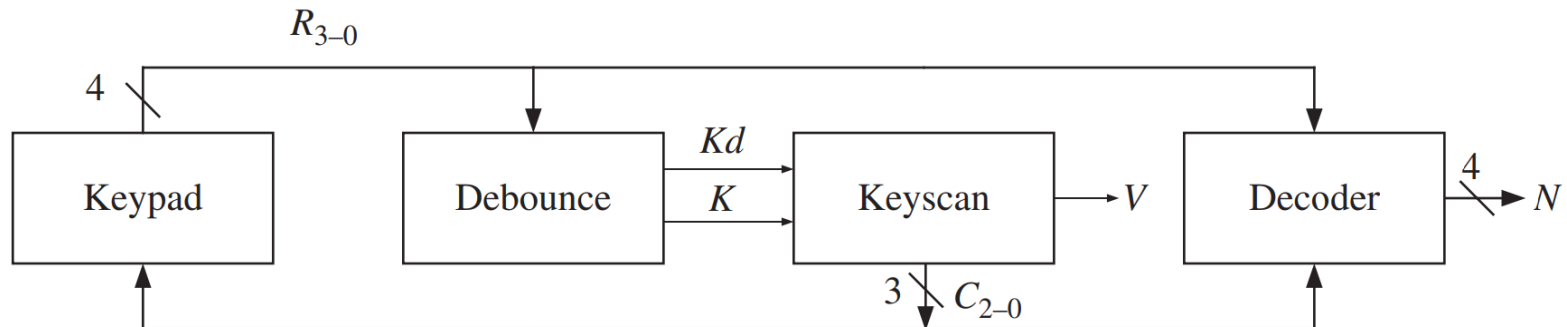

Chapter 4 Design Examples

	Contents
1	BCD to Seven-Segment Display Decoder
2	A BCD Adder
3	32-Bit Adders
4	Traffic Light Controller
5	State Graphs for Control Circuits
6	Scoreboard and Controller
7	Synchronization and Debouncing
8	Add-and-Shift Multiplier
9	Array Multiplier
10	A Signed Integer/Fraction Multiplier
11	Keypad Scanner
12	Binary Dividers

4.12.1 Unsigned Divider(无符号数除法器)

Start here

↓

Divisor (除数)	1101	/	10000111	Quotient (商)
			1101	Dividend (被除数)
			0111	
			0000	
			1111	
			1101	
			0101	
			0000	
			0101	Remainder (余数)

(135 ÷ 13 = 10 with 5)


Division can be carried out by a series of **subtract** & **shift** operations

4.12.1 Unsigned Dividers

(135 ÷ 13 = 10 with 5)

```
      1010
1101 ) 10000111
      1101
      0111
      0000
      1111
      1101
      0101
      0000
      0101
```

Dividend register (9 bits?)

 

? Quotient and remainder register


4.12.1 Unsigned Dividers

$$\begin{array}{r} 1010 \\ 1101 \overline{) 10000111} \\ \underline{1101} \rightarrow \\ 0111 \\ \underline{0000} \\ 1111 \\ \underline{1101} \rightarrow \\ 0101 \\ \underline{0000} \\ 0101 \end{array}$$

Divisor is shifted right →

X8 is used to store the bit when the dividend is shifted left

Instead, we shift the dividend left ←

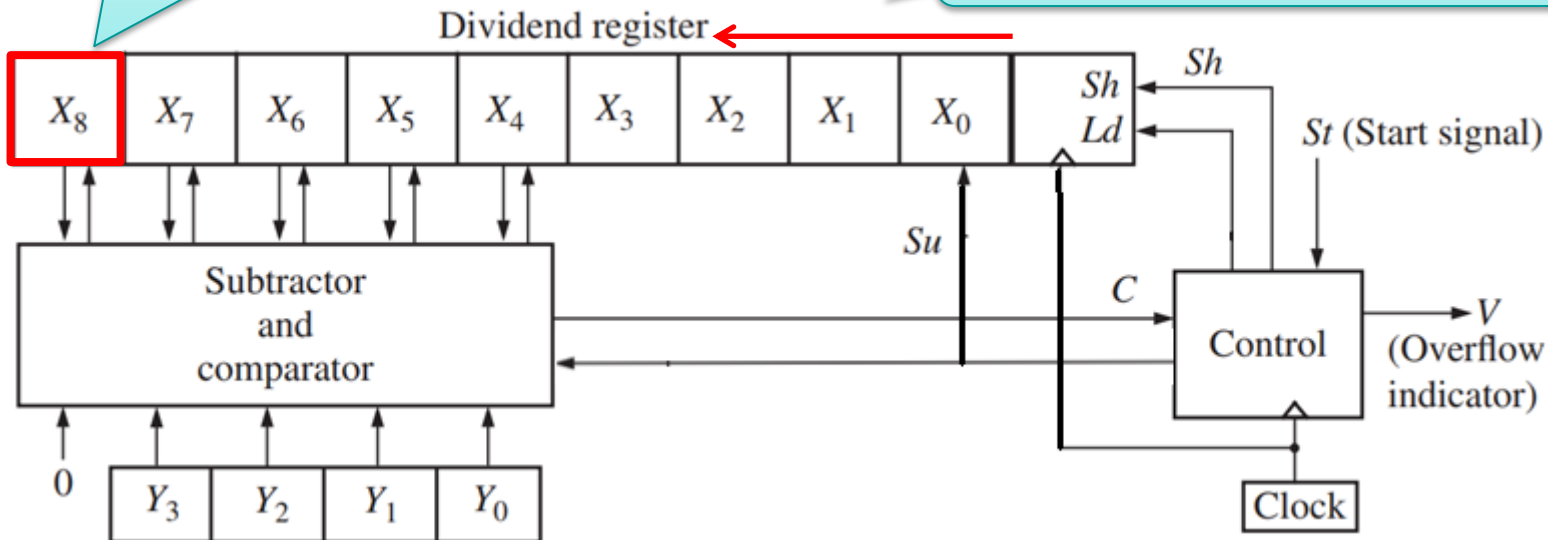


4.12.1 Unsigned Dividers

(135 ÷ 13 = 10 with 5)

```
      1010
1101 ) 10000111
      1101
      0111
      0000
      1111
      1101
      0101
      0000
      0101
```

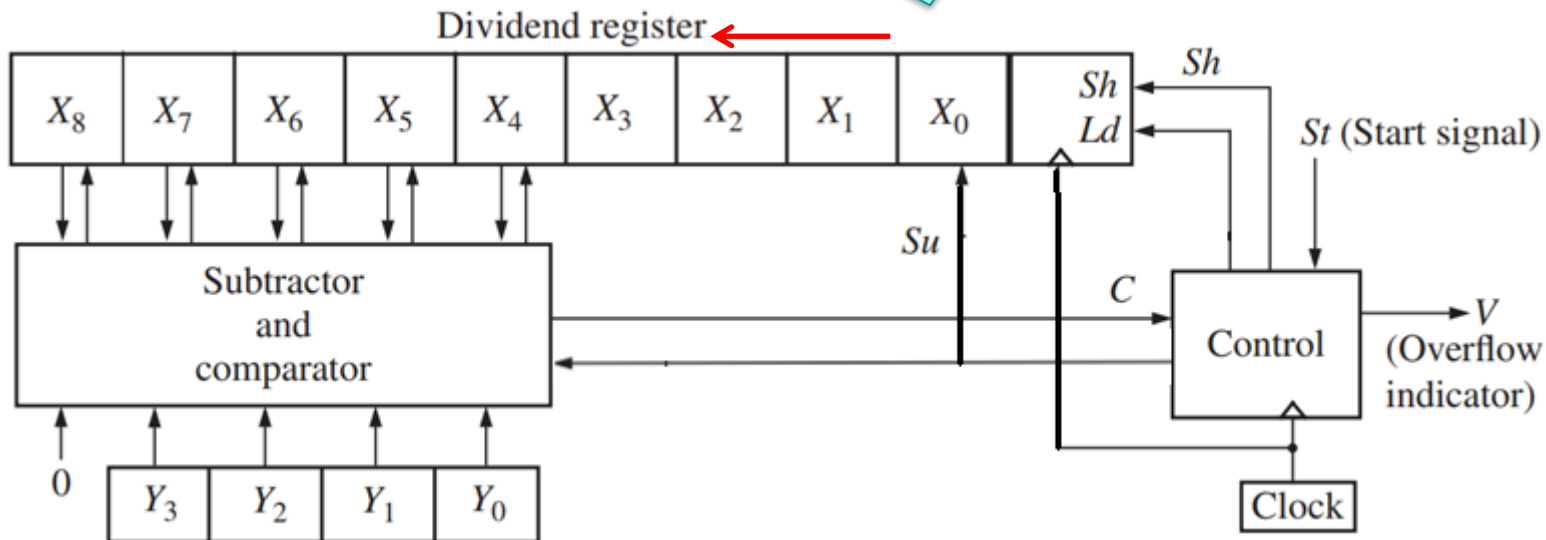Quotient is stored bit-by-bit into the right end of X




4.12.1 Unsigned Dividers

$$\begin{array}{r} 1010 \\ 1101 \overline{) 10000111} \\ \underline{1101} \\ 0111 \end{array}$$

(135 ÷ 13 = 10 with

Controller outputs:

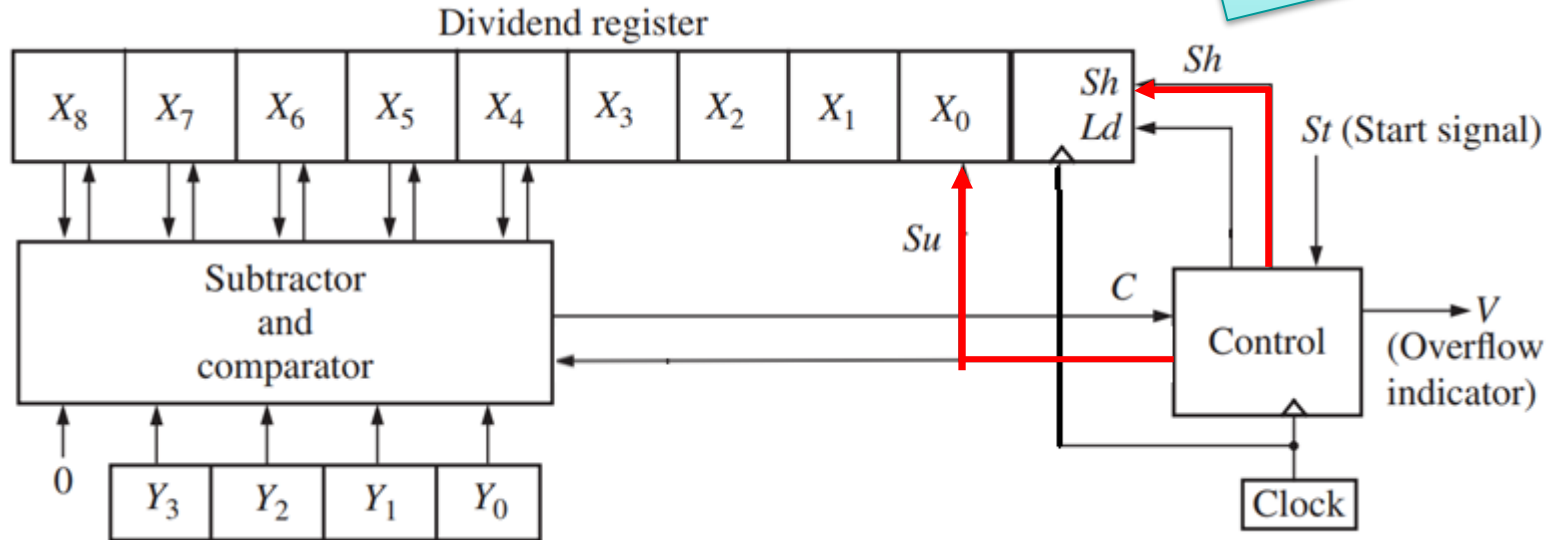
- **Sh**: shift dividend one bit to the left
- **Su**: subtract divisor Y(3:0) from X(8:4) and set quotient bit X(0) to 1




$$\begin{array}{r} \overline{) 1010} \\ \underline{1101} \\ 0111 \end{array}$$

(135 ÷ 13 = 10 with

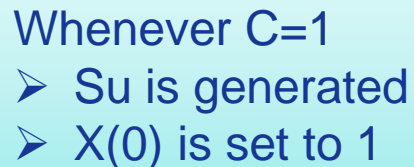- **St**: Start signal
- **C**: C=0 when divisor > X(8:4); otherwise, C=1



4.12.1 Unsigned Dividers

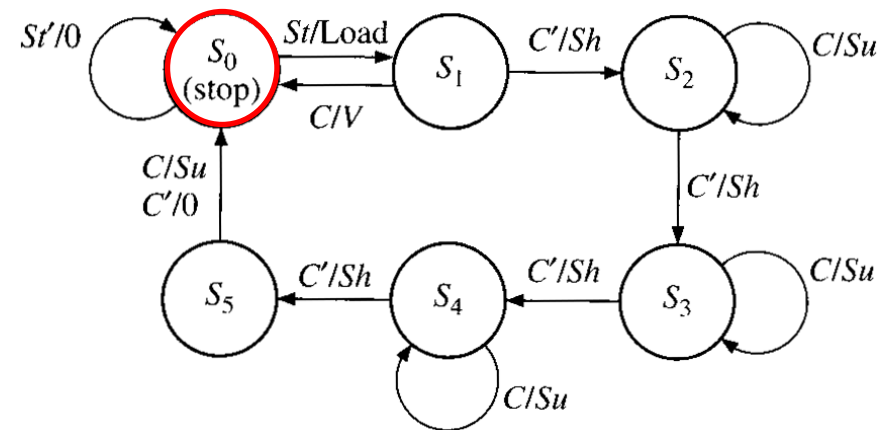

$$1101 \overline{) 10000111}$$

$$\underline{1101}$$

$$0111$$

$$\underline{0000}$$

$$1111$$


$$\underline{1101}$$

$$0101$$


$$\underline{0000}$$

$$0101$$

(135 ÷ 13 = 10 with 5)

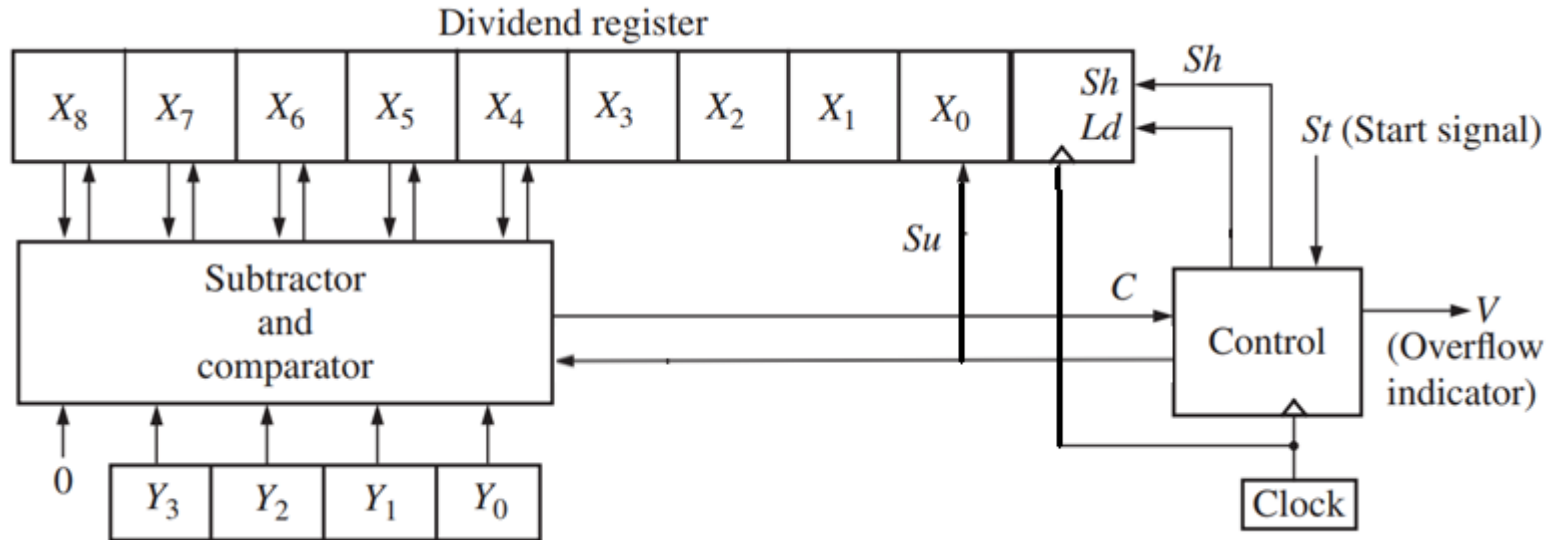


4.12.1 Unsigned Dividers

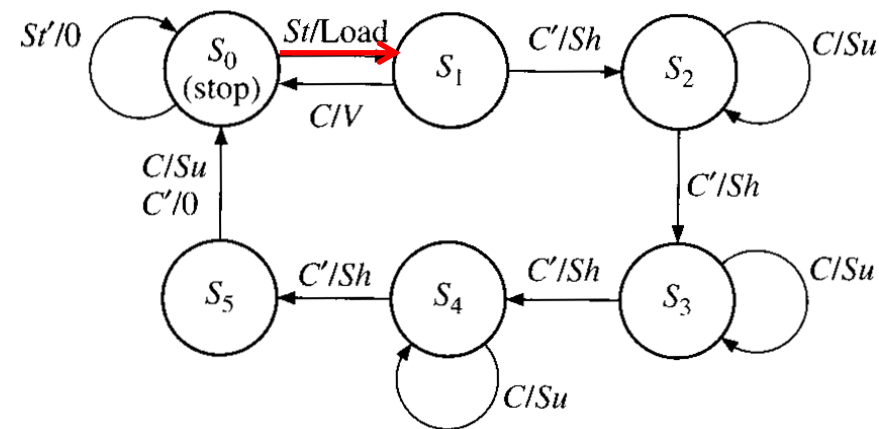


$$\begin{array}{r} 1010 \\ 1101 \overline{) 10000111} \\ \underline{1101} \\ 0111 \\ \underline{0000} \\ 1111 \\ \underline{1101} \\ 0101 \\ \underline{0000} \\ 0101 \end{array}$$

$(135 \div 13 = 10 \text{ with } 5)$

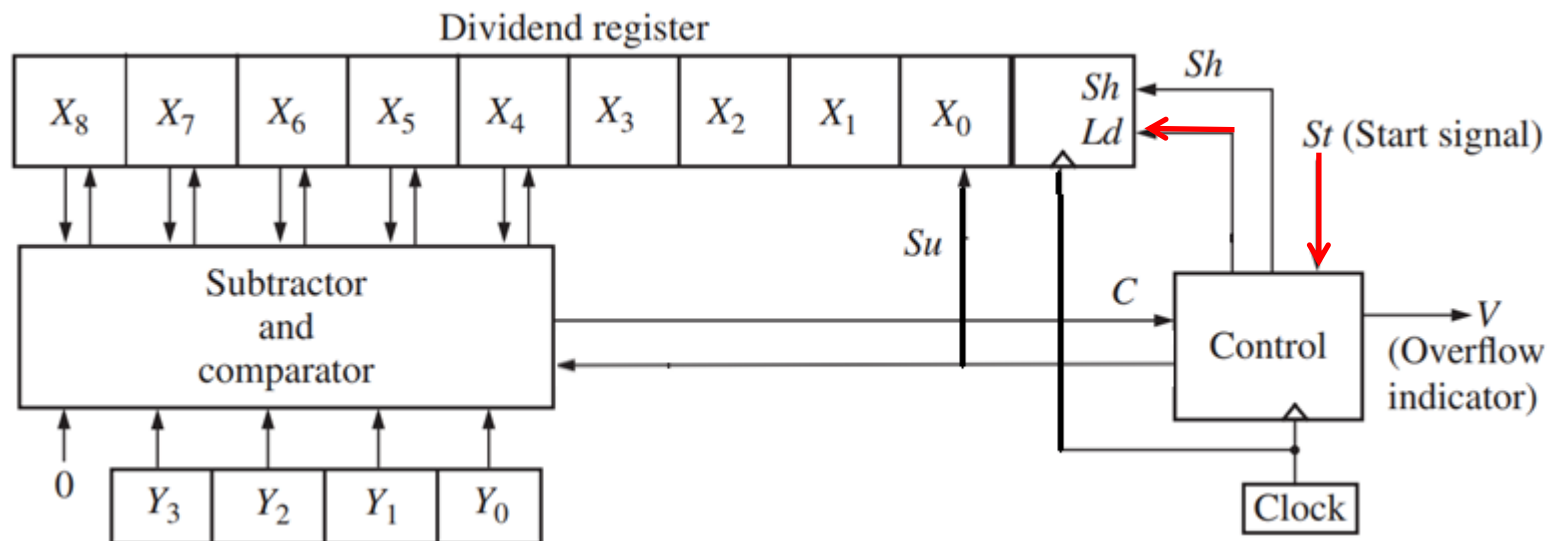


4.12.1 Unsigned Dividers

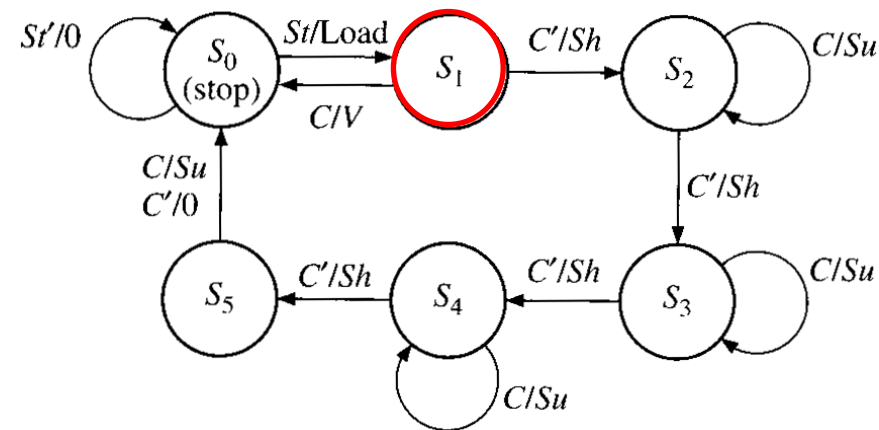


$$\begin{array}{r} 1010 \\ 1101 \overline{) 10000111} \\ \underline{1101} \\ 0111 \\ \underline{0000} \\ 1111 \\ \underline{1101} \\ 0101 \\ \underline{0000} \\ 0101 \end{array}$$

$(135 \div 13 = 10 \text{ with } 5)$

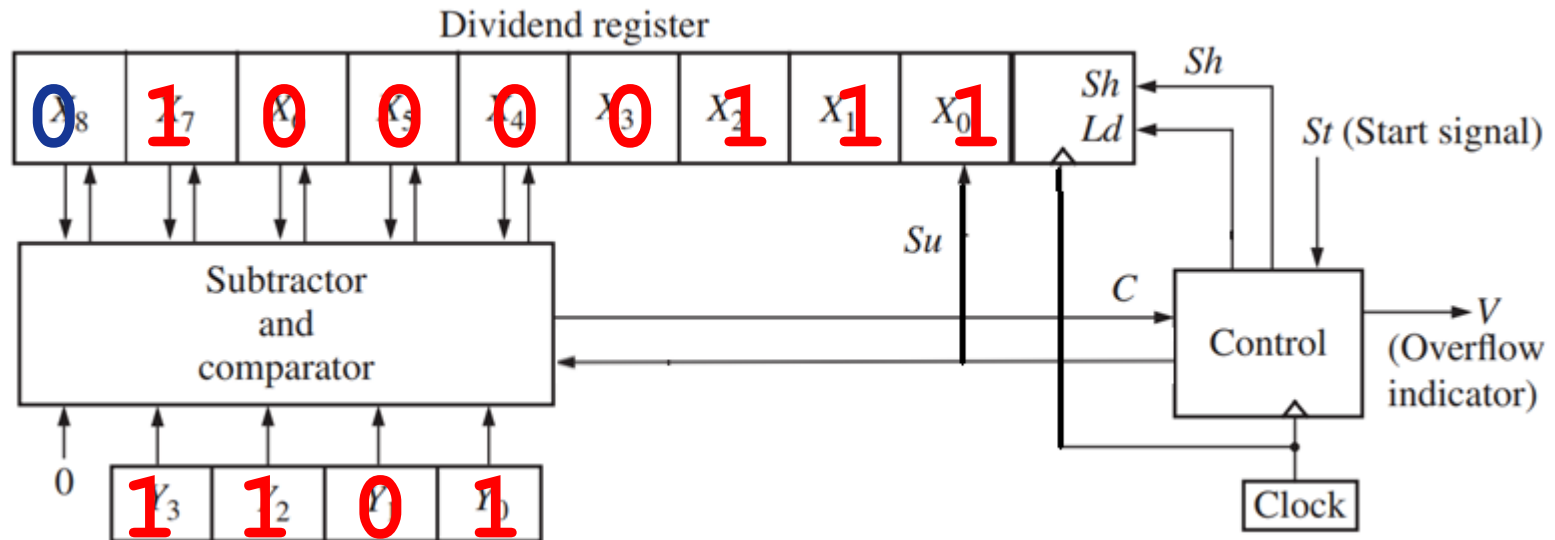


4.12.1 Unsigned Dividers

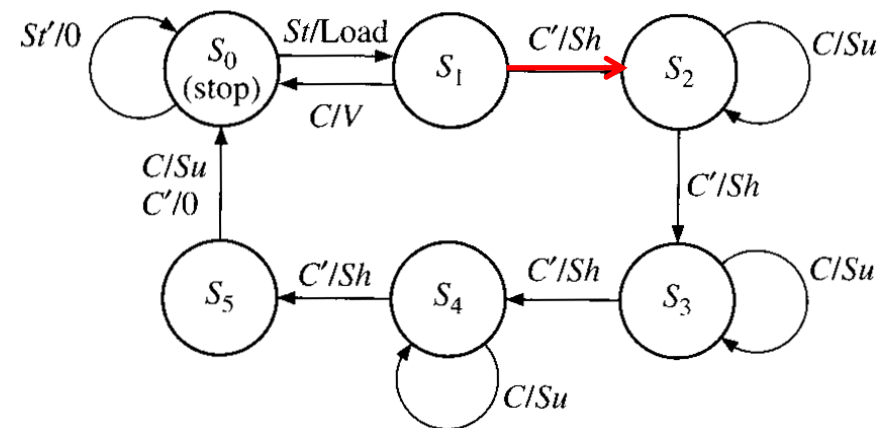


$$1101 \overline{) 10000111} \\ \underline{1101} \\ 0111 \\ \underline{0000} \\ 1111 \\ \underline{1101} \\ 0101 \\ \underline{0000} \\ 0101$$

(135 ÷ 13 = 10 with 5)

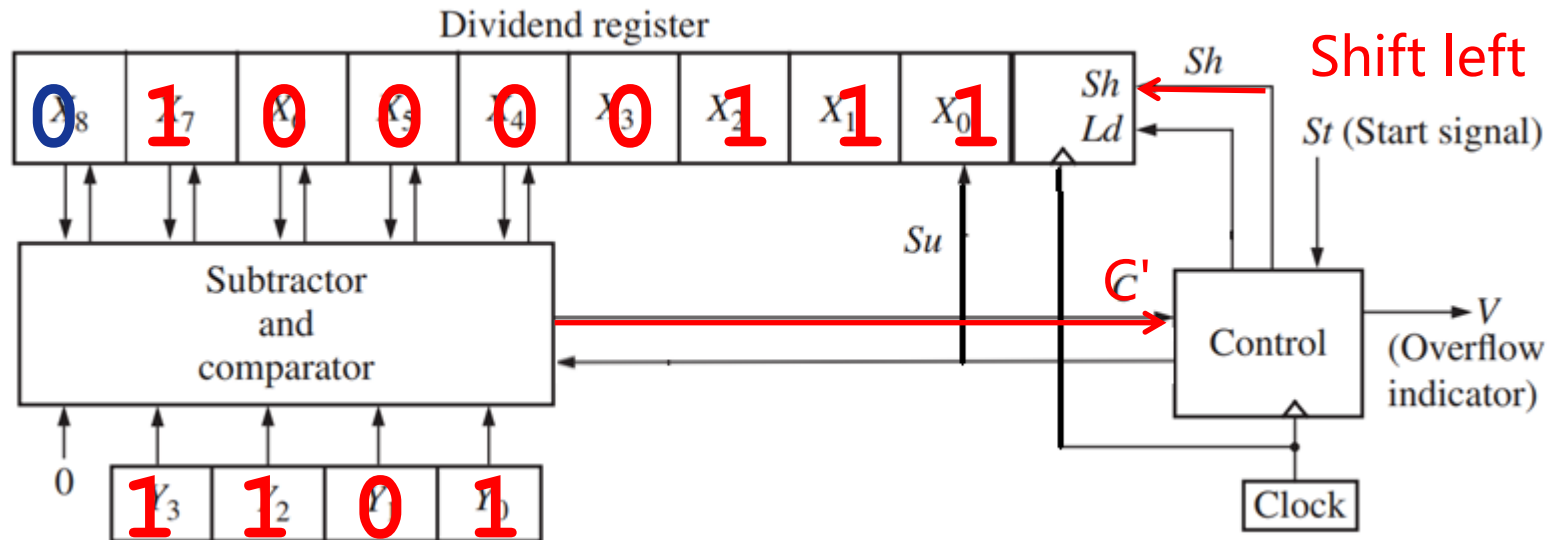


4.12.1 Unsigned Dividers

 


(135 ÷ 13 = 10 with 5)

```

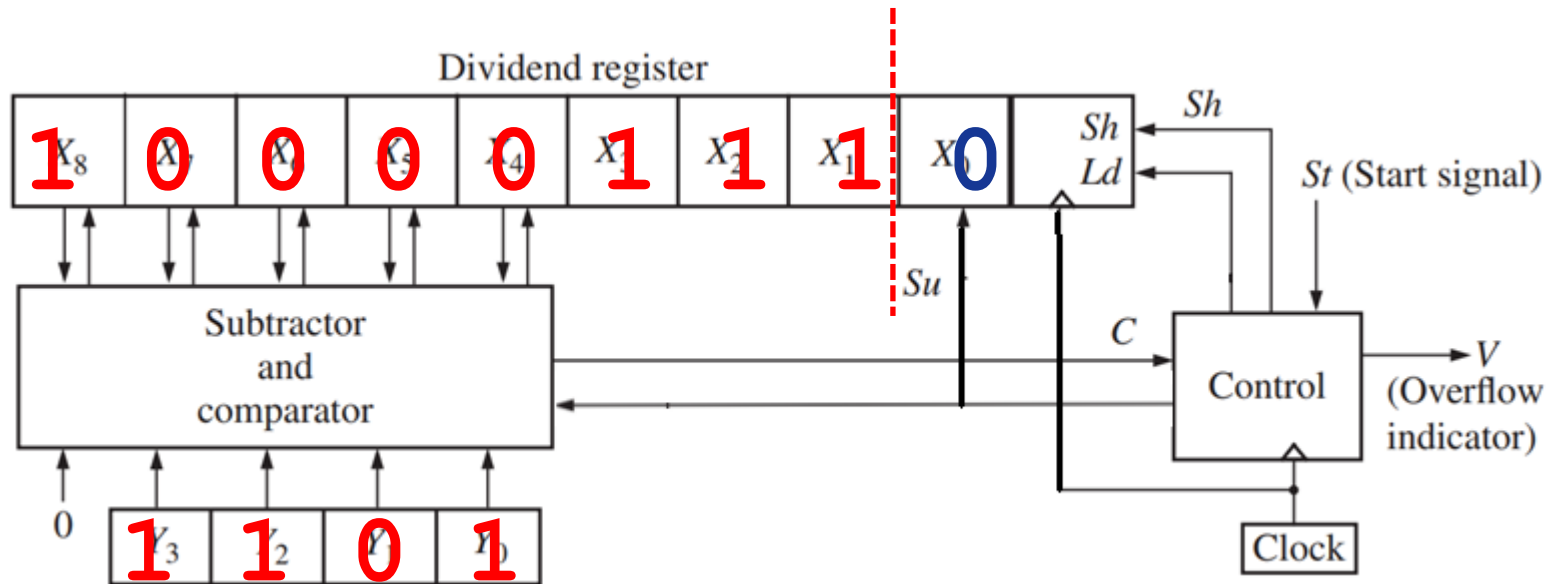      1010
1101 ) 10000111
      1101
      ---
      0111
      0000
      ---
      1111
      1101
      ---
      0101
      0000
      ---
      0101
  
```




4.12.1 Unsigned Dividers

 


(135 ÷ 13 = 10 with 5)

```

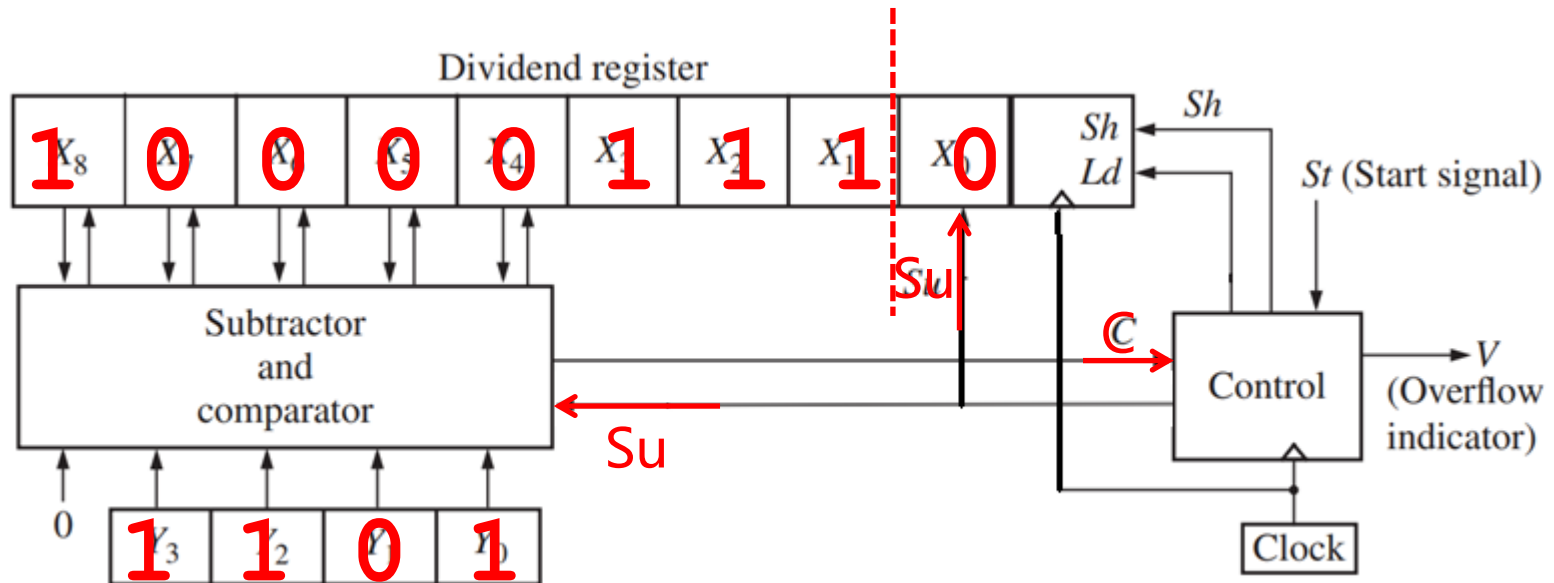      1010
1101 ) 10000111
      1101
      ----
       0111
       0000
       ----
        1111
        1101
        ----
         0101
         0000
         ----
          0101
    
```




4.12.1 Unsigned Dividers

 


(135 ÷ 13 = 10 with 5)

```

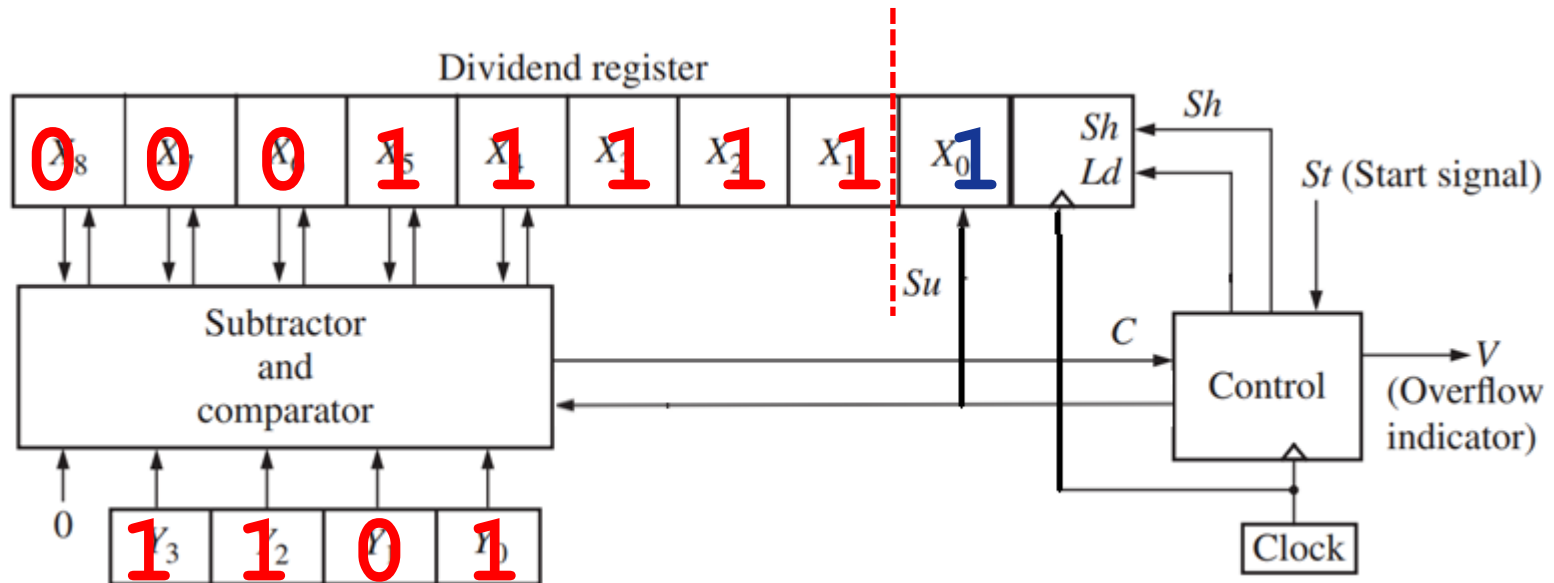      1010
1101 ) 10000111
      1101
      ---
       0111
       0000
       ---
        1111
        1101
        ---
         0101
         0000
         ---
          0101
    
```




4.12.1 Unsigned Dividers

 


(135 ÷ 13 = 10 with 5)

```

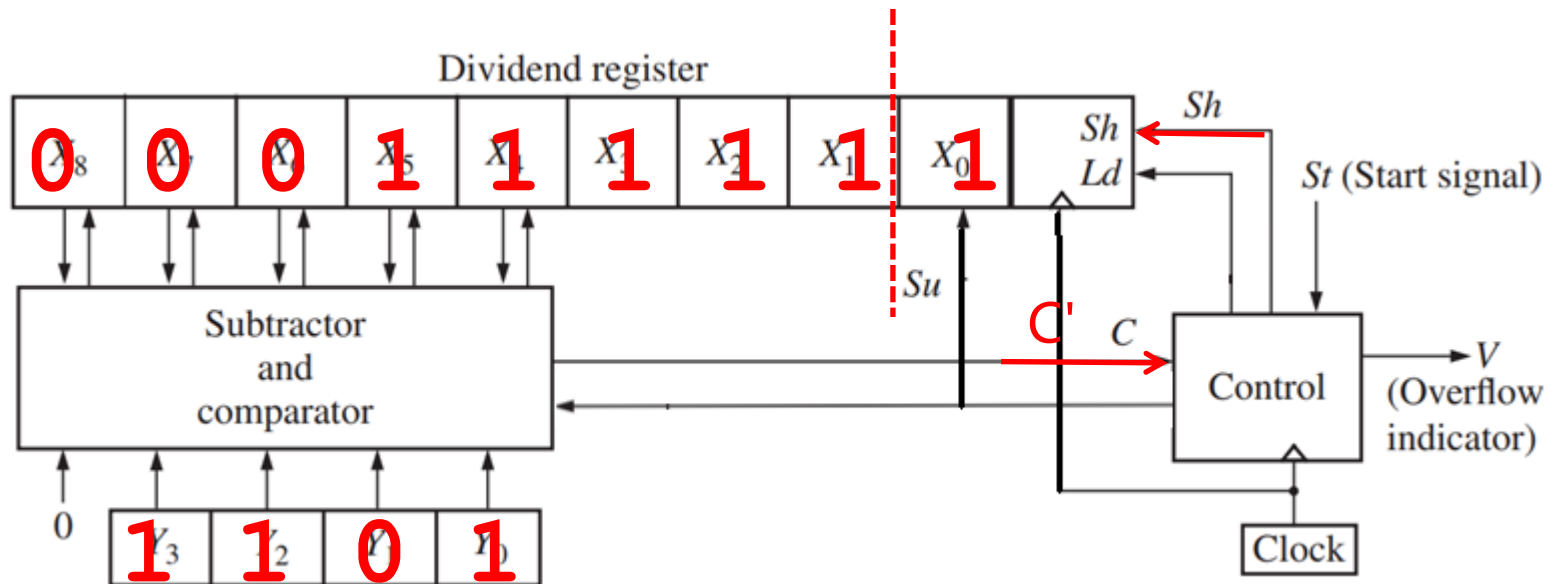      1010
1101 ) 10000111
      1101
      ---
       0111
       0000
       ---
        1111
        1101
        ---
         0101
         0000
         ---
          0101
  
```




4.12.1 Unsigned Dividers

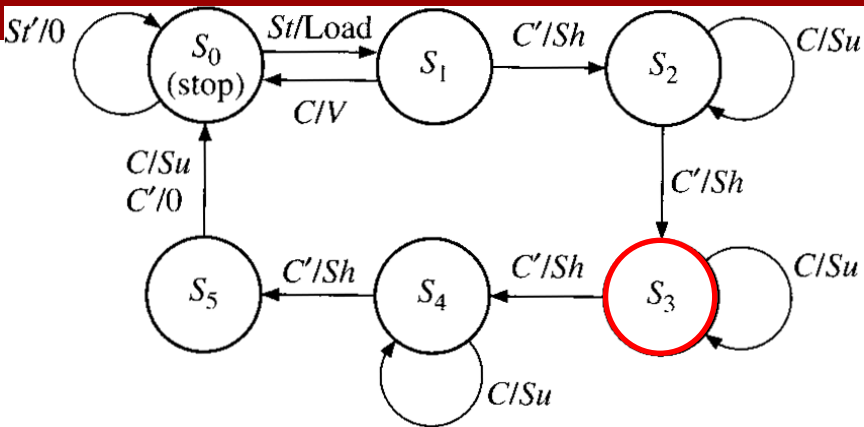


(135 ÷ 13 = 10 with 5)

```

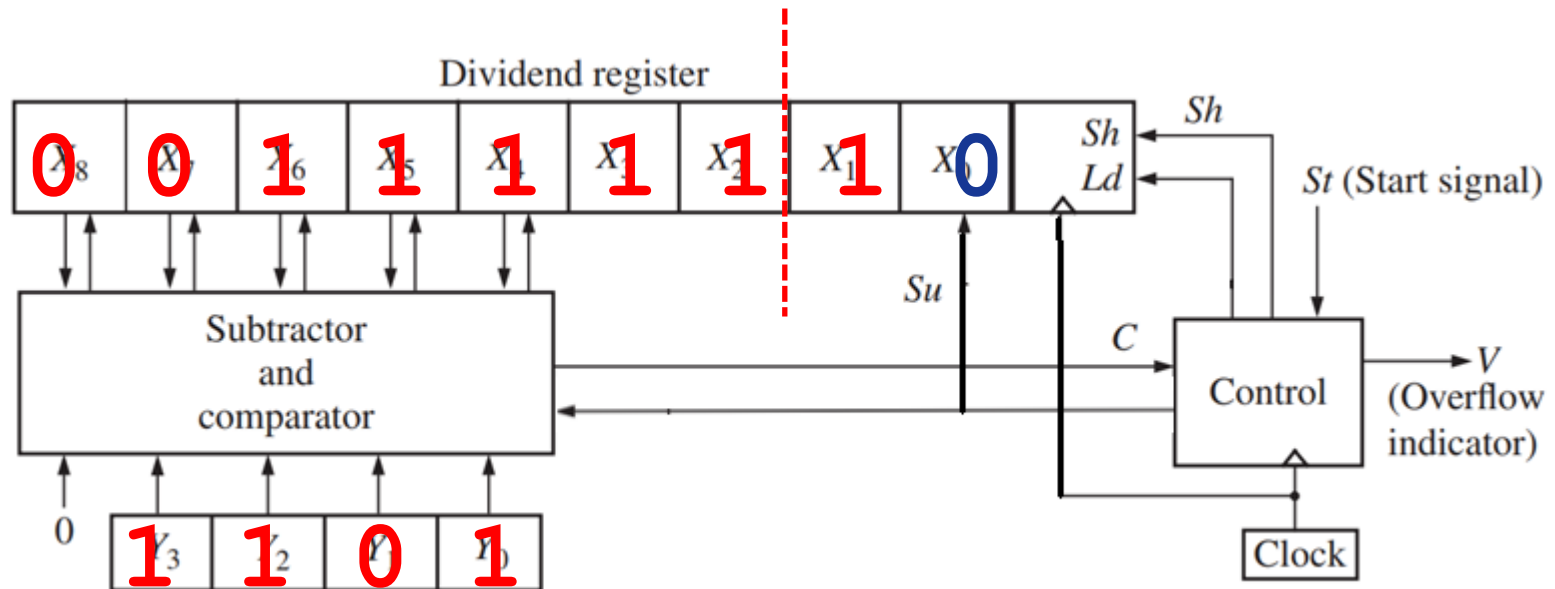      1010
1101 ) 10000111
      1101
      ----
      0111
      0000
      ----
      1111
      1101
      ----
      0101
      0000
      ----
      0101
    
```




4.12.1 Unsigned Dividers

 


(135 ÷ 13 = 10 with 5)

```

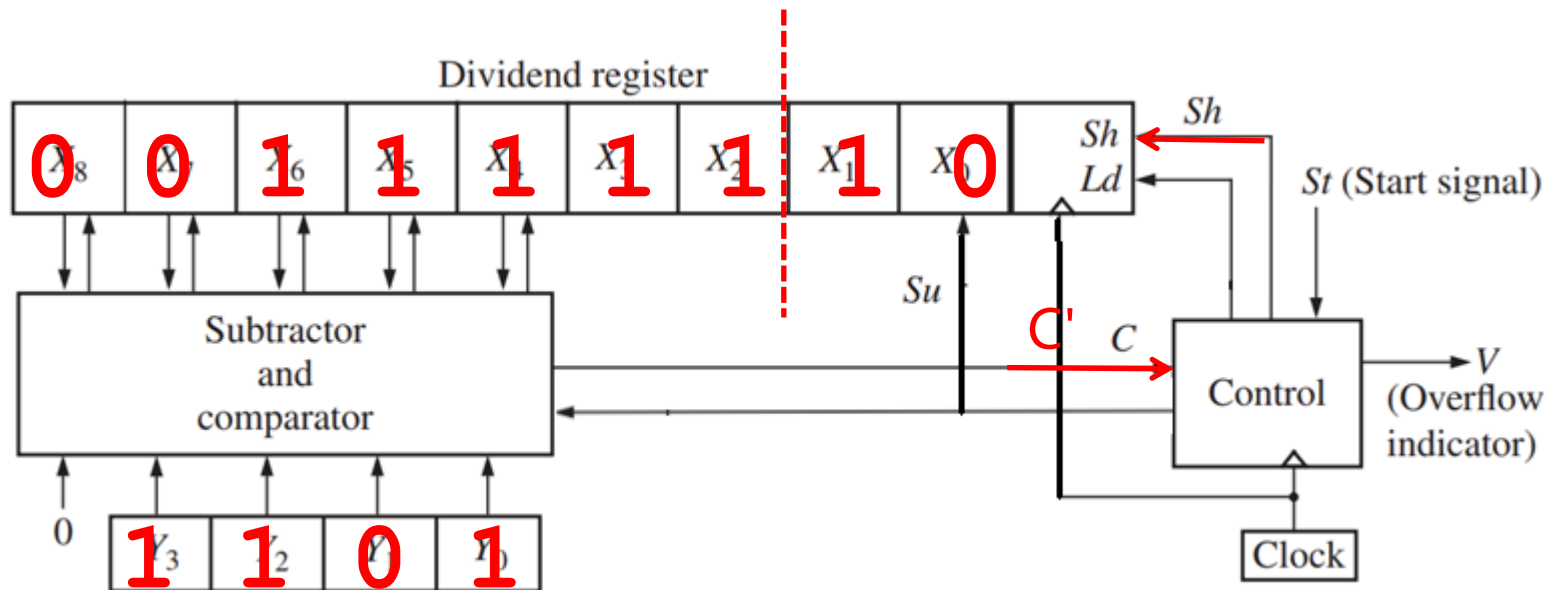      1010
1101 ) 10000111
      1101
      ---
      0111
      0000
      ---
      1111
      1101
      ---
      0101
      0000
      ---
      0101
    
```




4.12.1 Unsigned Dividers

 


(135 ÷ 13 = 10 with 5)
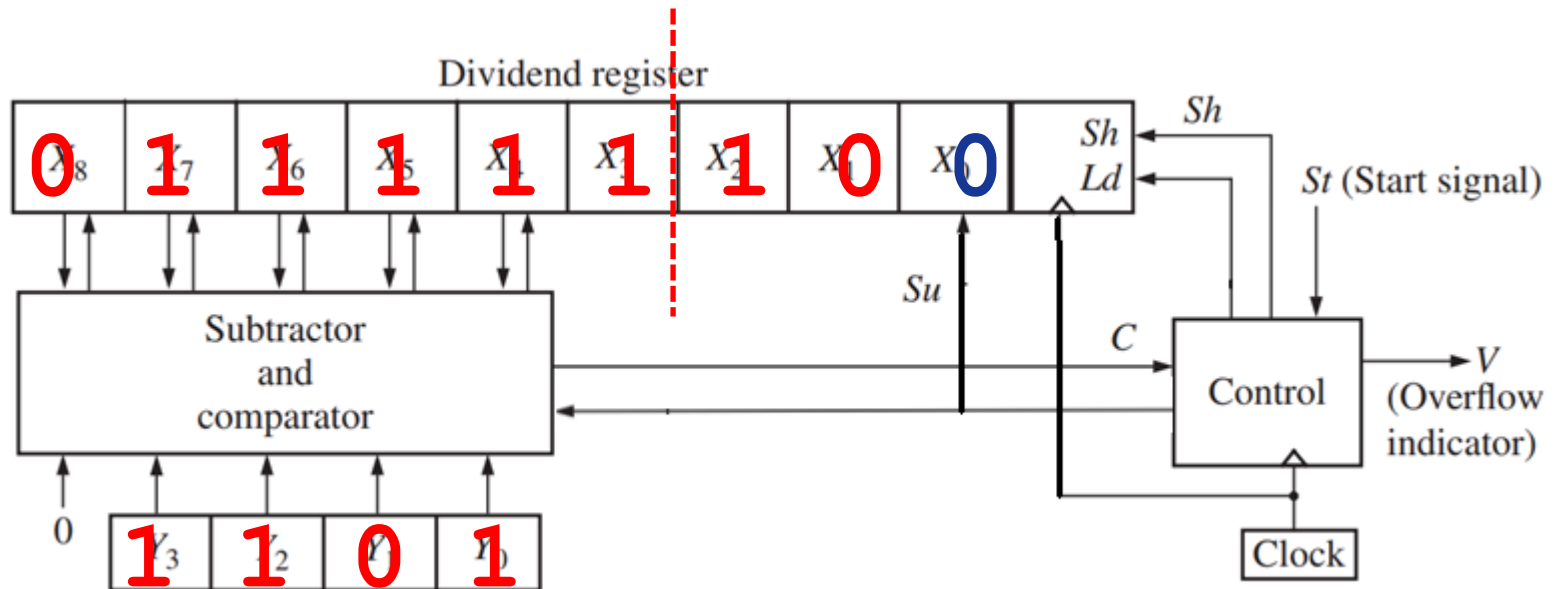
$$\begin{array}{r}
 1010 \\
 1101 \overline{) 10000111} \\
 \underline{1101} \\
 0111 \\
 \underline{0000} \\
 1111 \\
 \underline{1101} \\
 0101 \\
 \underline{0000} \\
 0101
 \end{array}$$




4.12.1 Unsigned Dividers

 


(135 ÷ 13 = 10 with 5)
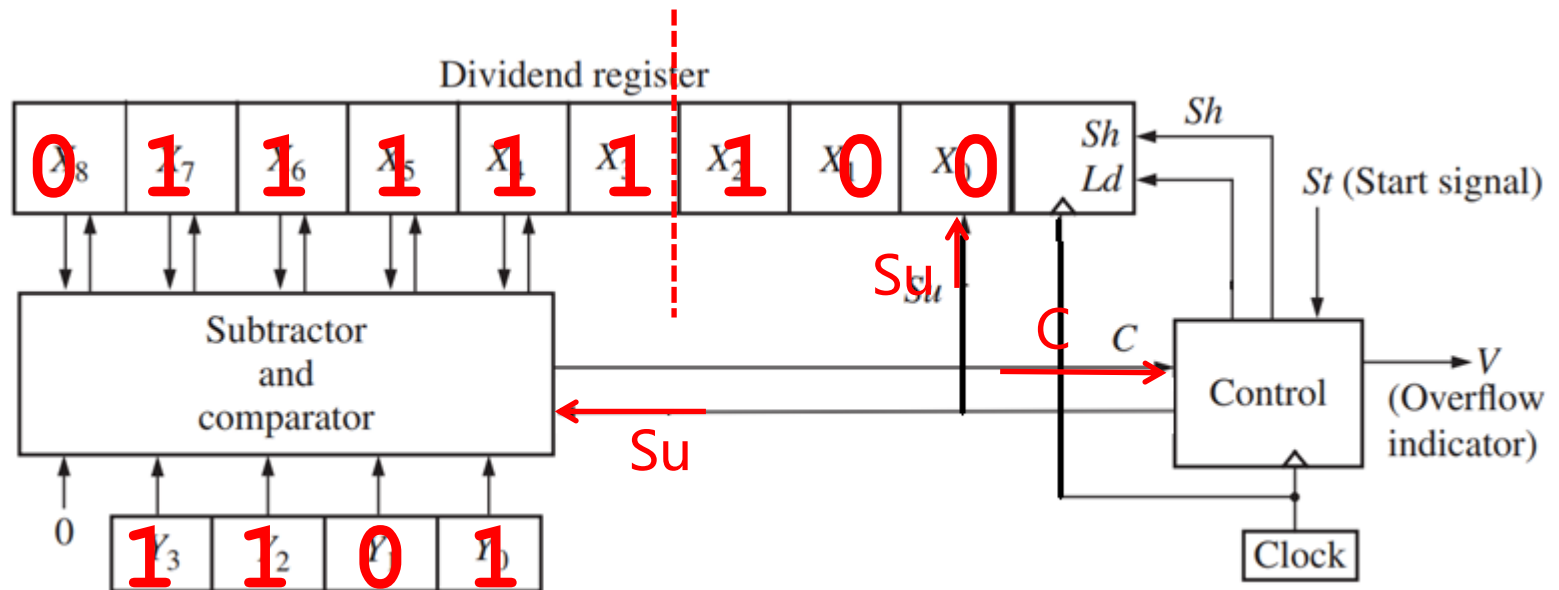
$$\begin{array}{r}
 \overline{) 1010} \\
 \underline{1101} \\
 0111 \\
 \underline{0000} \\
 1111 \\
 \underline{1101} \\
 0101 \\
 \underline{0000} \\
 0101
 \end{array}$$




4.12.1 Unsigned Dividers

 


(135 ÷ 13 = 10 with 5)

```

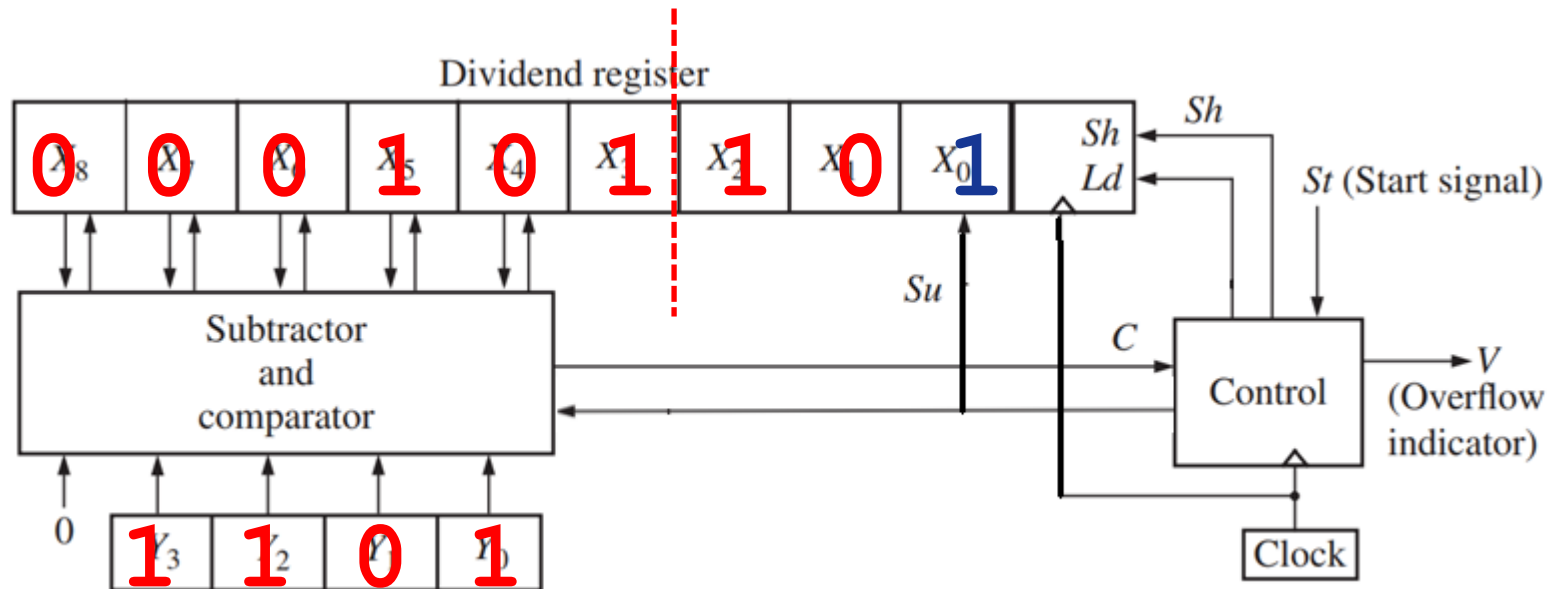      1010
1101 ) 10000111
      1101
      ----
       0111
       0000
       ----
        1111
        1101
        ----
         0101
         0000
         ----
          0101
  
```




4.12.1 Unsigned Dividers

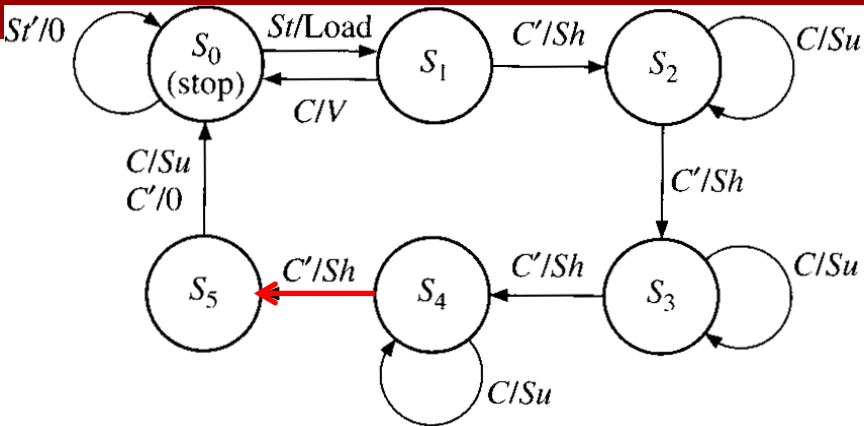


(135 ÷ 13 = 10 with 5)

```

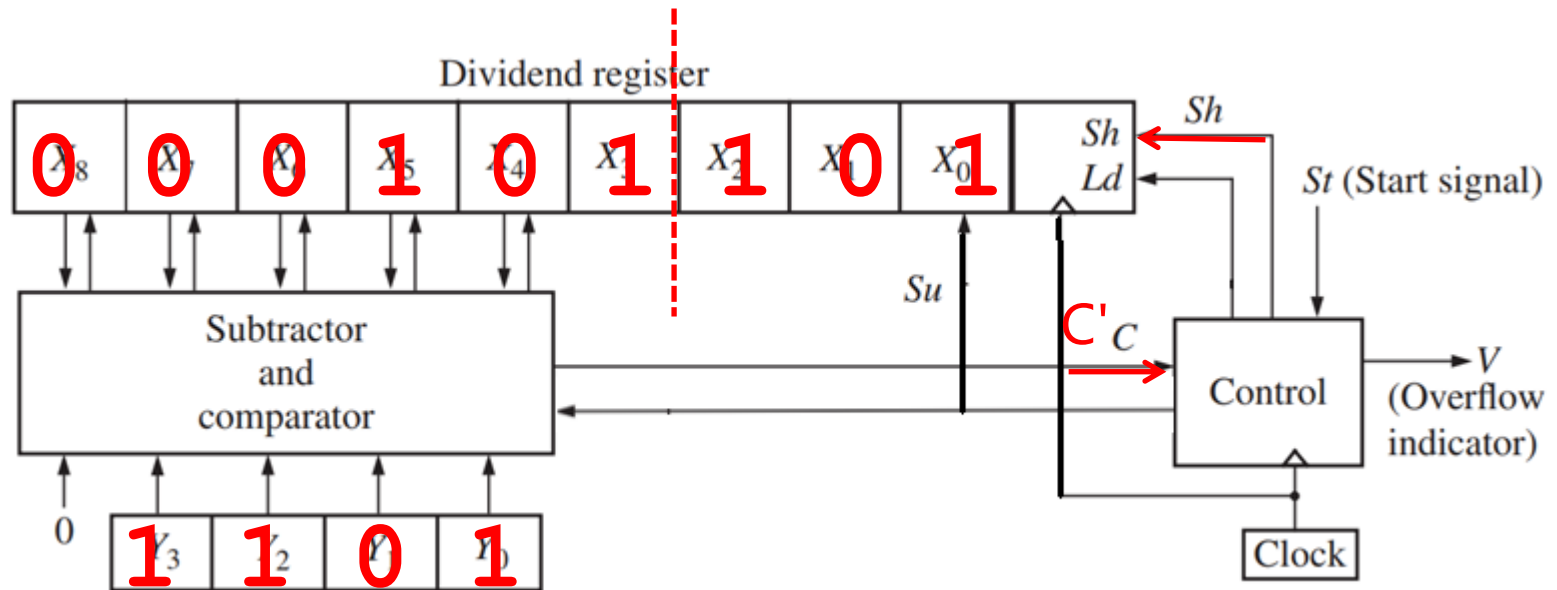      1010
1101 ) 10000111
      1101
      ---
      0111
      0000
      ---
      1111
      1101
      ---
      0101
      0000
      ---
      0101
  
```




4.12.1 Unsigned Dividers

 


(135 ÷ 13 = 10 with 5)
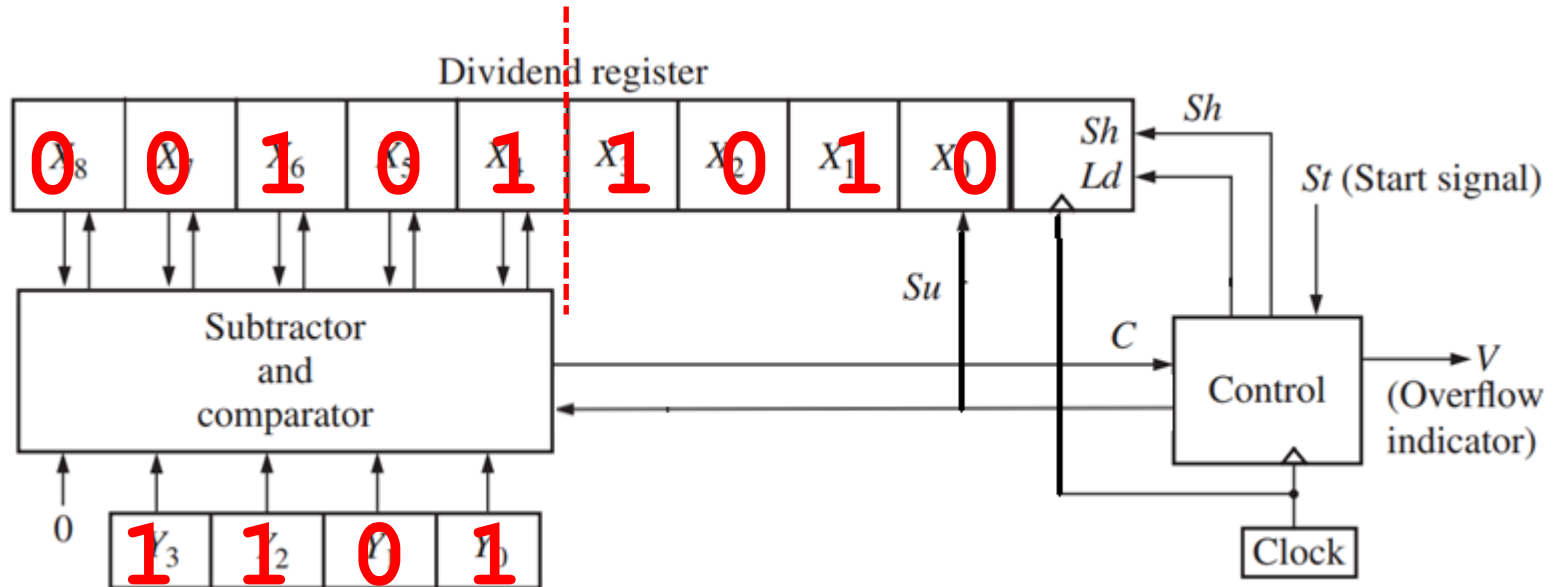
$$\begin{array}{r}
 \overline{) 1010} \\
 \underline{1101} \\
 10000111 \\
 \overline{) 1101} \\
 \underline{0111} \\
 \underline{0000} \\
 1111 \\
 \underline{1101} \\
 0101 \\
 \underline{0000} \\
 0101
 \end{array}$$




4.12.1 Unsigned Dividers

 


(135 ÷ 13 = 10 with 5)

```

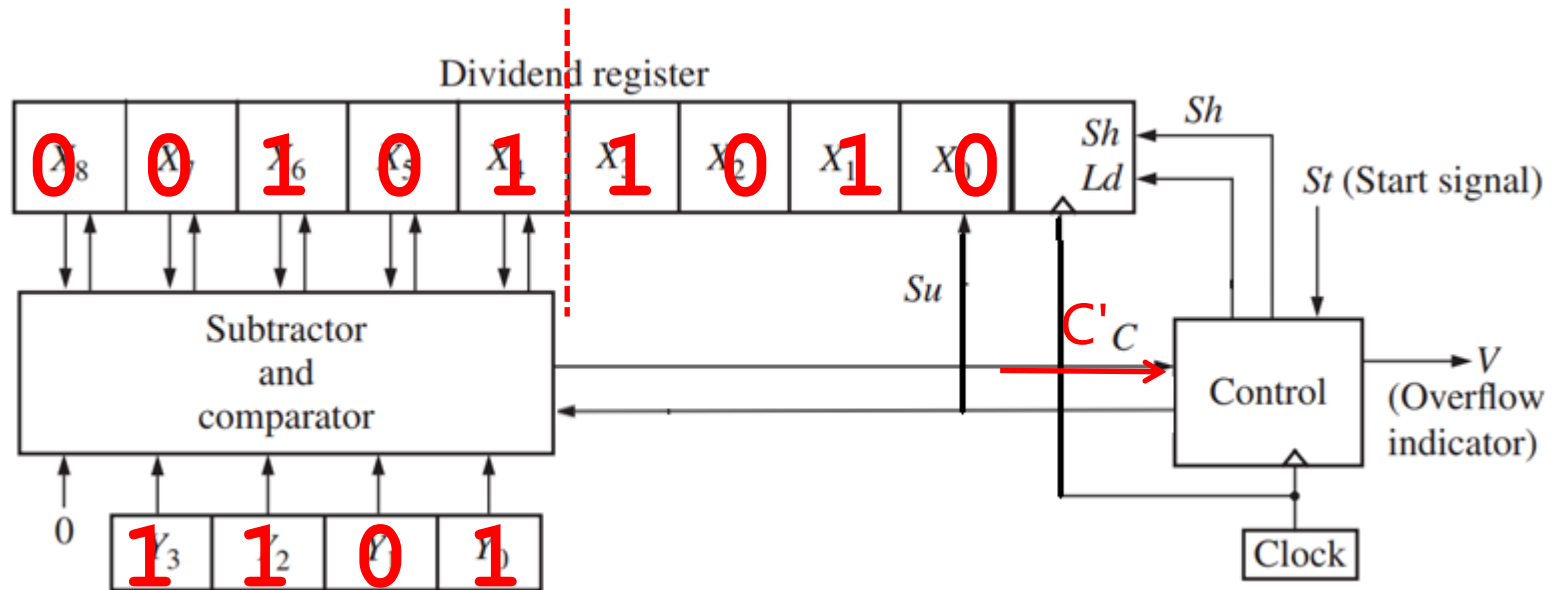      1010
1101 ) 10000111
      1101
      ----
       0111
       0000
       ----
        1111
        1101
        ----
         0101
         0000
         ----
          0101
  
```




12 Binary Dividers

 

(135 ÷ 13 = 10 with 5)

```

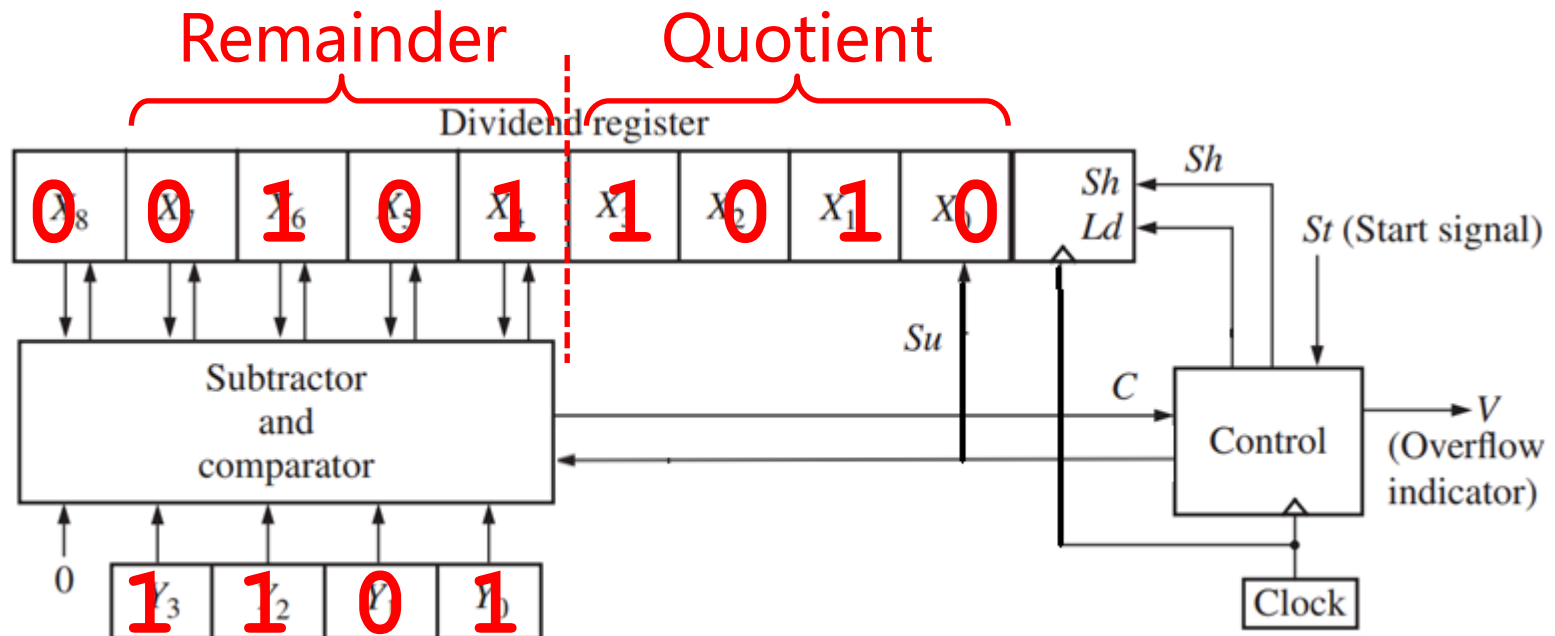      1010
    1101 ) 10000111
          1101
          ---
          0111
          0000
          ---
          1111
          1101
          ---
          0101
          0000
          ---
          0101
  
```




shift		0	1	0	0	0	0	1	1	1	Dividend
			1	1	0	1	Divisor				
Compare, subtract		1	0	0	0	0	1	1	1	?	
			1	1	0	1					
shift		0	0	0	1	1	1	1	1	1	
			1	1	0	1					
Compare, shift		0	0	1	1	1	1	1	1	?	
			1	1	0	1					
Compare, subtract		0	1	1	1	1	1	1	0	?	
			1	1	0	1					
shift		0	0	0	1	0	1	1	0	1	
			1	1	0	1					
Compare, shift		0	0	1	0	1	1	0	1	?	
			1	1	0	1					
		0	0	1	0	1	1	0	1	0	
Rema i n d e r						Quot i e n t					

4.12.1 Unsigned Dividers


Overflow (溢出)

Overflow occurs when the quotient contains **more bits** than are available for storing the quotient


quotient > 15 → overflow

 

12 Binary Dividers

 



Example:
 $135 / 7 = 19 \dots 2$

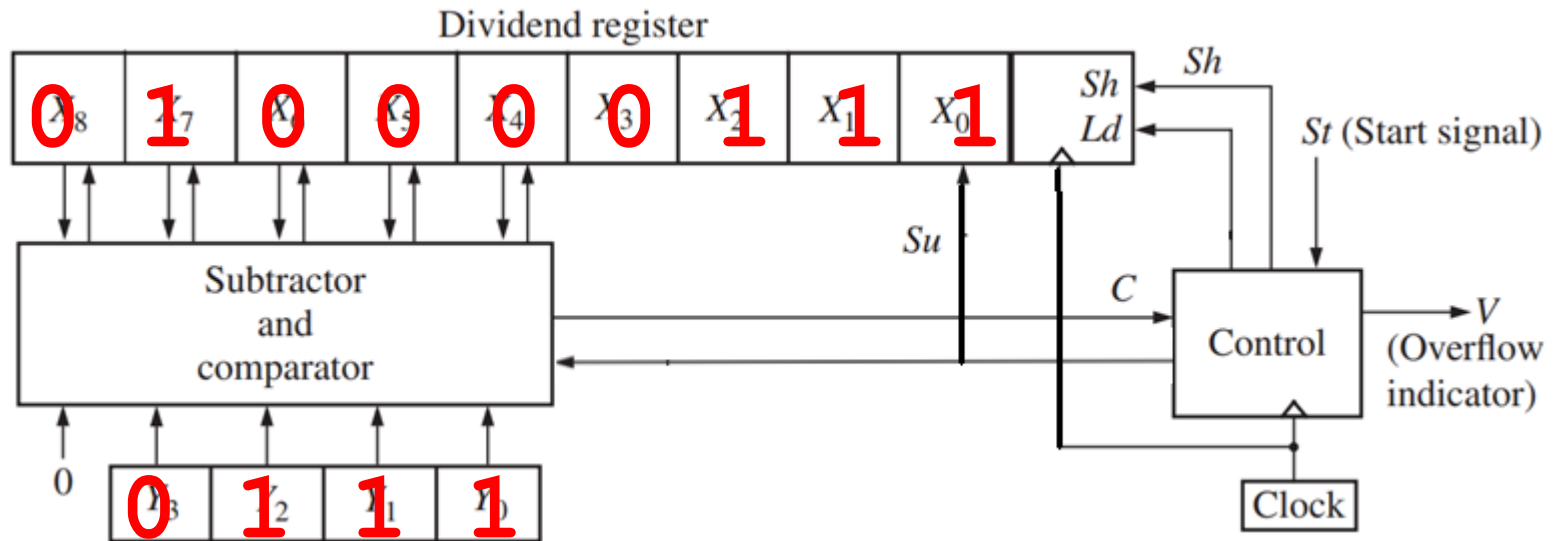

12 Binary Dividers

Example:


$$135 / 7 = 19 \dots 2$$

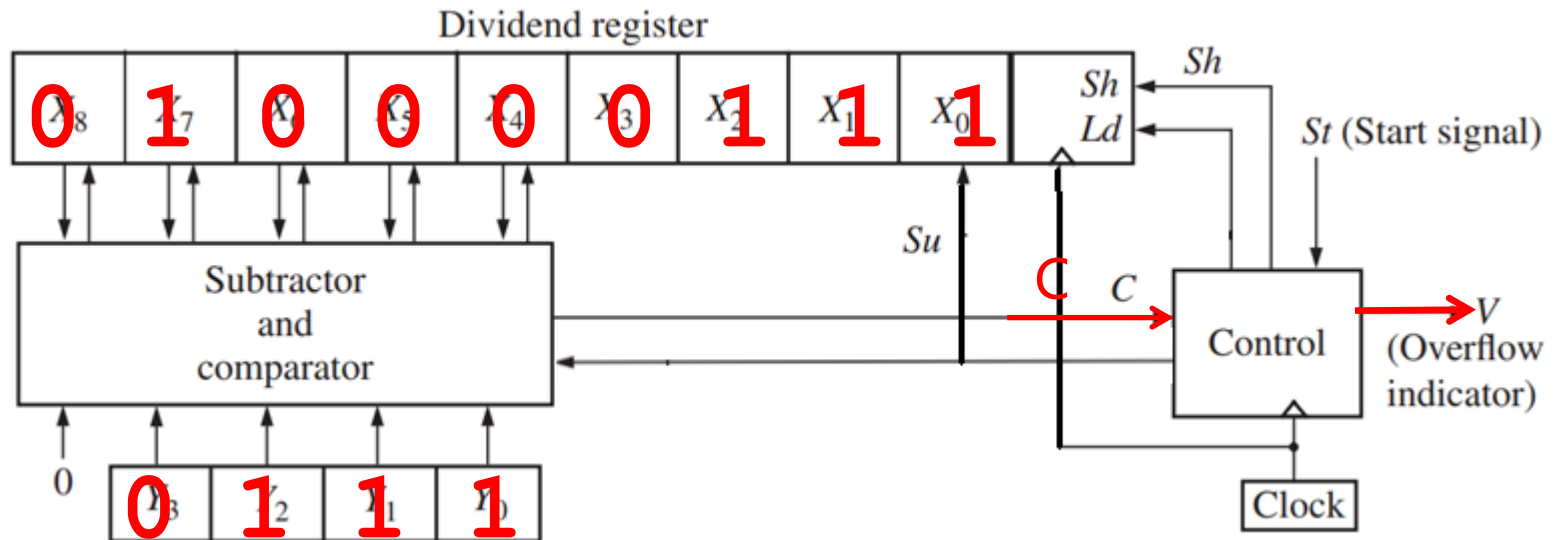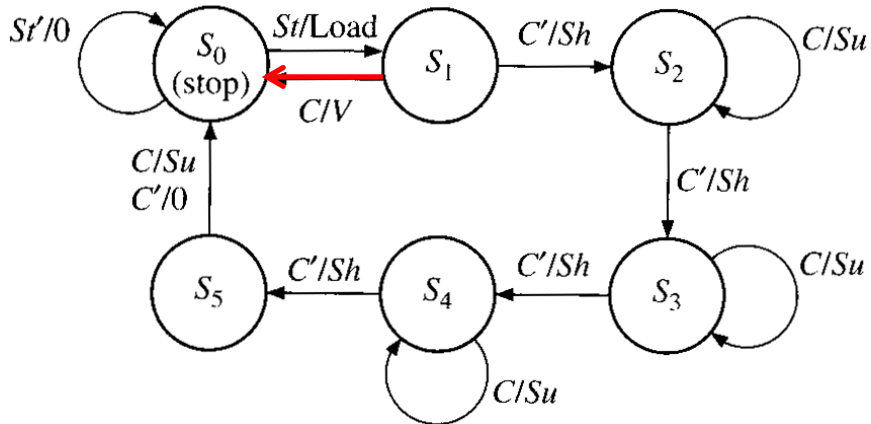

12 Binary Dividers

Overflow


Example: 135 / 7

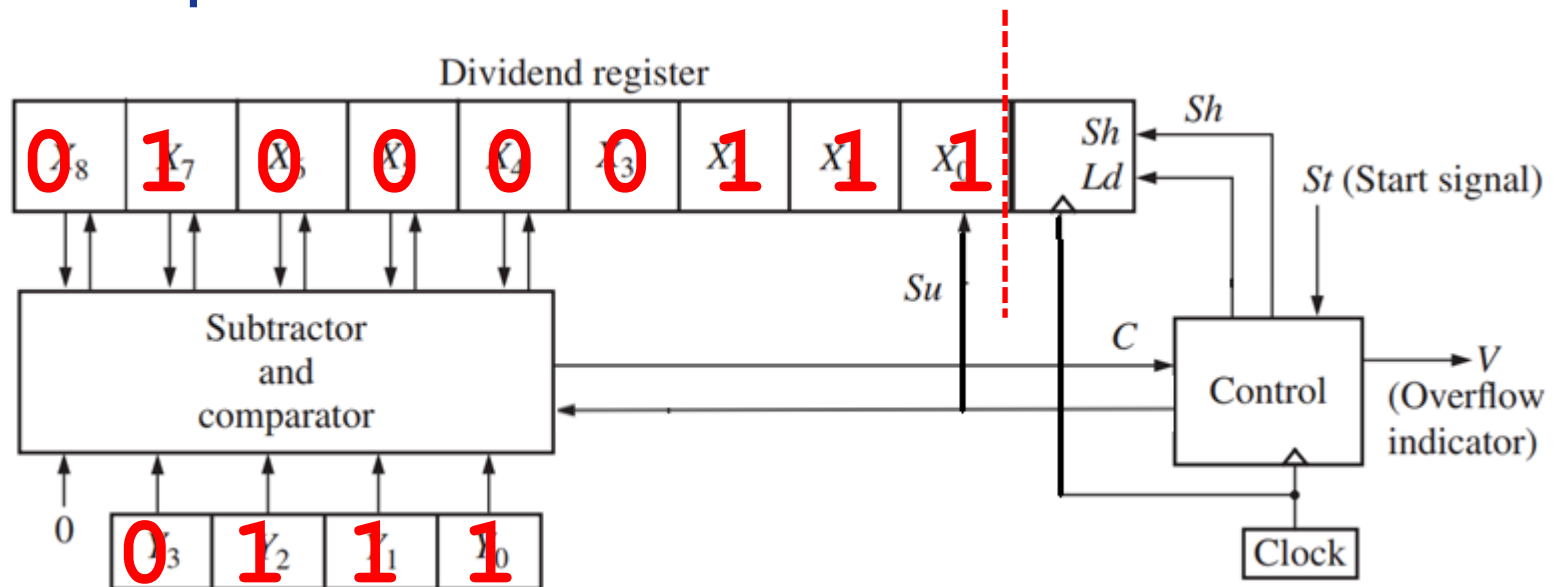

$$X_8X_7X_6X_5X_4 \geq Y_3Y_2Y_1Y_0$$

$$\frac{X_8X_7X_6X_5X_4X_3X_2X_1X_0}{Y_3Y_2Y_1Y_0} \geq \frac{X_8X_7X_6X_5X_40000}{Y_3Y_2Y_1Y_0} = \frac{X_8X_7X_6X_5X_4 \times 16}{Y_3Y_2Y_1Y_0} \geq 16$$

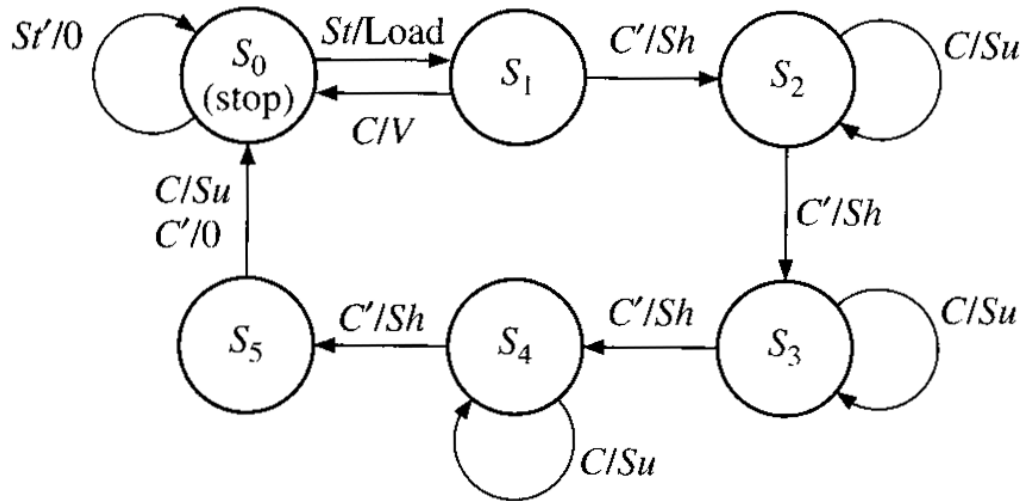State Diagram for Divider Control Circuit




State Table for Divider Control Circuit


State	StC				StC	00	01	11	10
	00	01	11	10					
S_0	S_0	S_0	S_1	S_1	0	0	Load	Load	
S_1	S_2	S_0	—	—	Sh	V	—	—	
S_2	S_3	S_2	—	—	Sh	Su	—	—	
S_3	S_4	S_3	—	—	Sh	Su	—	—	
S_4	S_5	S_4	—	—	Sh	Su	—	—	
S_5	S_0	S_0	—	—	0	Su	—	—	

-- : "don't care" because
St = 0 in $S_1 \sim S_5$

4.12.2 Signed Divider

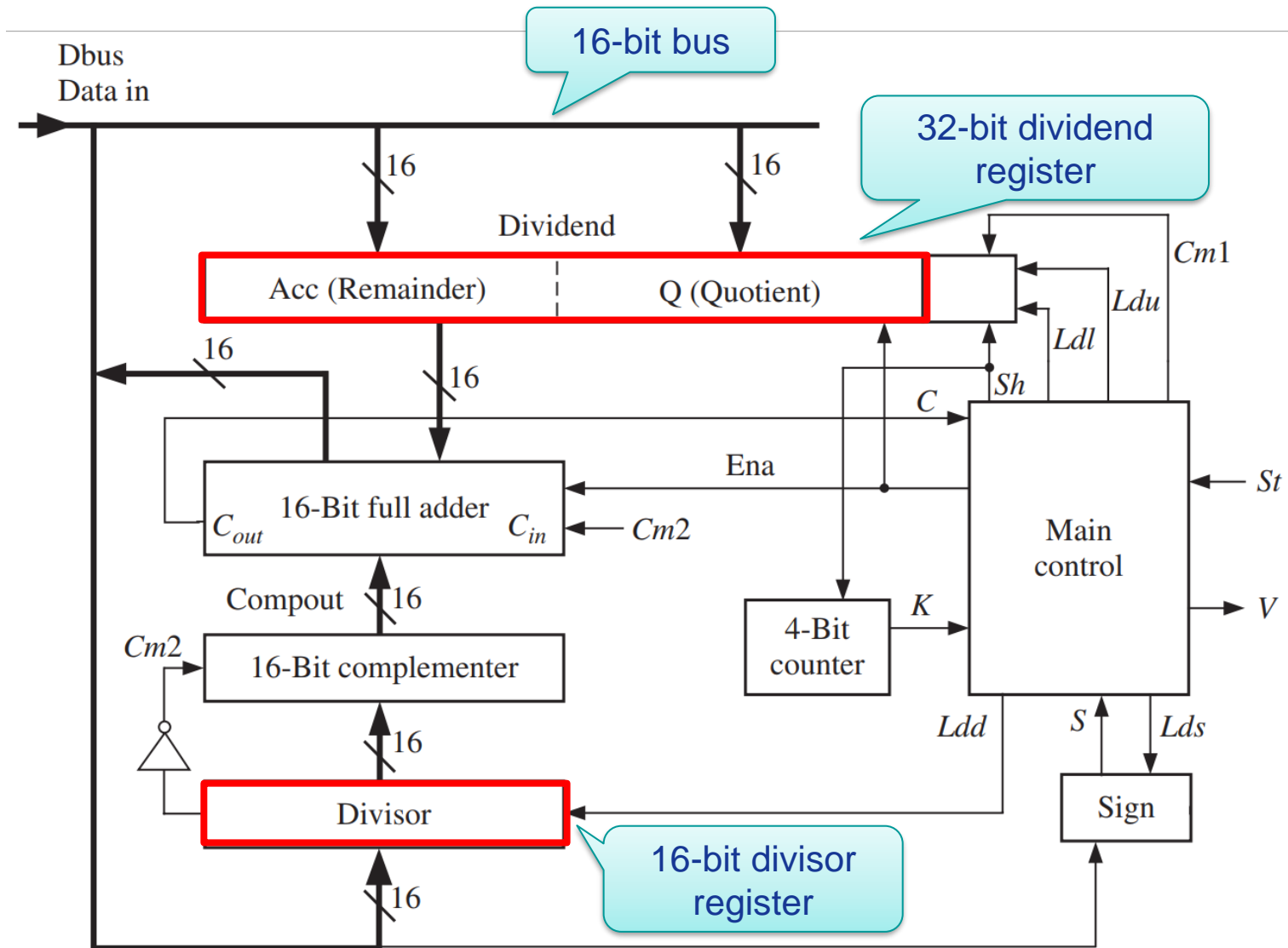


4.12.2 Signed Divider

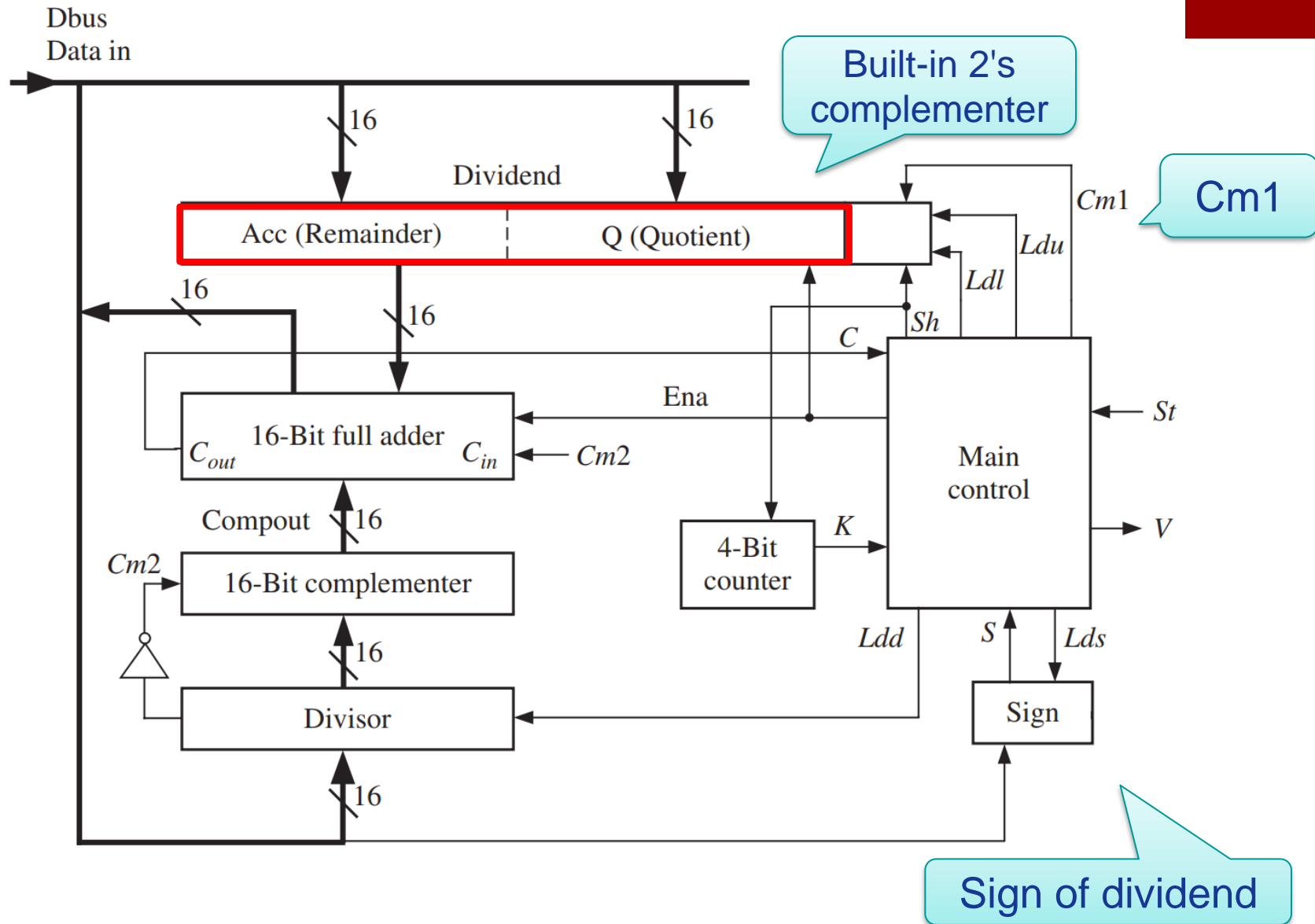




- Cm2: Enable complement
- A positive divisor is complemented and a negative divisor is not


4.12.2 Signed Divider

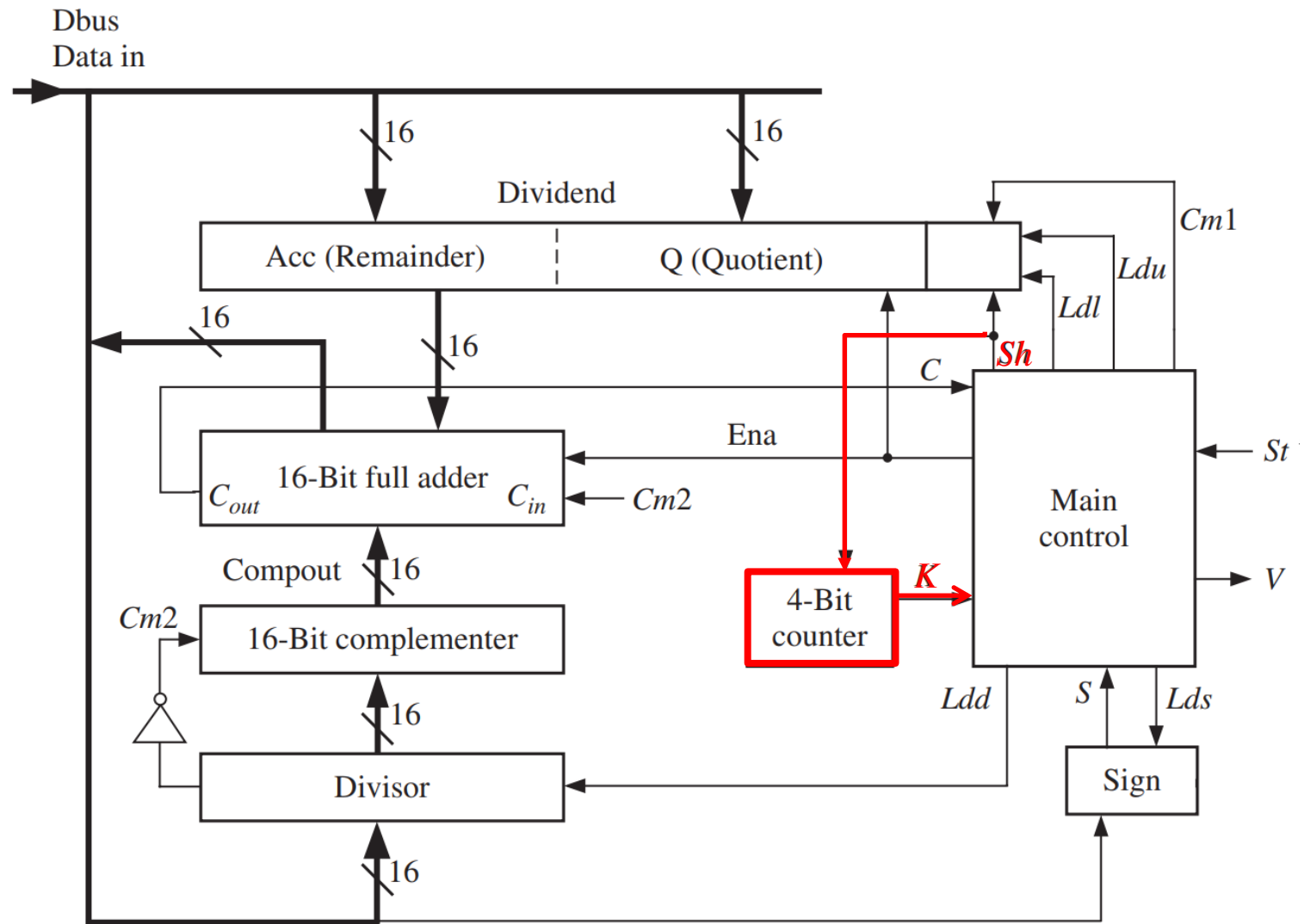

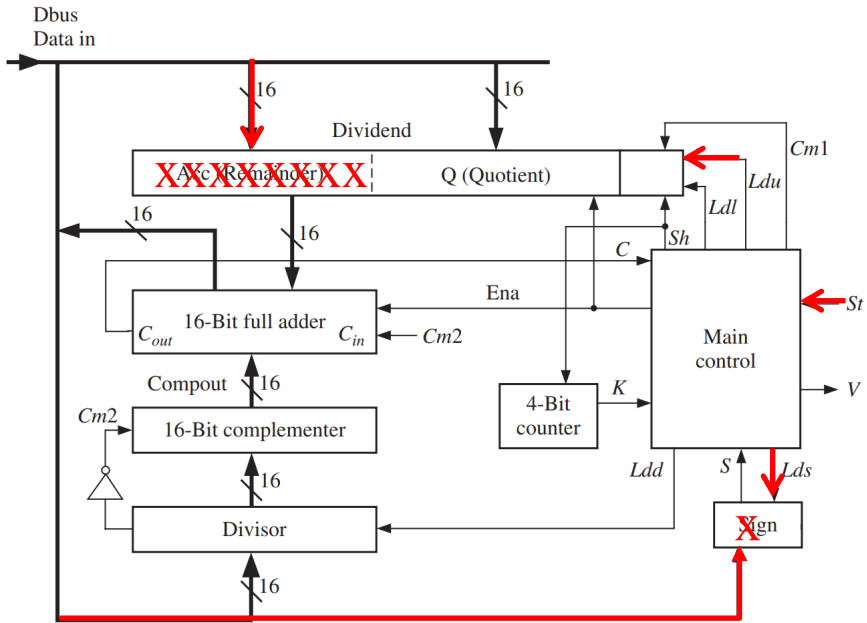
Procedure for carrying out the signed division



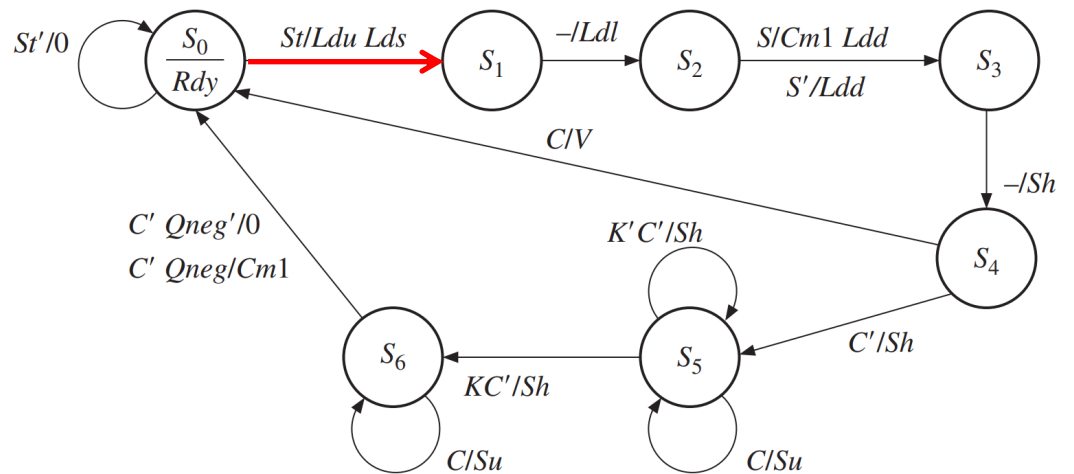
1. Load dividend(31:16) from the bus
Copy dividend(31) into sign flip-flop **S**



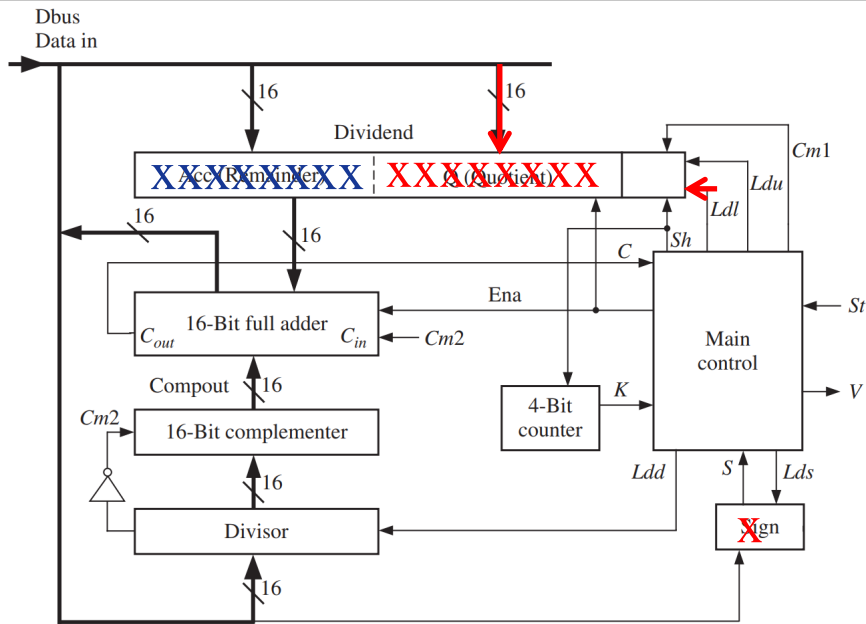
Procedure for carrying out the signed division




2. Load dividend(15:0) from the bus

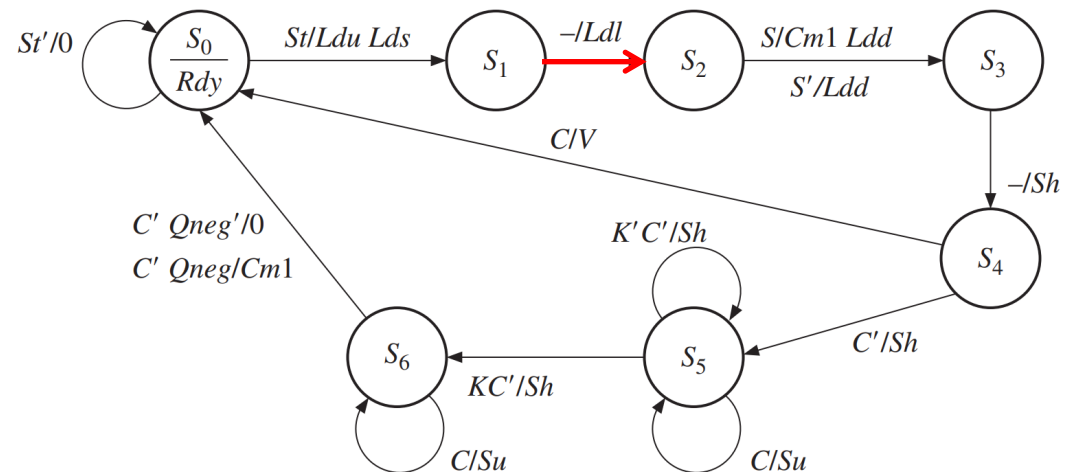

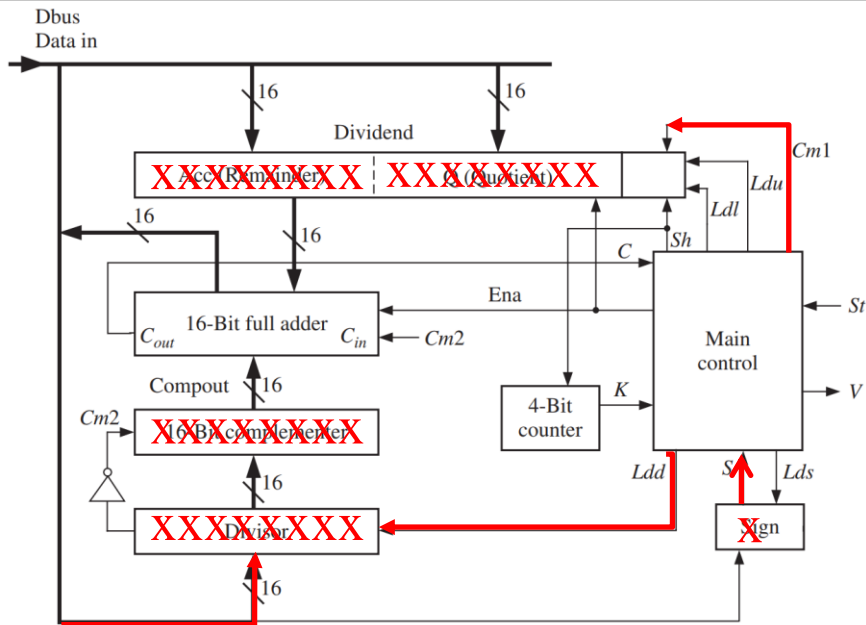
Procedure for carrying out the signed division



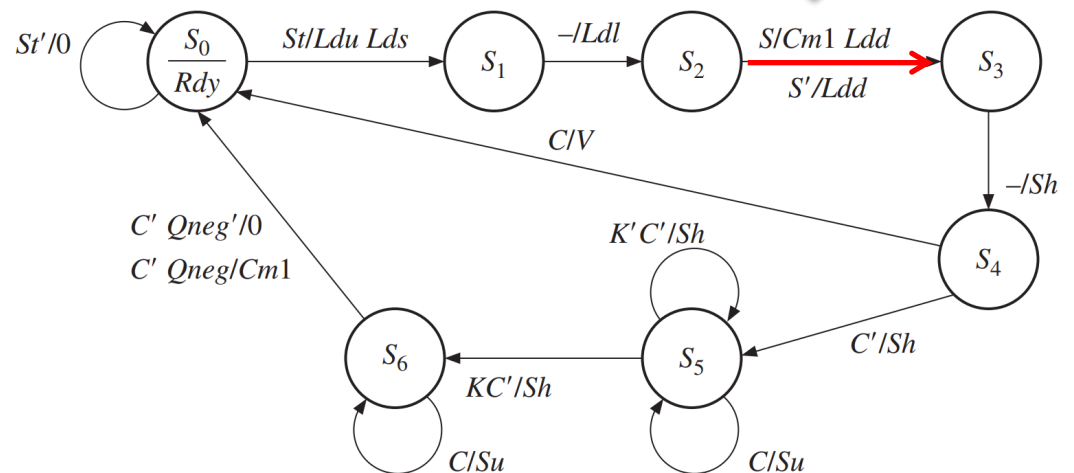
3. Load the divisor from the bus
4. Complement the dividend if it is negative



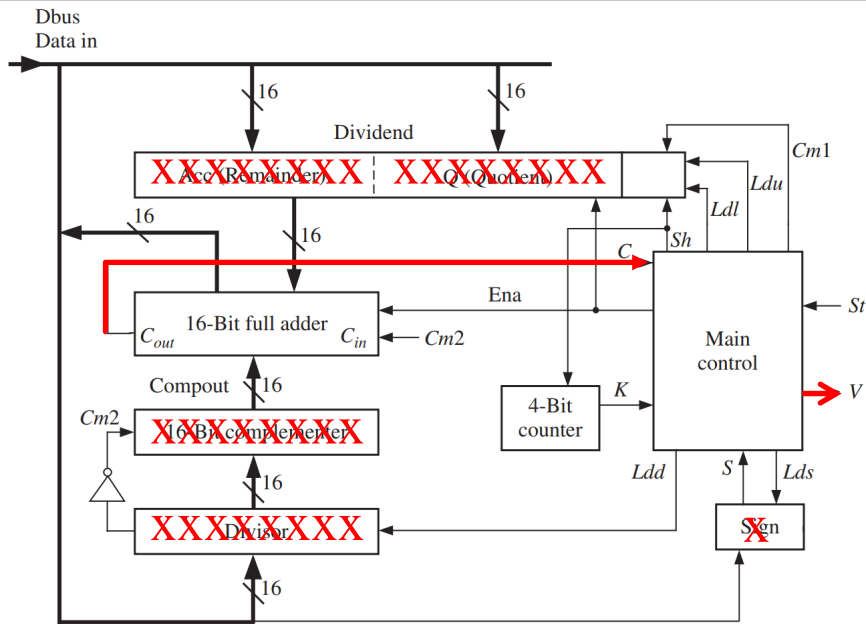Procedure for carrying out the signed division




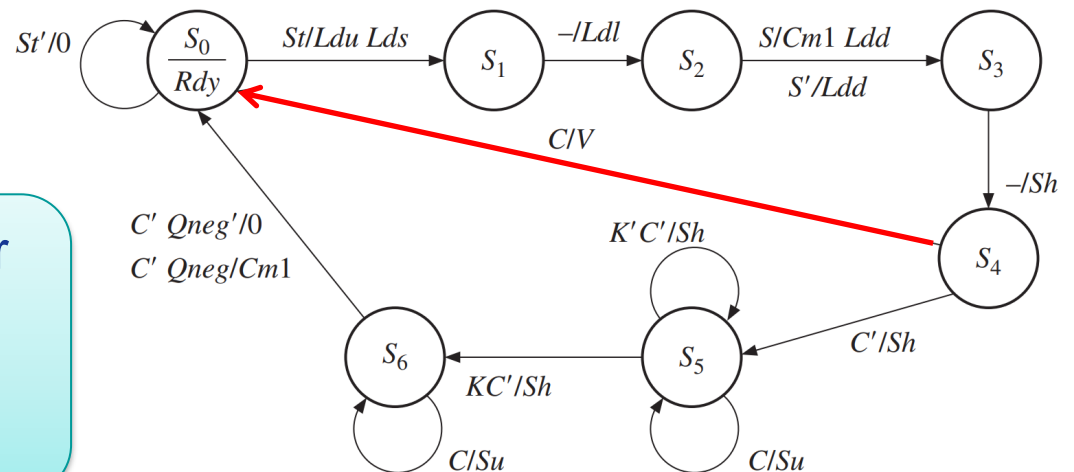5. If an overflow condition is present, go to the done state




- C: Carry output from adder
- If $C = 1$, the divisor can be subtracted from the upper dividend

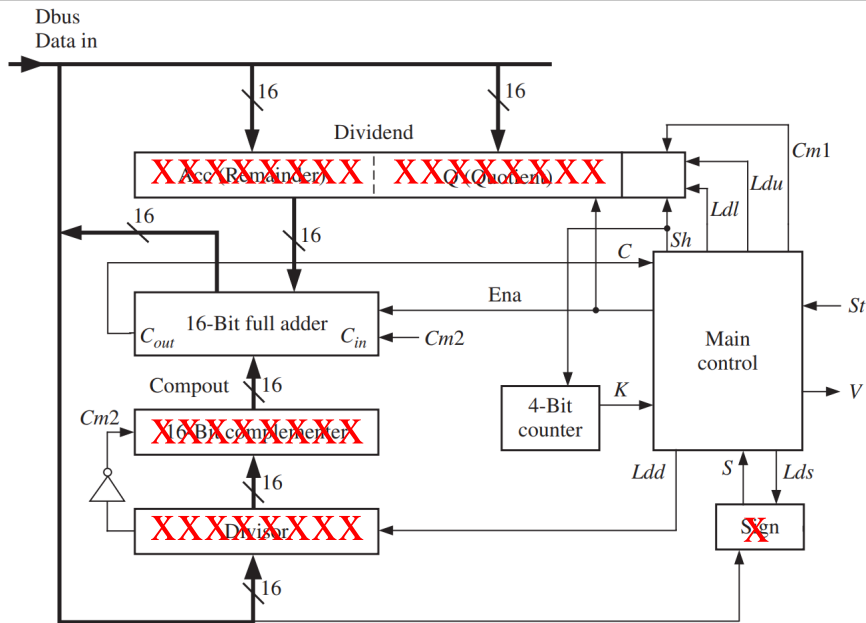
Procedure for carrying out the signed division



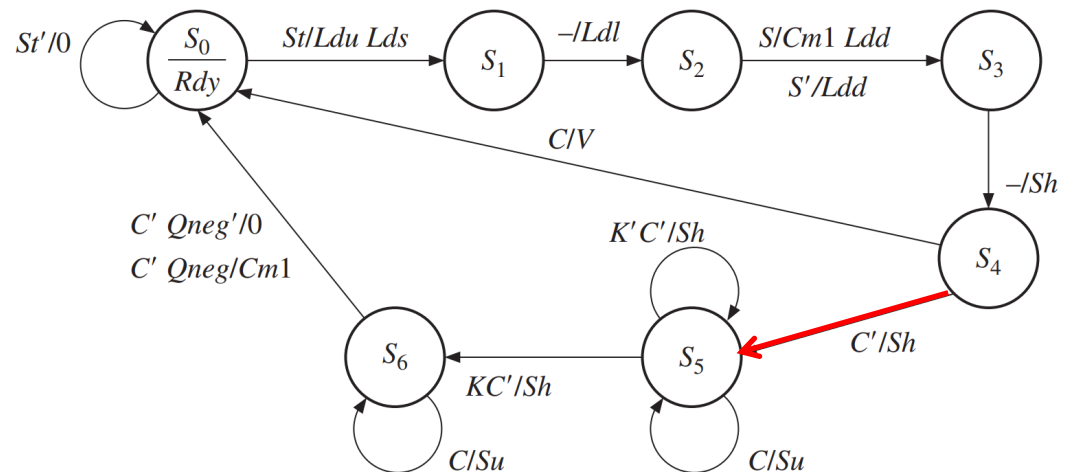6. Else carry out the division by a series of shifts and subtracts




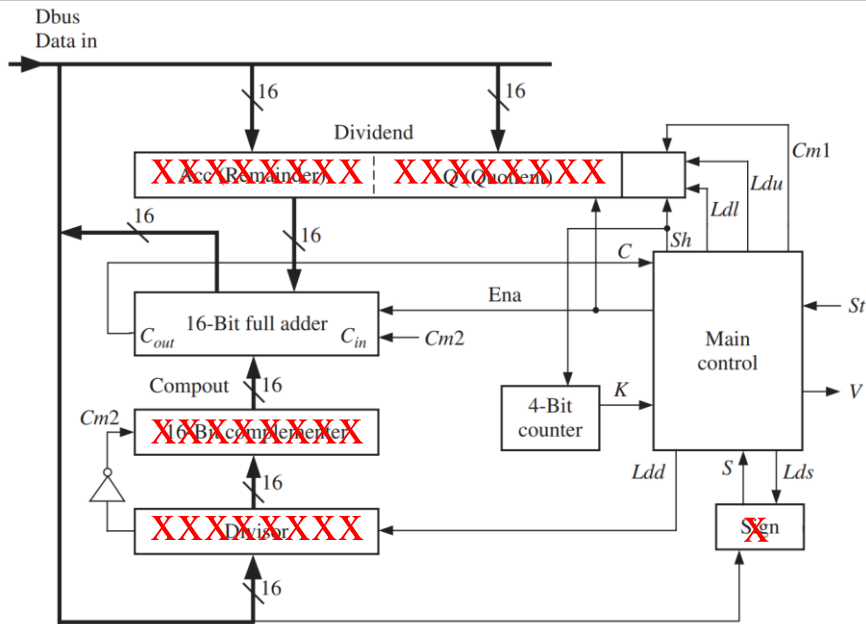Procedure for carrying out the signed division




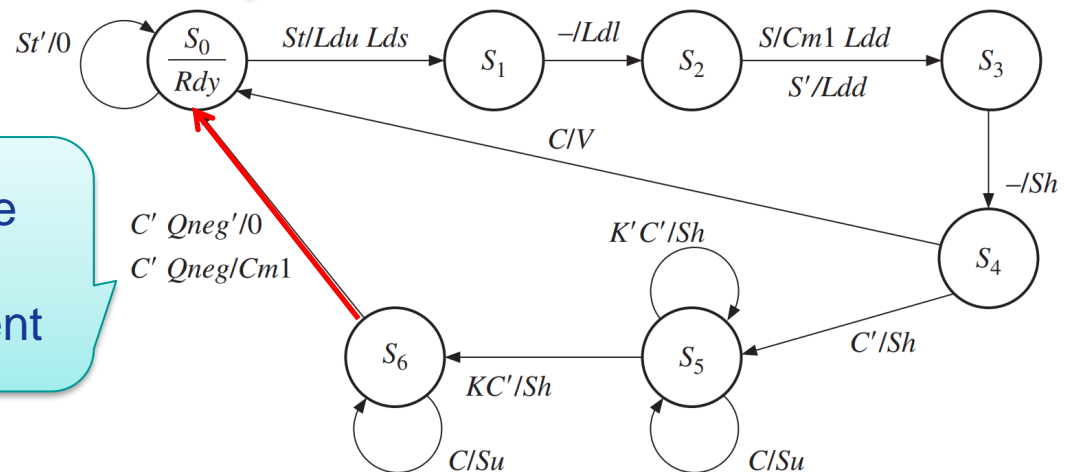7. When division is complete, complement the quotient if necessary, and go to the done state

- Qneg: Quotient will be negative
- Qneg = 1 when the sign of the dividend and divisor are different



VHDL Model of 32-Bit Signed Divider

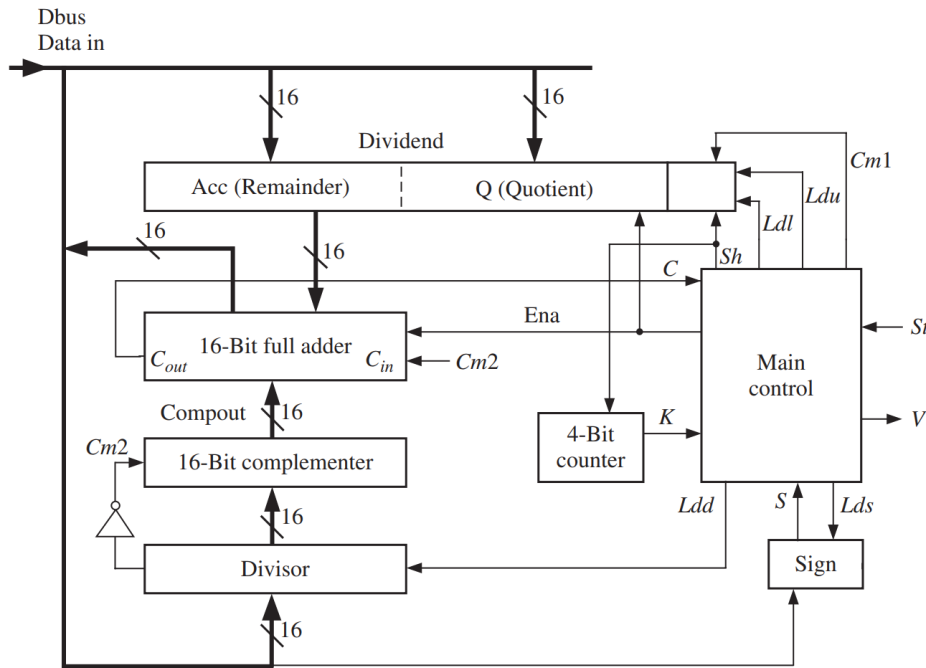


```
library IEEE;
use IEEE.numeric_bit.all;
```

```
entity sdiv is
    port(CLK, St: in bit;
         Dbus: in unsigned(15 downto 0);
         Quotient: out unsigned(15 downto 0);
         V, Rdy: out bit);
end sdiv;
```


Remainder is not
an output here

VHDL Model of 32-Bit Signed Divider

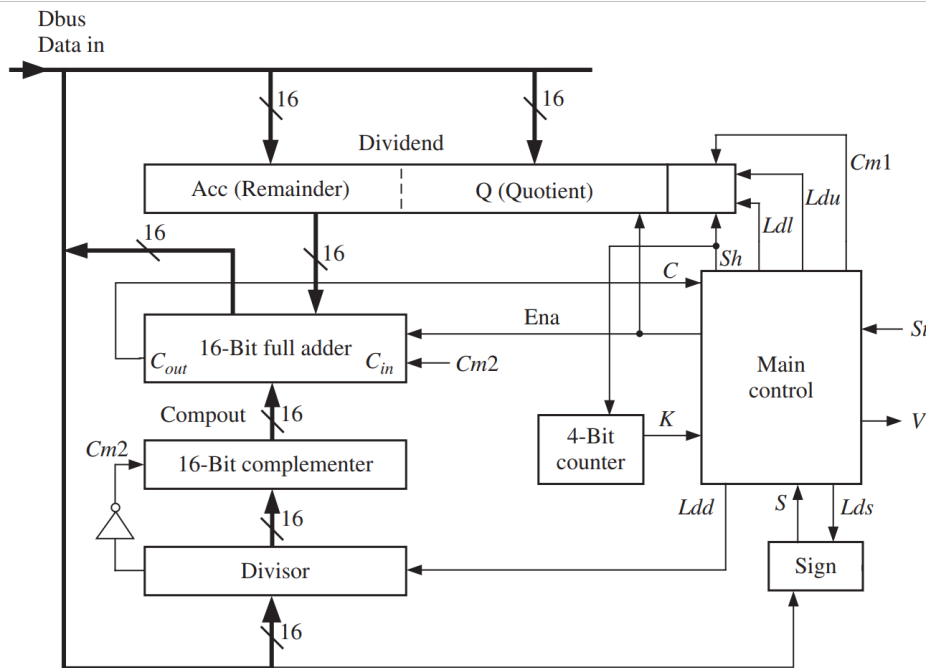

```
architecture Signdiv of sdiv is
    signal State: integer range 0 to 6;
    signal Count: unsigned(3 downto 0); -- integer range 0 to 15
    signal Sign, C, Cm2: bit;
    signal Divisor, Sum, Compout: unsigned(15 downto 0);
    signal Dividend: unsigned(31 downto 0);
    alias Acc: unsigned(15 downto 0) is Dividend(31 downto 16);
```

VHDL Model of 32-Bit Signed Divider

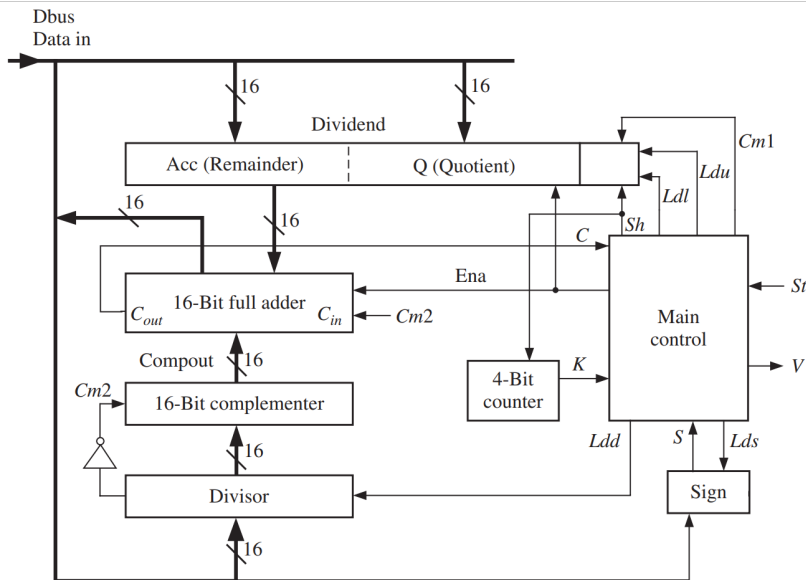

```

begin
    Cm2 <= not divisor(15);
    compout <= divisor when Cm2 = '0'
                else not divisor;
    Sum <= Acc + compout + unsigned'(0=>Cm2);
    C <= not Sum(15);
    Quotient <= Dividend(15 downto 0);
    Rdy <= '1' when State = 0 else '0';
    process(CLK)
    begin


```

VHDL Model of 32-Bit Signed Divider

```

process(CLK)
begin
  if CLK'event and CLK = '1' then
    case State is
      when 0 =>
        if St = '1' then
          Acc <= Dbus;      -- load upper dividend
          Sign <= Dbus(15);
          State <= 1;
          V <= '0';         -- initialize overflow
          Count <= "0000";  -- initialize counter
        end if;
    end case;
  end if;

```

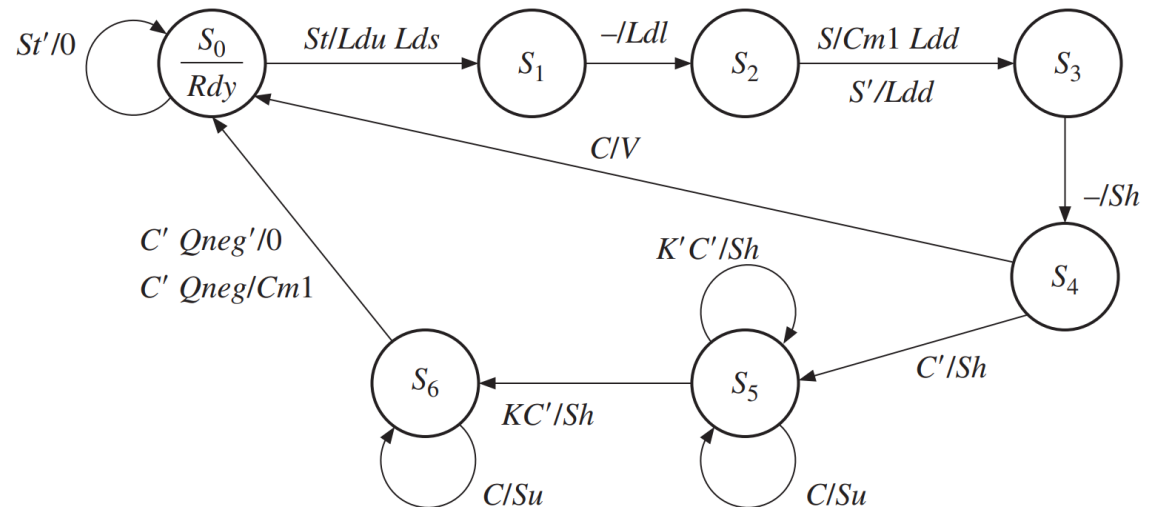


VHDL Model of 32-Bit Signed Divider

```

when 1 =>
    Dividend(15 downto 0) <= Dbus; -- load lower dividend
    State <= 2;
when 2 =>
    Divisor <= Dbus;
    if Sign = '1' then -- two's complement Dividend if necessary
        Dividend <= not Dividend + 1;
    end if;
    State <= 3;
when 3 =>
    Dividend <= Dividend(30 downto 0) & '0'; -- left shift
    Count <= Count + 1;
    State <= 4;

```

 


VHDL Model of 32-Bit Signed Divider

```

when 4 =>
  if C = '1' then
    V <= '1';
    State <= 0;
  else
    Dividend <= Dividend(30 downto 0) & '0';
    Count <= Count + 1;
    State <= 5;
  end if;
when 5 =>
  if C = '1' then
    Acc <= Sum;      -- subtract
    Dividend(0) <= '1';
  else
    Dividend <= Dividend(30 downto 0) & '0';  -- left shift
    if Count = 15 then State <= 6; end if;      -- KC'
    Count <= Count + 1;
  end if;

```

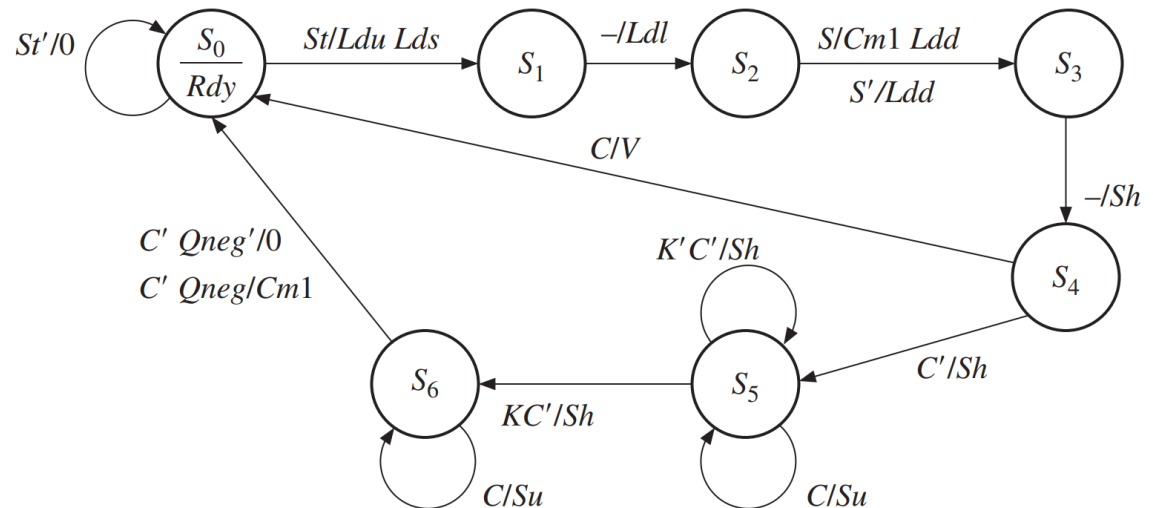


VHDL Model of 32-Bit Signed Divider

```

when 6 =>
  State <= 0;
  if C = '1' then
    Acc <= Sum;      -- subtract
    Dividend(0) <= '1';
    State <= 6;
  elsif (Sign xor Divisor(15)) = '1' then  -- C'Qneg
    Dividend <= not Dividend + 1;         -- 2's complement Dividend
  end if;
end case;
end if;
end process;
end Signdiv;

```

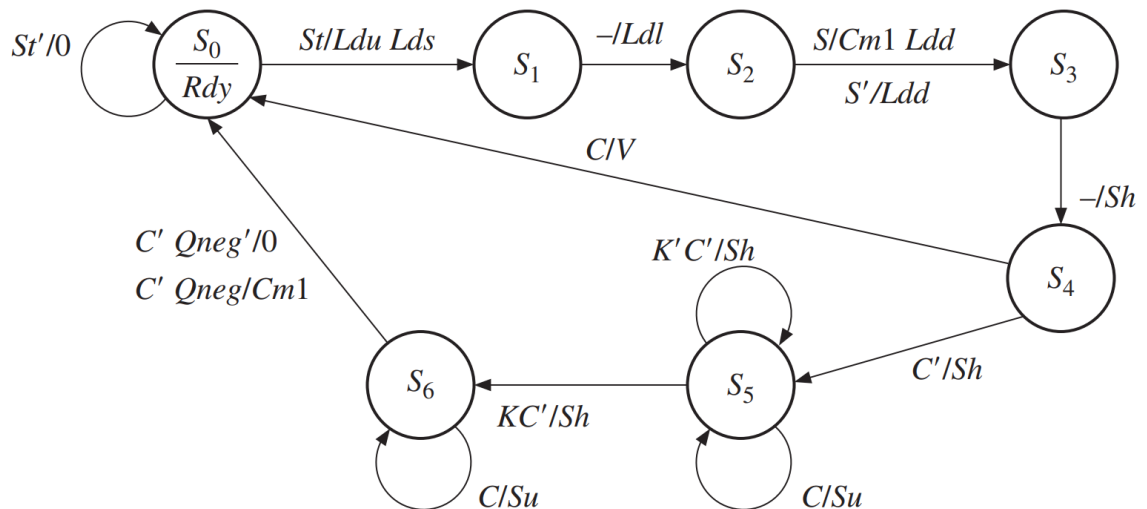

Test bench for signed divider

```
library IEEE;
use IEEE.numeric_bit.all;

entity testsdiv is
end testsdiv;

architecture test1 of testsdiv is
  component sdiv
    port (CLK, St: in bit;
          Dbus: in unsigned(15 downto 0);
          Quotient: out unsigned(15 downto 0);
          V, Rdy: out bit);
  end component;

  constant N: integer := 12;  -- test sdiv1 N times
  type arr1 is array(1 to N) of unsigned(31 downto 0);
  type arr2 is array(1 to N) of unsigned(15 downto 0);
  constant dividendarr: arr1 := (X"0000006F", X"07FF00BB", X"FFFFFFE08",
    X"FF80030A", X"3FFF8000", X"3FFF7FFF", X"C0008000", X"C0008000",
    X"C0008001", X"00000000", X"FFFFFFFF", X"FFFFFFFF");
  constant divisorarr: arr2 := (X"0007", X"E005", X"001E", X"EFFA", X"7FFF", X"7FFF",
    X"7FFF", X"8000", X"7FFF", X"0001", X"7FFF", X"0000");
  signal CLK, St, V, Rdy: bit;
  signal Dbus, Quotient, divisor: unsigned(15 downto 0);
  signal Dividend: unsigned(31 downto 0);
  signal Count: integer range 0 to N;
```

Test bench for signed divider

```
begin
  CLK <= not CLK after 10 ns;
  process
  begin
    for i in 1 to N loop
      St <= '1';
      Dbus <= dividendarr(i) (31 downto 16);
      wait until (CLK'event and CLK = '1');
      Dbus <= dividendarr(i) (15 downto 0);
      wait until (CLK'event and CLK='1');
      Dbus <= divisorarr(i);
      St <= '0';
      dividend <= dividendarr(i) (31 downto 0); -- save dividend for listing
      divisor <= divisorarr(i); -- save divisor for listing
      wait until (Rdy = '1'); -- save index for triggering
      count <= i;
    end loop;
  end process;
  sdiv1: sdiv port map(CLK, St, Dbus, Quotient, V, Rdy);
end test1;
```

Test bench for signed divider

```
VSIM 70> add list -notrigger dividend divisor quotient V -trigger count
VSIM 71> run 5300 ns
```

ns		/testsddiv/Dividend		/testsddiv/V	
delta		/testsddiv/divisor		/testsddiv/Quotient	
				/testsddiv/Count	
0	+0	00000000	0000	0000 0 0	
470	+3	0000006F	0007	000F 0 1	
910	+3	07FF00BB	E005	BFFE 0 2	
1330	+3	FFFFFFE08	001E	FFF0 0 3	
1910	+3	FF80030A	EFFA	07FC 0 4	
2010	+3	3FFF8000	7FFF	0000 1 5	
2710	+3	3FFF7FFF	7FFF	7FFF 0 6	
2810	+3	C0008000	7FFF	0000 1 7	
3510	+3	C0008000	8000	7FFF 0 8	
4210	+3	C0008001	7FFF	8001 0 9	
4610	+3	00000000	0001	0000 0 A	
5010	+3	FFFFFFFF	7FFF	0000 0 B	
5110	+3	FFFFFFFF	0000	0002 1 C	